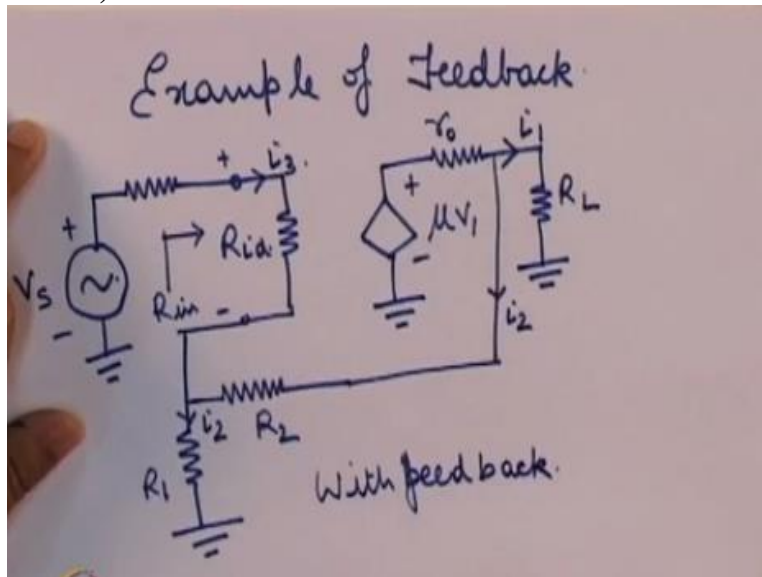


Analog Circuits
Prof. Jayanta Mukherjee
Department of Electrical Engineering
Indian Institute of Technology-Bombay

Week -04
Module -01
Effect of feedback and stability


Hello, welcome to another module of this course analog circuits, we are now in the week four and in the previous module last week we had covered about feedback and the various effects of feedback like gain the sensitivity bandwidth enhancement increase in linearity.

(Refer Slide Time: 00:45)



In this module let us see an example of feedback that is applied to a circuit suppose we have a circuit like this now the circuit this is with feedback and the circuit without feedback is like this.

(Refer Slide Time: 02:50)

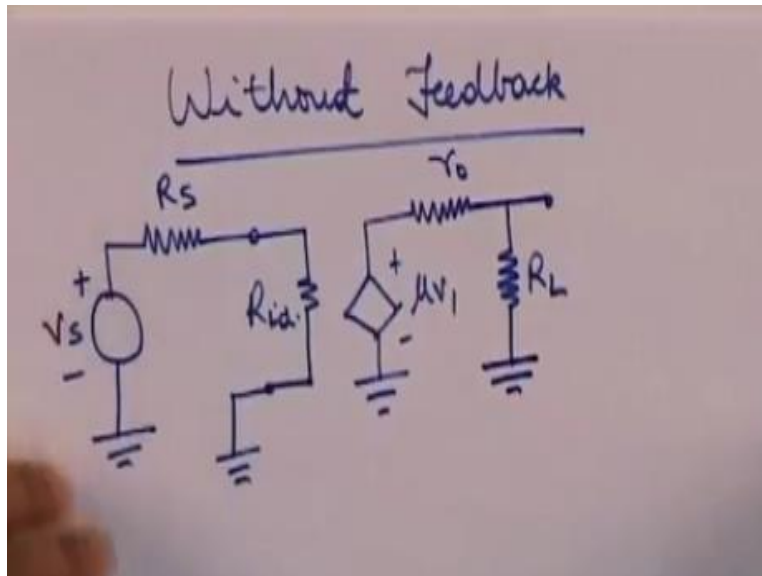

So after feedback the only difference between this circuit and this circuit is this additional resistance is R_1 and R_2 which are connected like this now what is the impact of these resistances on the overall performance, first note that here we are tapping the voltage at the output and feeding it back to the input at the input when we feedback what is happening is some portion of the input voltage that should have been applied directly is being subtracted by an amount equal to this voltage or by an amount equal to the voltage appearing across R_1 .

(Refer Slide Time: 05:07)

Without Feedback

$$V_o = \frac{\mu V_1}{R_L + r_o} \times R_L$$

$$= \frac{\mu V_s R_{id}}{R_s + R_{id}} \times \frac{R_L}{R_L + r_o}$$

So this is an example of what we call voltage-voltage feedback it is a negative feedback but the type of negative feedback is voltage-voltage ok, so then what do we see what we see here is The output voltage V_0 is given by μV_1 upon $R_L + r_o$ times R_L which in turn is $= \mu V_s R_{id}$ upon

$R_s + R_{id}$ times R_L upon $+ r_o$ so this is my expression without feedback now with feedback my output voltage is given by an expression which is like this.

(Refer Slide Time: 06:14)

$$A_v = \frac{v_o}{v_s} = \frac{m}{1 + mn}$$


$$\text{where, } m = \frac{\mu [R_L // (R_1 + R_2)]}{[R_L // (R_1 + R_2)] + r_o}$$

$$\times \frac{R_{id}}{R_{id} + R_s + (R_1 // R_2)}$$

$$m = \frac{R_1}{R_1 + R_2}$$

And this N is given as like this, now another effect of feedback which I did not discuss in the previous module was that the output and input impedances depending on the kind of feedback that is provided the output and input impedances are also modified so for a voltage amplifier as you know.

(Refer Slide Time: 08:02)

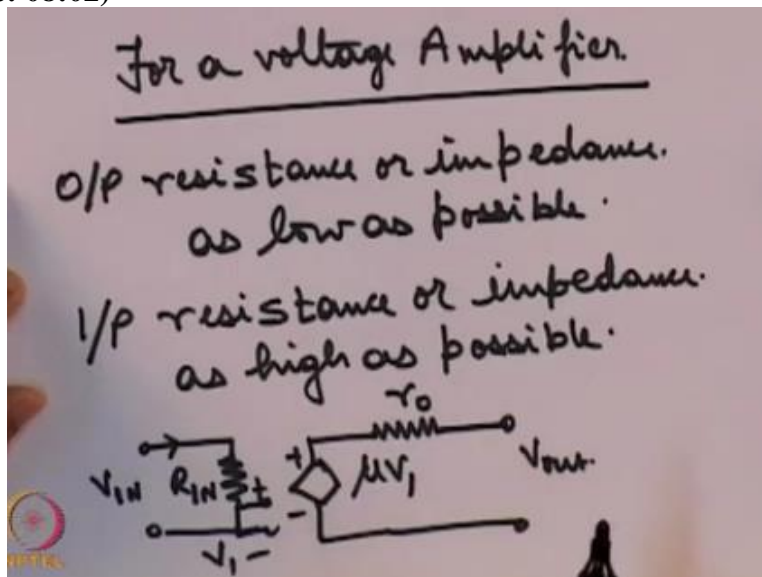


So for a voltage amplifier as you know output resistance or impedance as low as possible, why an input resistance or impedance as high as possible why is this because if we go back to the model of a voltage amplifier so in a voltage amplifier we have a voltage dependent voltage

source an input voltage V_{in} with input impedance R_{in} any output impedance r_0 and output voltage is V_o .

Now the reason this R_{in} should be as high as possible is because we want entire V_{in} to appear at the input okay should I should have mentioned, so this is V_1 is the voltage that is actually appearing in the inside of the amplifier removed from R_L and that voltage dependent voltage source produces an output μV_1 this is proportional to V_1 this voltage V_1 if R_{in} is not very high then there will be some current flowing through this R_{in} as a result of which the entire V_{in} will not appear at V_1 .

On the other hand if R_{in} is very high then no current will flow inside R_{in} and therefore the entire voltage V_{in} will appear at the input for the output however the scenario is different here we want this μV_1 to appear completely at the output so to appear completely at the output it should face as less potential drop across this r_0 as possible in other words this r_0 should be as low as possible okay let me take a different example of suppose we have what is called a trans conductance amplifier.

(Refer Slide Time: 11:23)

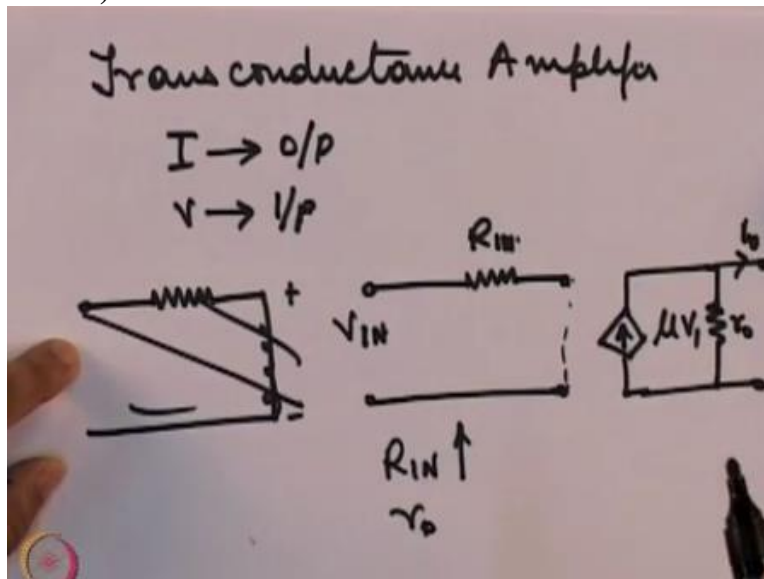


I at output that is current output and V at input and voltage input so for this trans conductance amplifier I should not I should not short this actually it should be like this I would like to correct the previous figure here it should not be shorted it should be open so this is open so it is like this

I mean open short basically this is the part where it is actually the voltage is being applied to the amplifier and for a trans conductance amplifier we will get a voltage dependent current source.

Now for a current source the output impedance is given as r_0 okay so this is V_{in} and this is the output current I_o for this case however the input conditions remain the same that is R_{in} as high as possible but this in this case r_0 should be also as high as possible the reason being we do not want any part of this current source the current produced by this current source to leak into this R_0 we want all of that current to go to I_0 hence r_0 should also be high so here we just disgrace a little bit about how the what kind of output impedances should be there for a voltage amplifier.

Voltage input voltage output amplifier and a trans conductance amplifier I leave it as an exercise for you to find out what should be the input and how high or how low the input impedances of an ideal current amplifier and that trans resistance amplifier should be so for a current amplifier the input is current output is current for a trans resistance amplifier input is current output is volt, so I leave it as an exercise for you to find out what should be the ideal values of the input and output resistances of such amplifiers.

(Refer Slide Time: 14:12)

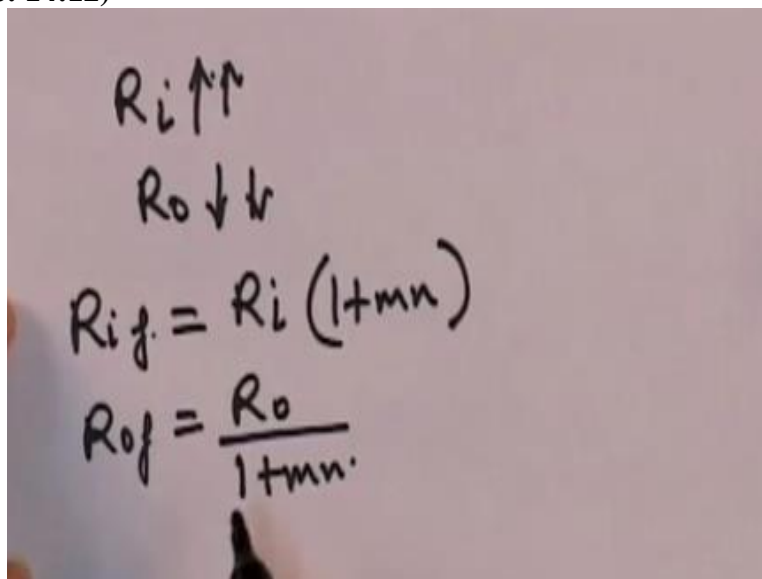

Handwritten notes on a whiteboard showing the formulas for input and output impedances with feedback:

$$R_i \uparrow \uparrow$$
$$R_o \downarrow \downarrow$$
$$R_{if} = R_i (1 + mn)$$
$$R_{of} = \frac{R_o}{1 + mn}$$

Now coming back to our to the voltage amplifier that we are studying so we should have the R_i as high as possible and R_o as low as possible it can be shown that this R_{if} with feedback the input impedance becomes like this and the output impedance with feedback becomes like this.

As you can see the input impedance with feedback is now significantly higher as compared to what was there initially and the output impedance is now significantly lower than what it was initially, so this is also one impact of feedback that we see that for voltage amplifiers where we apply voltage output tap the voltage at the output and feed it back as voltage to the input the input impedance increases the output impedance decreases or for a trans conductance amplifier.

What we will observe is that the where for a trans conductance amplifier of course we are taking current from the output and feeding it to the input as voltage in that case we will observe that the output impedance increases upon applying feedback and the input impedance also increases upon applying feedback so in this module we covered a sample analog circuit which was given a feedback of voltage-voltage feedback that is voltage from the output was fed back to the input as voltage.

What we observed is first of all the general feedback gain we got a gain expression we are with the feedback factor present and since the feedback factor was present therefore we would also get the other effects that we discussed in the previous module namely gain (A) (16:20).

Increase in linearity increase in bandwidth and in addition to that we also observed another effect that we had not discussed in the previous module that is the output impedance of this voltage-voltage of this amplifier with voltage-voltage feed the output impedance decreases and the input impedance increases, so in this module we shall end here in the next module we shall start with stability, thank you.