


Analog Circuits
Prof. Jayanta Mukherjee
Department of Electrical Engineering
Indian Institute of Technology-Bombay

Week -06
Module -04
Non Linear Applications of OPAMPS

Hello, welcome to another of this course analog circuits, so in the previous modules we have never come across what we called non linear circuits, all the circuits we have discussed so far including you know the Butterworth filters, the Chebyshev filters they are all belong to category called linear circuits because they follow the principle of linearity, even opamps as we were discussing initially they are linear circuits.

But I mean opamp is used for a simple summing amplifier for amplification in general opamps act as linear circuits, but the use of opamps is not just limited to linear circuits there are some specific non linear circuits which can also be designed using opamps using the various properties that an opamp has and these non linear circuits have a number of application as we shall see later, so let us start with some non linear applications of opamps.

(Refer Slide Time: 01:21)

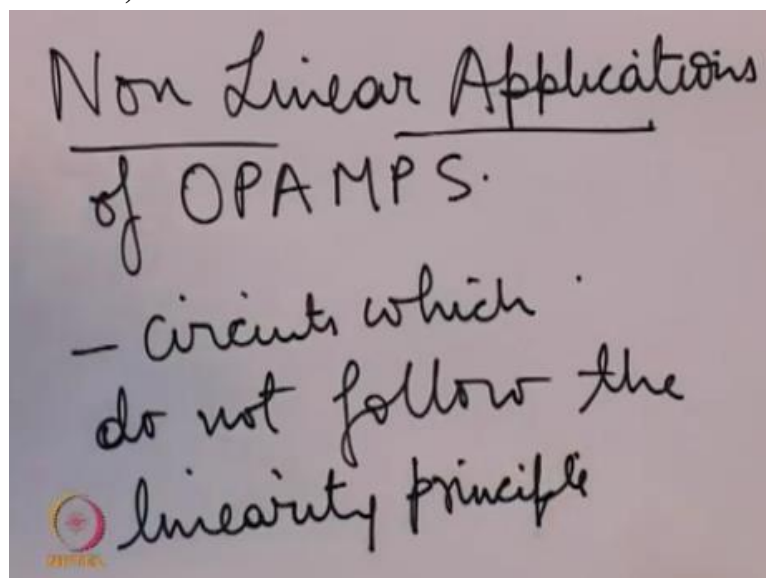

So when I say nonlinear application, it is those circuits which any circuit which does not or do not follow the linearity principle is a nonlinear circuit, so recall again what is the linearity principle first is that the output should be proportional to the input.


(Refer Slide Time: 02:10)

1. O/P proportional to I/P

2. Principle of Superposition is valid.

So these are the 2 main linearity properties which strict linear systems have output proportional to input and the second is principle of superposition is valid, so any circuit which does not follow any one of these 2 principles is a non linear circuit, now since linearity is easily defined non linearity as I said you know any circuit that does not follow the linearity principle so that implies that you know there can be lots of non linear circuits, so we shall discuss some specific ones that are useful for practical applications and one such circuit is that what is known as a limiter.

(Refer Slide Time: 03:08)

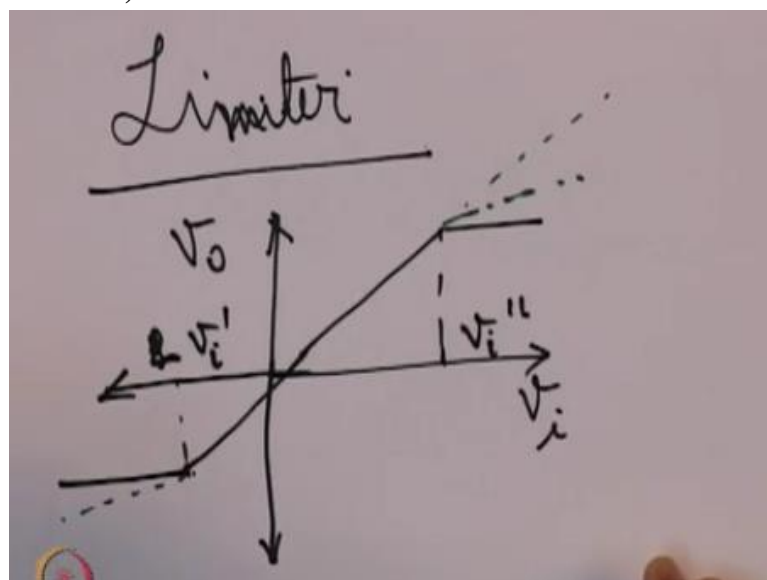


So limiter is the circuit that you know does not allow suppose this is my V_i and this is my V_o so V_i is the input voltage and V_o is say the output voltage limiter is a circuit that will not allow the output to go on increasing at a constant so ideally a limiter should be like this similarly on the negative side also if I extend my axis on the negative side also beyond a particular negative voltage V_i some value say L or say let us call it V_i dash and V_i double

dash, it will again for an ideal limiter it will not allow the output voltage to go any further down so that is an ideal limiter.

But suppose instead of such a strict cut off I have a circuit where instead of the output becoming flat after a certain input voltage say V_i double dash, say the slope also changes abruptly whereas original it was supposed to go like this but after this voltage input voltage V_i double dash the output follows a different slope and in this case also say the output follows a different slope then that circuit is also called a limiter, so how do we design a limiter? Now there are many circuits for limiter we shall discuss 2 of them so let me first draw the limiter circuit and then try to explain its properties.

(Refer Slide Time: 05:08)

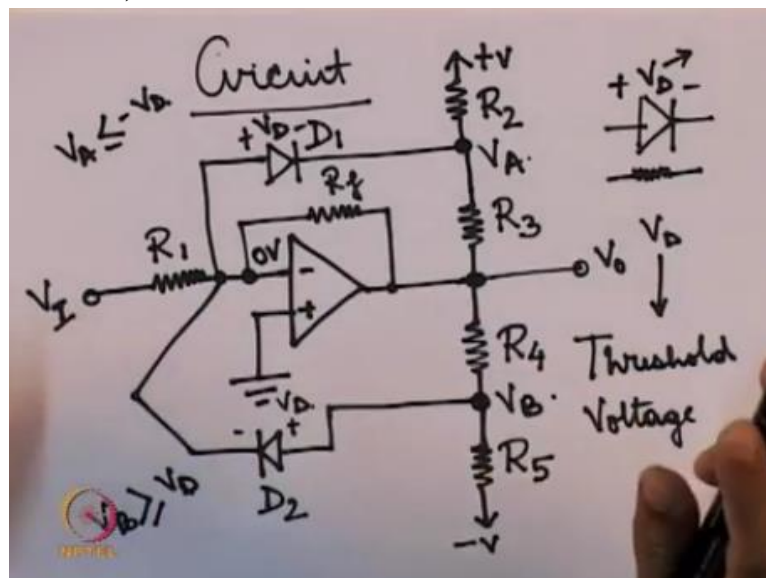

So this is the circuit why am I saying that this is a limiter first of all note that there are 2 diodes here, now we will discuss about the properties of a diode a little later but for now you can take it that a diode is a device that allows current to pass through it in only one direction, so if this is a diode then a minimum voltage called the threshold voltage so this V_D is known as threshold this has to be supplied across the terminals of the diode in order to make it conduct similarly for this diode D_2 also in order to make it conduct.

Now this triangle points to the direction in which the diode allows current through it, so in this diode current will pass only from this terminal to this terminal and also for this diode to conduct minimum voltage V_D has to be applied ok, now so as I said a diode is a device that allows current to pass in only one direction so in this case of course a diode has some

minimum internal resistance also but for that is a very small resistance and for this particular circuit we shall ignore it.

Now if this diode is conduction in one direction and if the internal resistance of the diode is very small then we can simply assume that this is a short between this terminal to this terminal, so if this diode is conducting then there is a short existing between this terminal and this terminal let us say the voltage at this terminal is called V_A and the voltage at this terminal is called V_B , now this terminal is at virtual short with the non inverting terminal hence and since the non inverting terminal is grounded therefore this terminal will also have a voltage of 0 voltage.

So if V_A is lesser or $= -V_D$ then this diode D_1 will conduct similarly if V_B is greater or $= V_D$ then this diode will conduct if V_A is lesser than $-V_D$, therefore this diode will conduct and so this resistance R_3 will then be in shunt with R_F similarly if D_2 conducts that is if V_B is greater than V_D then R_4 will be in shunt with R_F okay it can be shown that both D_1 and D_2 can never be conducting at the same time ok.

So let us see now how the voltage V_A and V_B change also remember that when D_1 or D_2 are not conducting suppose D_1 is not conducting then this there is an open between this terminal and this terminal if there is an open between this terminal and V_A so that means the total resistance appearing across this point and this point is R_F if D_1 is conducting then the total resistance between this point and this point is R_F in shunt with R_3 similarly if D_2 is conducting as I said R_4 will be in shunt with R_F but if D_2 is not conducting then simply R_F will be in shunt between this terminal and this terminal so with these in mind let us try to write some equations.


(Refer Slide Time: 12:05)

Say, initially V_A is high
 $\& V_B$ is low.
 $V_o \approx 0$.
 $D_1 \& D_2$ are both off.

$$V_o = -\frac{R_f}{R_1} V_i$$

So suppose initially V_A is high and V_B is low and say V_o is nearly = 0 okay D_1 and D_2 are both off okay then V_o will be = - R_f upon R_1 V_i okay right isn't it V_o will be simply = R_f upon R_1 that is a inverting opamp configuration V_o will be proportional to V_i okay, so then how will it look like if I draw the input output characteristics how will the input output characteristics look like if both D_1 and D_2 are off okay.

(Refer Slide Time: 13:28)

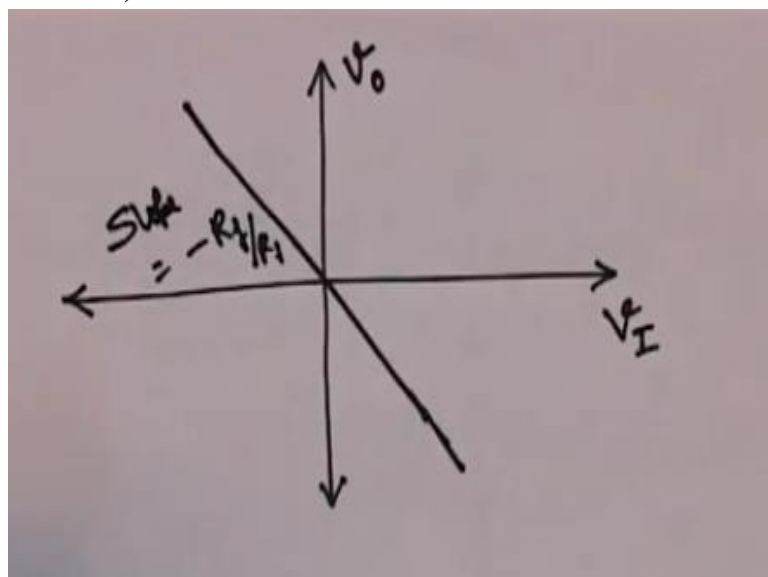

If it will be like this, now you see that as V_i becomes larger my V_o becomes smaller or rather I should say more negative till a point where V_o is so less okay that if you go back to a circuit for a minute so as V_i increases we see V_o goes on becoming more negative and as V_o goes on becoming more negative V_A also goes on becoming more negative.

So now what is the relationship between V_A and V_o , so this is a simple see D_1 is off so there are 2 voltages which are influencing the voltage at V_A one is V_o and other is the supply + V ,

so in order to get an expression for the voltage V_A we can apply the superposition principle where we first consider the effect of this $+V$ voltage after shorting V_0 and in the second case we short this terminal and consider the contribution of V_0 to V_A so if we do that the expression that we get for V_A is as follows.

(Refer Slide Time: 15:37)

$$V_A = \frac{+V R_3}{R_2 + R_3} + \frac{V_0 R_2}{R_2 + R_3}$$

$$L \cdot V_B = \frac{-V R_4}{R_4 + R_5} + \frac{V_0 R_5}{R_4 + R_5}$$

When, $V_A = -V_D \rightarrow D_1 \text{ Conducts.}$

$$-V_D = \frac{+V R_3}{R_2 + R_3} + \frac{L R_2}{R_2 + R_3}$$

V_A will be $= V R_3$ upon $R_2 + R_3 + V_0 R_2 R_2 + R_3$ so what we have here is this if let us just consider this part of the circuit only (Refer Slide Time 16:09), so see if $V + V$ voltage is shorted then the contribution of V_0 to V_A is R_2 divided by R_2 upon R_3 multiplied by V_0 and if V_0 is shorted then the contribution of $+V$ to V_A is $R_2 R_3$ I beg your pardon divided by $R_2 + R_3$ into $+V$.

So that is what we have similarly you know we can also write an expression for this part the lower V_B and the expression that we will get is the only difference between V_A and V_B is that V_B is influenced by $-V$ and V_0 whereas V_A is influenced by $+V$ and V_0 therefore proceeding similarly we can write an expression for V_B as okay now if you go back to the circuit once again.

So as V_0 increases my V_0 becomes more negative and as we can see from this expression the more negative V_0 becomes the more negative V_A also becomes and there might be a point at which you know V_A becomes so low that this diode starts conducting note that this terminal of the diode is connected to 0 volts so if V_A becomes sufficiently low that is if the voltage across the diode crosses the threshold voltage then this diode starts conducting.

(Refer Slide Time 18:20) Now what is that voltage suppose so we can say that when V_A is = $-V_D$ the threshold voltage D_1 conducts so then from this expression we can write from this expression just one arrow $-V_D$ is = $+V R_3$ upon $R_2 + R_3$ and let us suppose the value of the output voltage when V_A is = V_D is = is what I call L^- $L^- + L^- R_2$ upon $R_2 + R_3$.

So, if we go back to the graph once again so what is happening is that at this particular extend this is a certain value of output voltage which I am calling L^- at this output voltage diode starts conducting similarly when V_i is becomes more negative there will be another output voltage value which I am calling L^+ where diode D_2 starts conducting so for D_2 diode D_2 what should be the condition let us once again go back to our circuit

When V_i goes on decreasing the V_o goes on increasing and as V_o goes on increasing V_b also goes on increasing and that is also verified from this equation isn't it this is not there as we can see as V_o goes on increasing my V_B will also goes on increasing and there will be a certain value of V_B when the voltage across D_2 crosses the threshold voltage and D_2 starts conducting.

When that voltage is achieved this diode will start conducting and that output voltage for which V_B crosses the threshold voltage and I am calling that as L^+ and that is what I have marked in this graph L^+ so what is the value of this L^+ how will we determine we will determine it from this equation okay so let us plug in the value of V_B in this equation.

(Refer Slide Time: 21:33)

When $V_B = V_D$, Diode D_2 starts conducting.

$$V_D = \frac{-V R_4}{R_4 + R_5} + \frac{L^+ R_5}{R_4 + R_5}$$


$$L^- = -\frac{V R_3}{R_2} - V_D \left(\frac{1 + R_3}{R_2} \right)$$

$$L^+ = +V \frac{R_4}{R_5} + V_D \left(\frac{1 + R_4}{R_5} \right)$$

When V_B is = V_D diode D_2 starts conducting so then V_D is = - V upon R_F upon V_{R4} divided by $R_4 + R_5$ + if I call that value of V_0 as L^+ R_5 upon $R_4 + R_5$ so we have these 2 expressions for finding out L^+ and L^- and the value of L^+ and L^- that we obtained are as follows.


So L^- is given as - V_{R3} upon R_2 - V_D 1 + R_3 upon R_2 and L^+ is given as + V_{R4} upon R_5 + V_D 1 + R_4 upon R_5 , so once this happens you know that we reach these when V_A reaches L^- or I should say the V_0 reaches L^- or V_0 reaches L^+ diodes D_1 and D_2 start conducting and if they start conducting then what happens as I had mentioned at the beginning when Diode D_1 conducts in the net resistance appearing across the feedback loop is R_5 R_F in shunt with R_3 ok.

(Refer Slide Time 23:52)

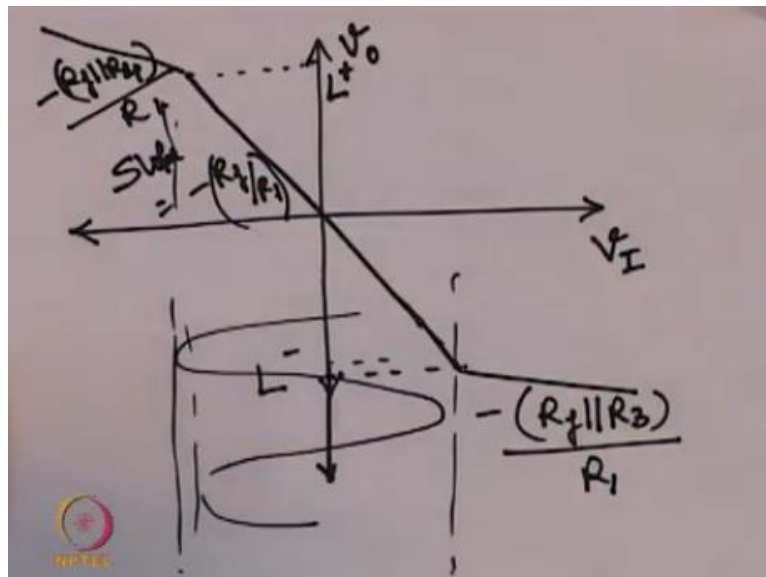

So then what we get here is that beyond L^- the slope will change so here the slope was - R_F upon R_1 here the slope will be - R_F in shunt with R_3 upon R_1 okay and here the slope will be - R_F in shunt with R_4 upon R_1 now see that this L^- and L^+ can be at just as independent the reason why the limiting action is happening suppose you are giving a sinusoidal input to the V_i okay so beyond this point the output will be clipped any input voltage which exceeds this value will be clipped or will be amplified with a different gain factor that is why the limiting action happens.

(Refer Slide Time: 25:15)

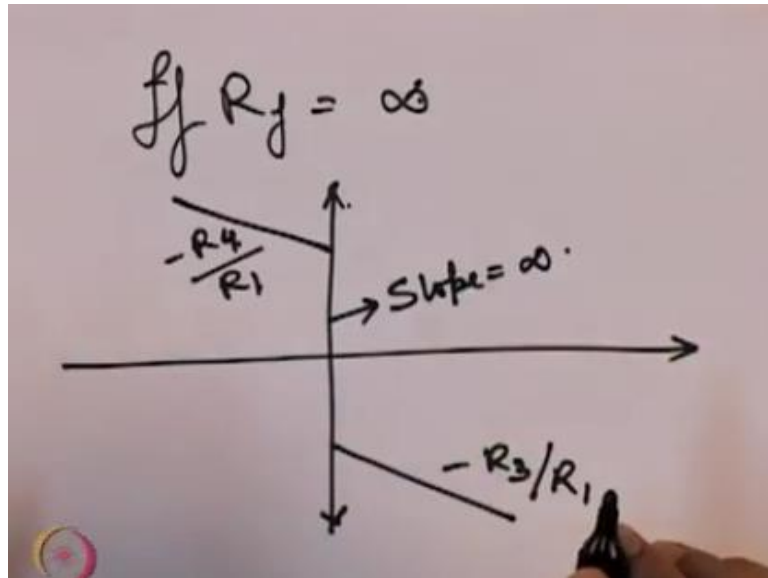

Now if you make R_f is = infinity, if R_f is = infinity then the characteristics becomes something like this the slope is - R_3 upon R_1 and here the slope is - R_4 upon R_1 here the slope is infinity, in this lecture we studied one of the 2 types of limiters that I had mentioned. In the next module will be continuing our discussion on limiters and also studying the in somewhat detail the properties of a diode, thank you.