

Analog Circuits
Prof. Jayanta Mukherjee
Department of Electrical Engineering
Indian Institute of Technology - Bombay


Week - 08
Module - 02
Rectifiers

Hello, welcome to another module of this course analog circuits, so we have been talking about various nonlinear circuits over the past few weeks and in this module we are going to introduce you to another nonlinear circuit which is very popular and this circuit is known as the rectifier. So a rectifier is a circuit that putting its simply converts an AC voltage to a DC voltage.

So basically what we do in rectifier design is that we allow the voltage to conduct or to pass through in one half cycle and let it just not pass through in the other half cycle, so this is the simplest construction where only the voltage is allowed to pass through in the first half cycle and the other half cycle we do not allow the voltage to pass, so that is the principle of a half wave rectifier.


In this module, we are going to study about other circuits which allow voltage to pass through in both half cycles but in the other half cycle they invert the half cycle thereby making the sense of the voltage at the output the same for both half cycles, so let us see those circuits.

(Refer Slide Time: 01:48)

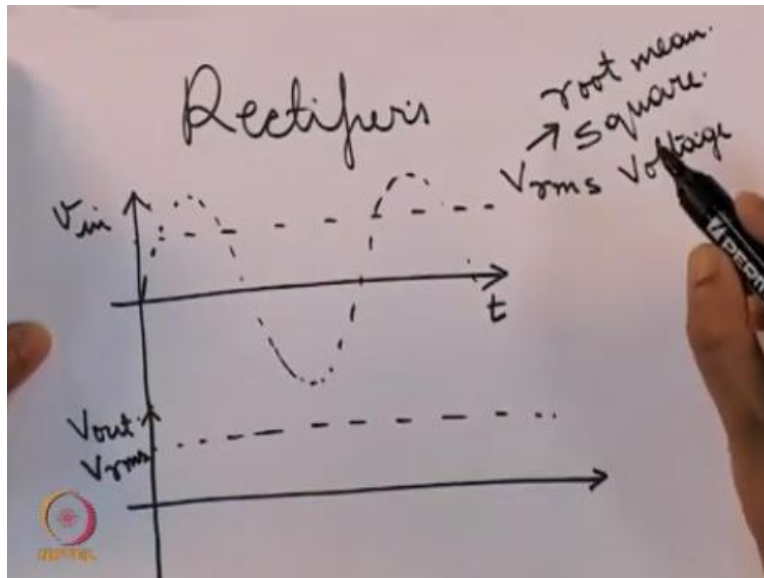


So ideally you know ideally if suppose you have an AC signal like this, you should get an output and let us say this is the RMS voltage then you should get an output which is like this, so V_{rms} is the root mean square voltage and after rectification the output should ideally be = V_{rms} but that is never possible that is never possible because there is no ideal rectifier which can do such a conversion but we can approximate it or go nearby, for example this negative half cycle of the input sinusoidal voltage if we can flip it over so if you flip it over then we would get something like this.

(Refer Slide Time: 03:40)

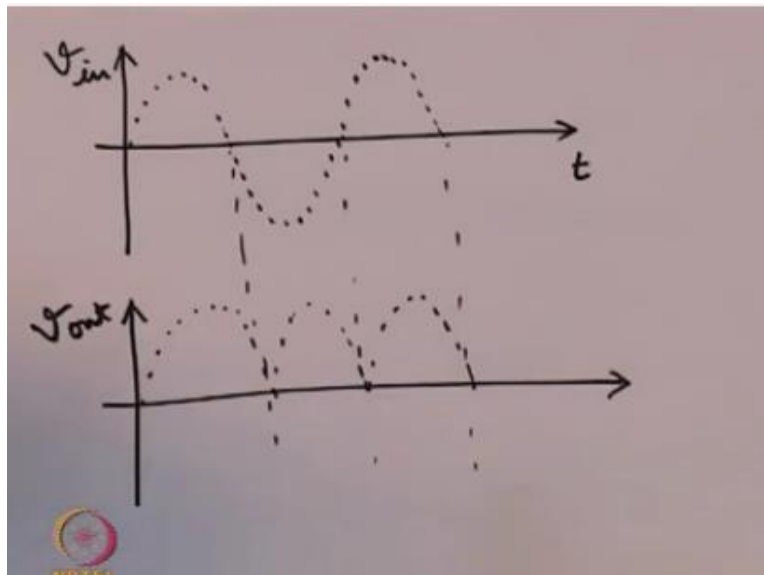


So after flipping over, we get something like this you see the negative half cycle here now has gone become here so this is my V_{out} , so this is also form of rectification because now all the voltages at the output have only they have no negative component we have only positive components and so through now = the ideal they do approximate DC of course a DC voltage which kind of varies slightly with time, so this is the principle on which we are going to design our rectifier circuit, so the first type of rectifier is known as what we call the half wave rectifier.

(Refer Slide Time: 05:26)

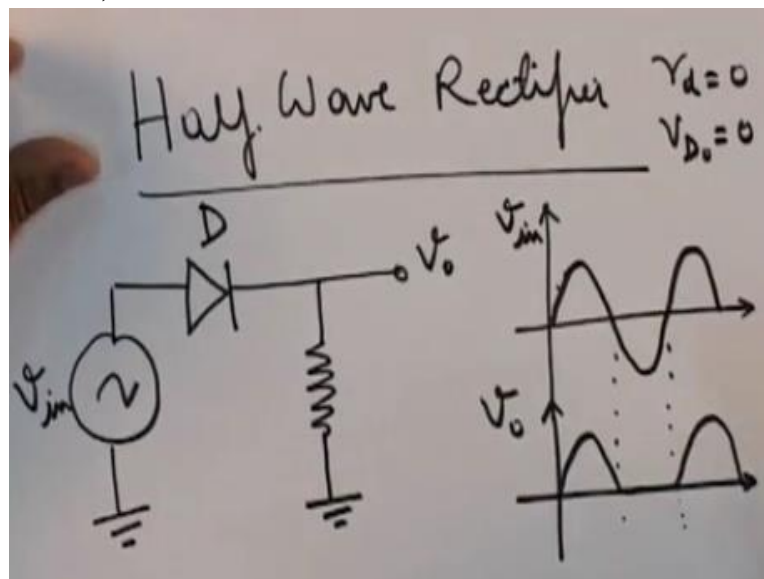

As the name suggests this rectifier only allows half the sinusoidal voltage only a half cycle of the sinusoidal voltage to pass through it okay it does not allow the other half cycle to pass through it, so the circuit for this is now usually if we consider an ideal diode then of course our rectification will be like this, so for an ideal diode the resistance R_d is = 0 and the threshold voltage is also = 0 so for such a diode this is what will happen if this is my input this is what my output will be but in real diodes where we have a finite value of our R_d and V_{D_0} the characteristics of such a diode will be of this form the V_i characteristics that is.


(Refer Slide Time: 07:37)

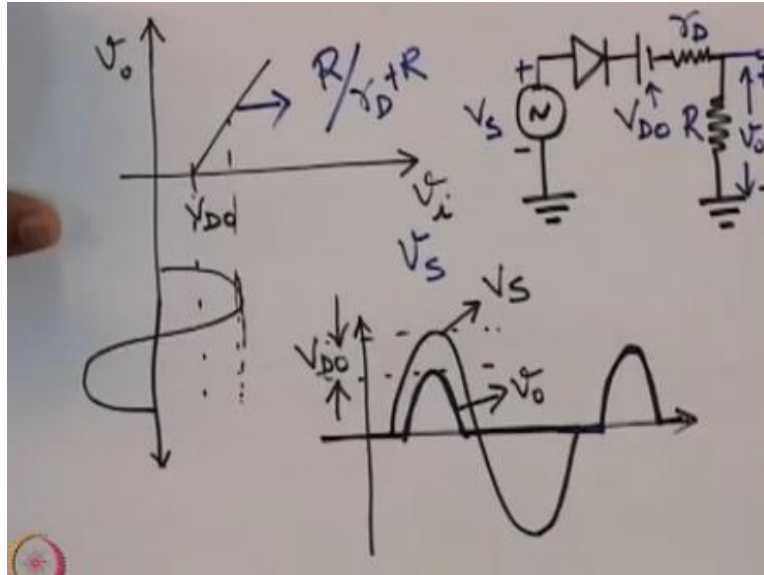

So the circuit corresponding circuit is like this, this is V_s the slope of this line is given by R upon $R_d + R$ so with this kind of you know here is my V_{D0} okay and suppose my input if I draw it on this way along the Y-axis then you should touch here so then the output that I will get will be something of this sort this is V_s and this what the supply voltage is and this inner curve this is my actual output. So this V_0 and the spacing between the peaks of V_s and V_0 is V_{D0} and of course after this we will again get a 0 voltage and then finally after some time we will get again the reputation of this curve, so this is how it will repeat again this curve.

So, my output if I use a blue marker, output will follow like this to go here follow this come down like this follow up and like this so this blue curve this gives my actual output voltage when I consider the presence of this threshold voltage V_{D0} and also a finite resistance diode resistance R_d in order for us to rectify the circuit even during the negative half cycle of the input we need to modify the circuit and the circuitry obtained is known as a full wave rectifier.


(Refer Slide Time: 12:14)

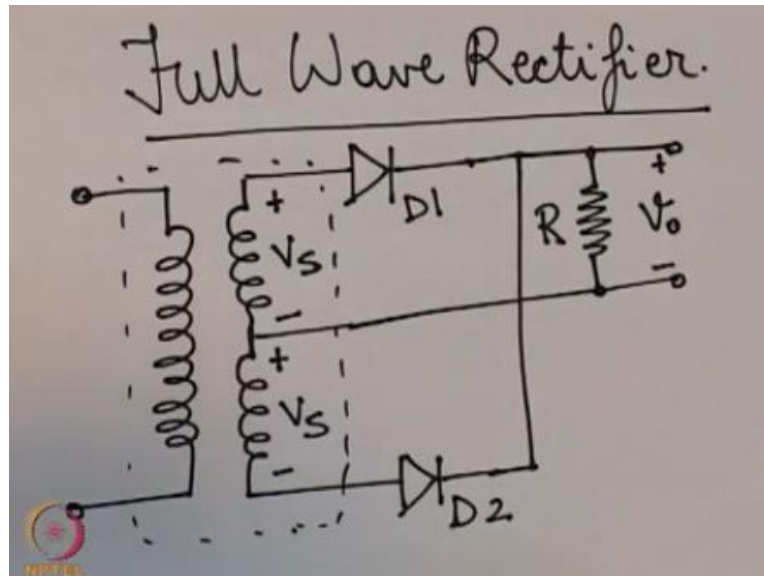

The circuit for that is given like this, so here this part which was not sure not present in the circuit for the half wave rectifier this is actually a transformer this whole thing now the transformer does not really play any role in the rectification, but it is necessary to show it show this element just to just to let you know that there are actually 2 sources $+ - V_s$ and $+ - V_s$.

So, the transformer takes in an output and after up conversion it produces 2 different in out outputs which are our actual source inputs V_s and V_s okay, so each of these small windings in the transformer will produce $+ V_s + V_s$ voltage output line shown like this now how does this circuit operate say we are in the positive.

(Refer Slide Time: 14:53)

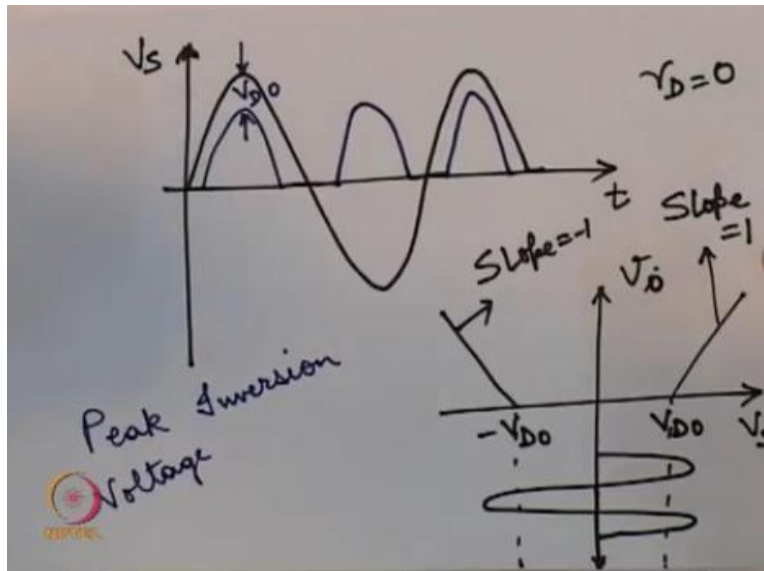

Let me draw the circuit say V_s is positive so then, so this is T this is V_s , so when this is say this voltage is positive V_s is positive then or in the pause or we are in the positive half cycle of V_s this diode D1 will be forward biased and when V_s is above the threshold voltage of D1 this will start conducting when V_s is in the positive half cycle however diode D2 will be reverse biased and will not conduct.

So the voltage V_s will therefore appear across the resistance R_0 that is it will appear across the output voltage V_0 during the positive half cycle in the negative half cycle D2 will be forward biased D1 is reverse biased therefore the negative half cycle also we will have V_s appearing across the voltage V_0 , so now ideally if our diodes were ideal then we would have simply out output would simply reflect the input but since our diodes are not ideal and if we consider both the negative and half and positive half cycle of the input voltage then the output characteristics of this diode will be something like this.

So this is this is V_o and this V_s here so it will be something like this the slope = 1 here the slope = -1 this is $-V_{D0}$ and this is $+V_{D0}$ where V_{D0} is the threshold voltage and suppose we have input sinusoidal voltage like this okay so this my V_s this curve I have shown it here like a exaggerated version of this one now here the slope is 1 because we assuming that the internal resistance of the diode is = 0.

So if this is my V_s which is which I have drawn along the Y-axis which is in this graph is shown along the X-axis then the output that I will get is something like this let me use the blue so my overall output will be as shown by the blue marker just like you know just like the previous case we will have a diode drop V_{D0} between the supply and the actual output fine now an important parameter in determining the success of any circuit of any rectifier circuit is known as the peak inversion voltage.


I am calling it is necessary it is important success of any circuit of any inverter circuit because peak inversion voltage is a gives us an idea about what is the maximum voltage that a diode is subjected to when it is present in a rectifier circuit, so in this case if we go back to our circuit for a moment the full invert full wave rectifier any of these diodes will experience the maximum voltage across their terminals when they are in reverse bias mode in the forward bias mode.

It is conducting the diodes are conducting therefore the voltage drop across the diode will be same as the threshold voltage but it is in the reverse bias mode when the diodes phase the maximum voltage across the terminals now suppose D1 is conducting that is V_s is positive and D2 is negative is in the reverse bias mode, so what is the maximum voltage that D2 will be subjected to.

So here we have $-V_{D0}$ right and here we have $2V_s$ right, so the maximum reverse bias voltage across D2 I can write this peak inversion voltage as $2V_s - V_{D0}$ what about the case for a half wave rectifier if we can go back to the circuit for a half wave rectifier for a moment what was the maximum voltage that this diode D that it could experience in the reverse bias mode, so peak inversion voltage for this diode will be $= V_s$ which is the supply voltage, since we do not have any diodes conducting in the reverse biased mode.


So the peak inverse voltage is $= V_s$ now this is a problem of this kind of full wave rectifier circuit if our V_s is very large then there is a risk that the diodes can break down and therefore to avoid that we always try to reduce the peak inversion voltage so one circuit where we are able to do such a where we are able to do a full wave rectification yet reduce the peak inversion voltage is what is known as a bridge rectifier, so a bridge rectifier has a circuit as follows.

(Refer Slide Time: 22:37)

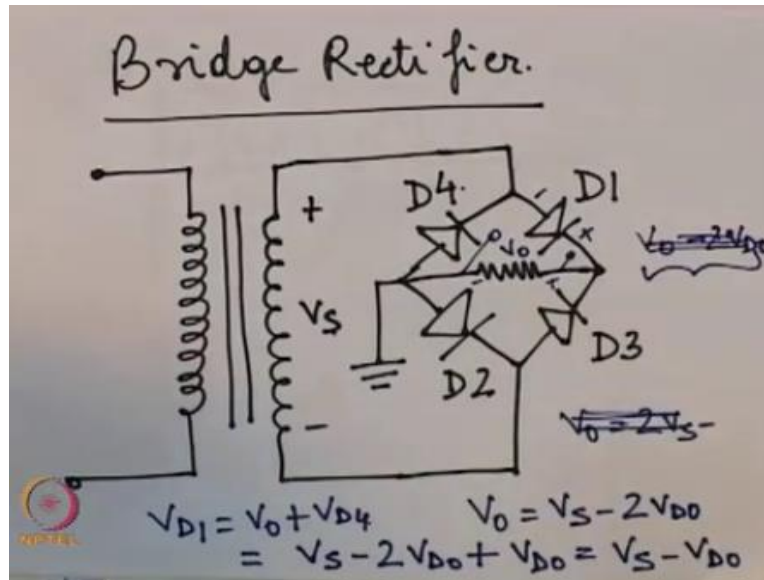

So again, we have a transformer which supplies a voltage of + and - V_s and then we have a bridge circuit, so the bridge circuit consists of 4 diodes connected as shown ok and the principal operation is similar to that of the full wave rectifier see during the positive half cycle this say when V_s is positive then D1 and D2 will be forward biased and during the negative half cycle D3 and D4 will be forward biased, so overall the output input and output relationship will be something like this.

(Refer Slide Time: 24:54)

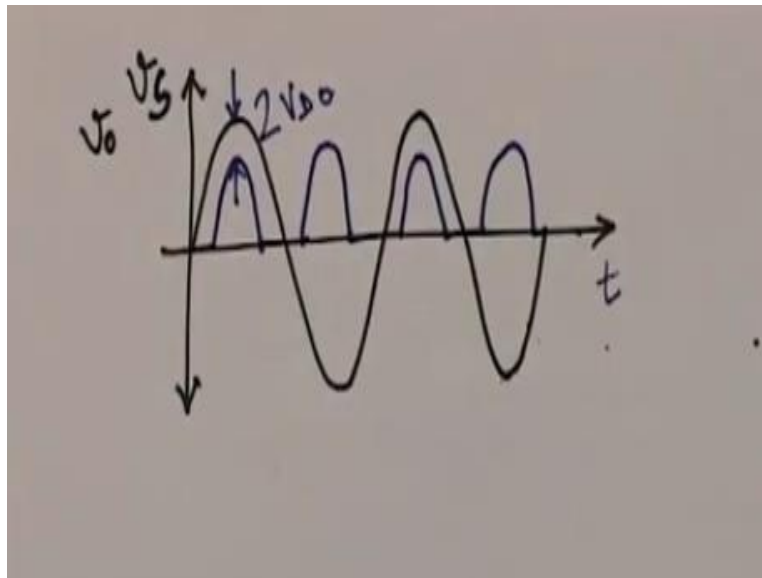

So the shape of the curve is similar to that of the full wave rectifier but the difference between the 2 peaks of the input and output is now $= 2V_{D0}$ because of the 2 diode drops that we have to

that the input, so this is my input my output by the way is taken between these 2 ports ok it is taken across the bridge so every time we take the output we have to undergo 2 diode drops and that is why the difference between the peak of the input and the peak of the output is $2V_{D0}$, however what about the peak inversion voltage.

Now let us consider the case when diode D3 and D4 are conducting ok then what is the voltage across this diode set so the voltage across this diode D1 can be consider to be $= V_0 - 2V_{D0}$ so this is sorry I just want to correct it so we have $V_0 = 2V_s$ - we have $V_0 = V_s - 2V_{D0}$ just note this correction and that the voltage the reverse bias voltage across this diode D1 is $= V_0$ okay suppose we are taking, so this is my positive this is my negative this voltage + the voltage across this transistor D4 okay so I have $V_{D1} = V_0 + V_{D4}$ the voltage across D4 is = the diode drop isn't it V_{D0} so this will be $= V_s - 2V_{D0} + V_{D0}$ which is $= V_s - V_{D0}$.

So what we see here is that for the bridge rectifier the peak inversion voltage is $= V_s - V_{D0}$ which is much less compared to the peak inversion voltage for a full wave rectifier which was $= 2V_s - V_{D0}$, so that is one big advantage of the reverse of this bridge rectifier in that the diodes do not break down easily, the disadvantage of course for this bridge rectifier is that the difference between the peaks of the input and the output is now to V_{D0} as compared to V_{D0} for the full wave rectifier.

So in this module we covered some topics on rectifier design there are some variation of this rectifier designs as well something known as a peak rectifier and then we are and of course there is the problem of threshold voltage as we are seeing in all kinds of rectifiers the output never matches the input there is always the diode drop present between the output and the input, so to get rid of this problem we have some special circuits known as super diodes where this threshold voltage problem is removed so that is also something we will be covering in the next module, thank you.