

INDIAN INSTITUTE OF TECHNOLOGY KANPUR

NPTEL

**NPTEL PROGRAMME ON
TECHNOLOGY ENHANCED LEARNING**

**Course Title
Electromagnetic Waves in Guided and Wireless**


**Lecture - 08
Additional Applications of Smith Chart**

**By
Dr. K Pradeep Kumar
Department Of Electrical Engineering
IIT Kanpur**

Hello and welcome to NPTEL MOOC on Electromagnetic Guided Waves, the Electromagnetic Waves in Guided and Wireless Media, this is our module 8, so in this module we are going to look at additional applications of Smith Chart, I'll mostly be giving you again a high level version of this mid charting, so you will have to have your mid charts, pencil, compass, scale and other things to verify my calculations, and doing so couple of problems will give you a good handle on how to use Smith charts, okay.


So we will look at two applications of Smith chart, one we have already seen the application but we did not mention it until the end of the problem. Shunt stub matching, we are familiar with the basic idea you have this main transmission line which is terminated with some unknown load Z_L , and this transmission line has to be matched to the characteristic impedance of the main transmission line, we are going to assume that the lines are lossless to simplify our calculations,

(Refer Slide Time: 01:17)

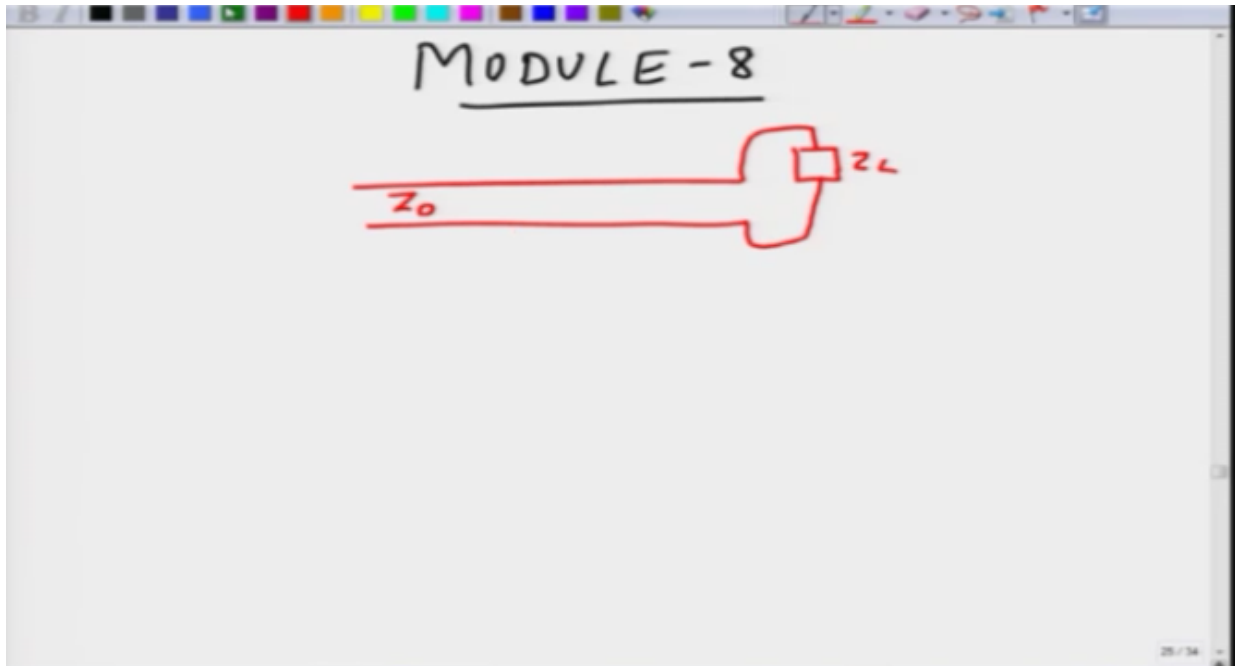

and the procedure also you know, you need to connect a stub of appropriate termination whether it would be an open circuit termination or it could be a short circuited termination, both will actually work but then depending on which termination you have chosen the length of that stub will change, so we will denote the length by D_2 and the position at which you are going to place this stub as D_1 , okay.

(Refer Slide Time: 01:42)

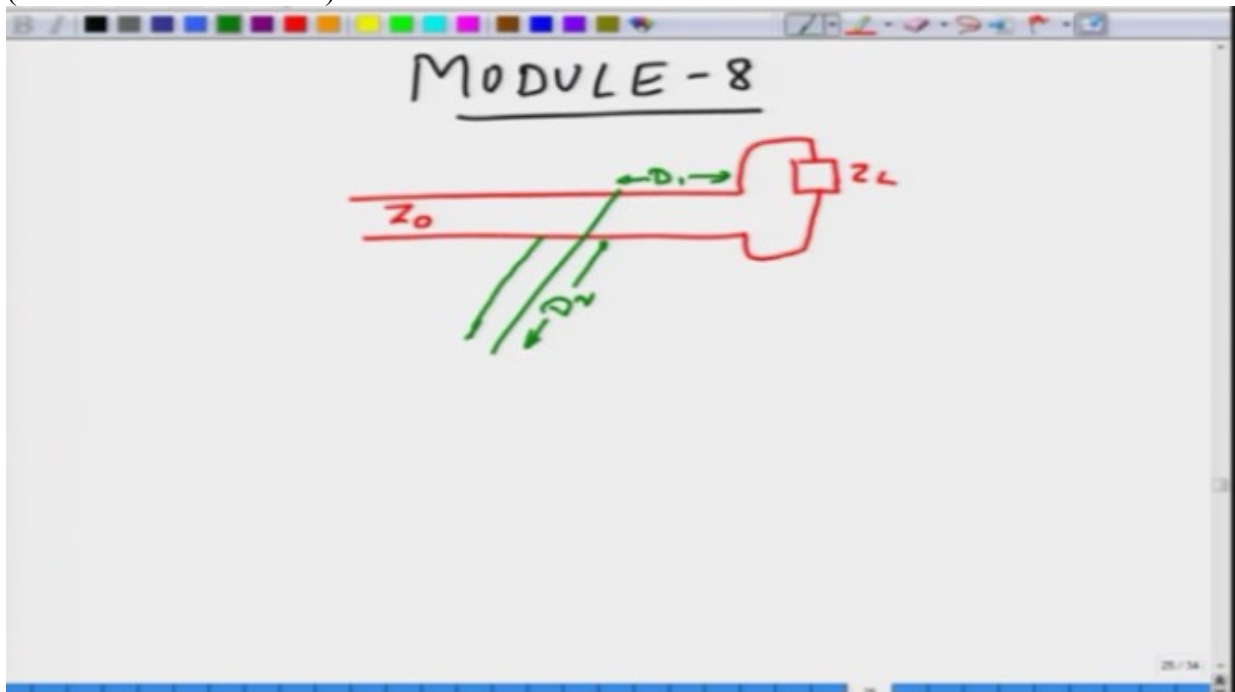


In the previous problem you were given D_1 , given D_2 , you are given Z_0 and Z_L and you are asked to find out what is the input impedance at this particular plane or rather we found that it is easier to deal with admittances and therefore we were asked to find out what is the

normalized input admittance at this plane and we found that this was actually equal to 1, okay, and it was equal to 1 because two things happened, one we start off with Z_L and then you convert it first Z_L to \bar{Z}_L , from \bar{Z}_L you convert it that into \bar{Y}_L , right, so that was actually the admittance that you would see right at the load point itself.


And then by moving \bar{Y}_L bar you know from starting from the point \bar{Y}_L bar and moving on to the WTG scale that is clockwise from the WTG scale, what you did was to find the intersection or rather it turned out that way that now you are going to do this one, so what you found was the new point which we called as say \bar{Y}_L bar was actually equal to $1 + \text{some } jB$, where B was the reactance that you form, B could be positive or negative doesn't matter, I'm just writing it as $1 + jB$, it could equally be $1 +$ or $1 - jB$ you know when B is negative.

(Refer Slide Time: 03:00)

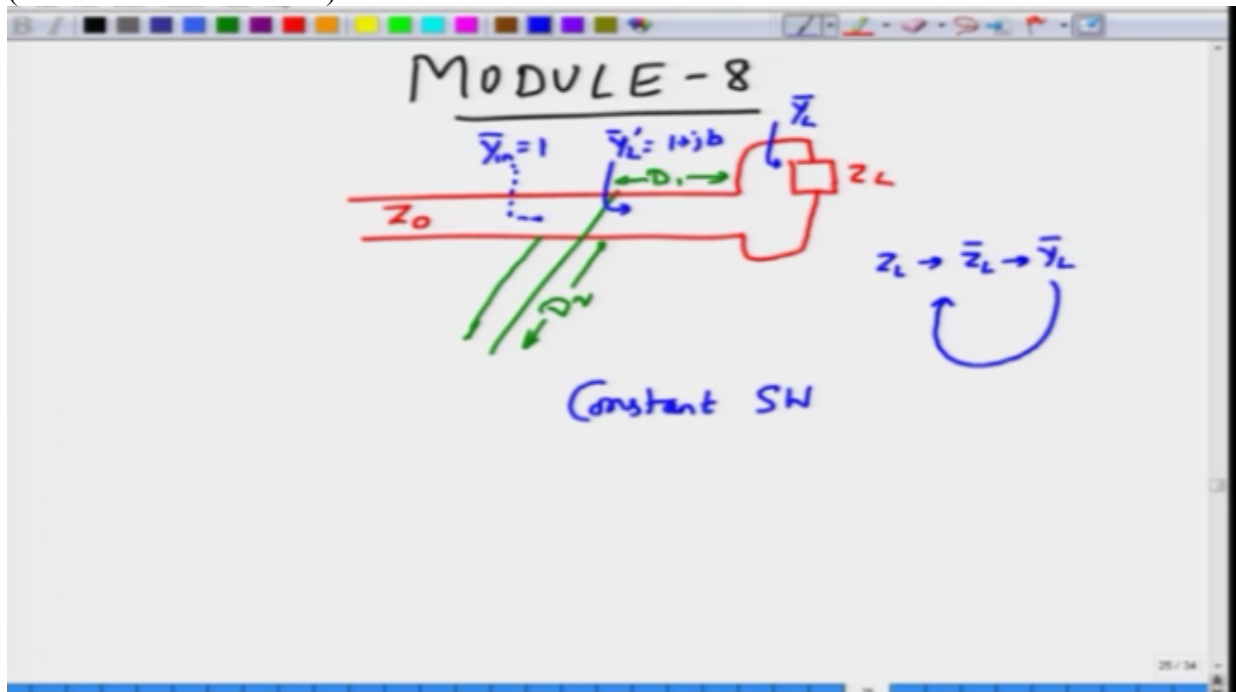


So what you found was starting from \bar{Y}_L right to $\mu \bar{Y}_L$ bar, \bar{Y}_L bar was actually the position where the constant SWR corresponding to Z_L intersected with unity or unit circle on the Smith chart, unit circle on the Smith chart was given by $R = 1$ this is a special circle and the point where the constant SWR circle and the $R = 1$ circle, this is $R = 1$ circle sorry this is $R = 1$ circle, this is constant SWR circle somewhere, okay, and when these two intersected you obtained the impedance or the admittance \bar{Y}_L bar as some form $1 + jB$.

(Refer Slide Time: 03:44)

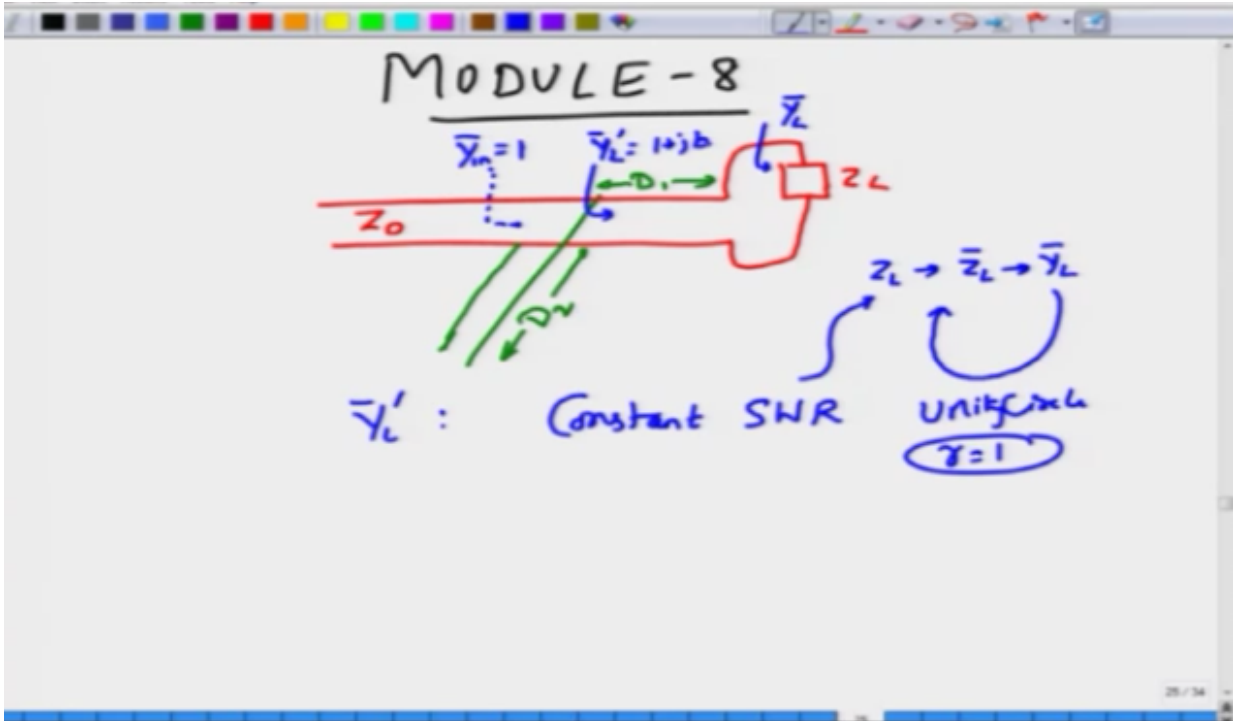


And what this stub actually did was to cancel off this B that is the reactive part by starting with either a open circuit or a short circuit in such a way that this \bar{Y}_S prime which was the stub admittance was exactly equal to $-jB$, okay, so if for example \bar{Y}_L prime was $1 + j2$ then the stub B supposed to give you $-j2$ if the \bar{Y}_L bar admittance is $1 - j2$, then the stub is going to give you $+j2$, right,
 (Refer Slide Time: 04:17)

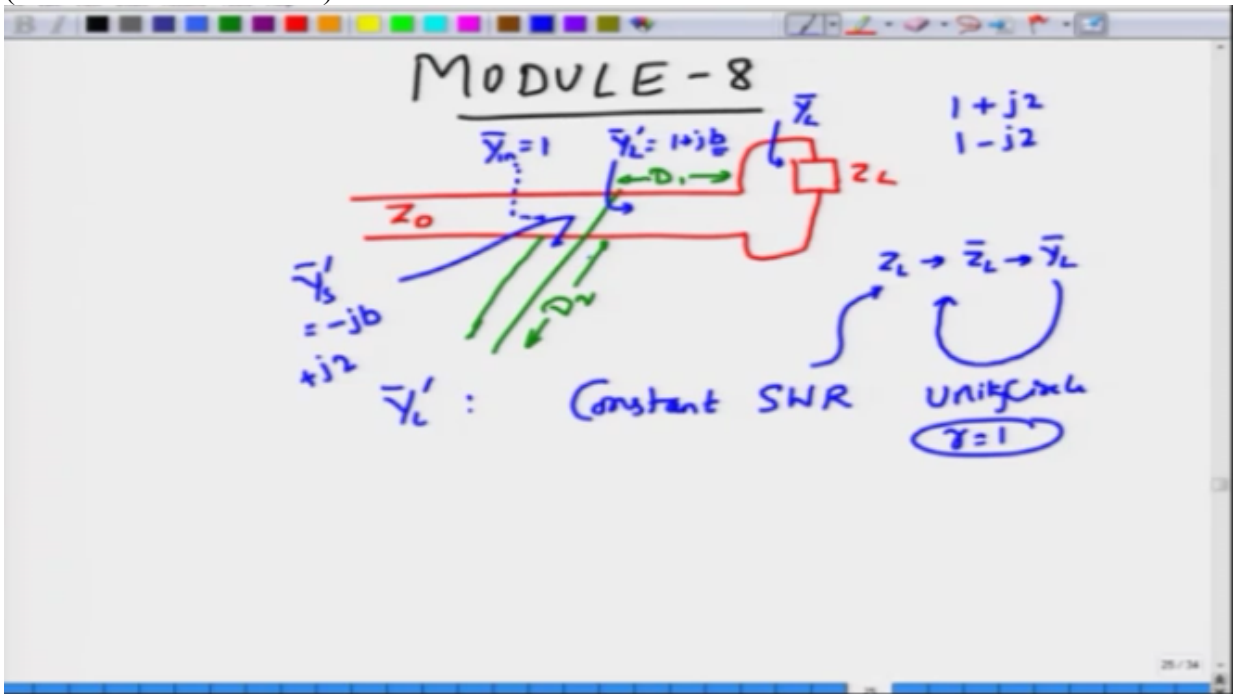

so this is the basic idea and the distance D_2 in order to give you that admittance can be found again by Smith chart, okay, so hopefully this process is very clear, we are going to solve a simple problem, right, and then we will see how to obtain this D_1 and D_2 , okay.


Let's assume that someone has already calculated what is the normalized load impedance which is Z_L bar, and this is given by $1 + j2$, okay, if we are already given what is $1 + j2$, then we really need not do anything else, you simply have to design D_2 , okay, of course here the problem is that you need to place the stub right at the load itself, okay, this problem of placing that load right at the load itself does not in any way make it impractical, because these are connections done in the parallel manner, if it was series, yes then you have to make some space for this you know line to be placed in series and that would have created a little bit of a problem, but because you are going to connect in parallel you can simply connect right at the source itself that is make $D_1 = 0$ and simply choose the length D_2 appropriately to convert either an open circuit at line we will take that in this problem into $-j2$, so all that you are trying to do is to obtain the length of the line such that you get $-j2$.

(Refer Slide Time: 05:39)

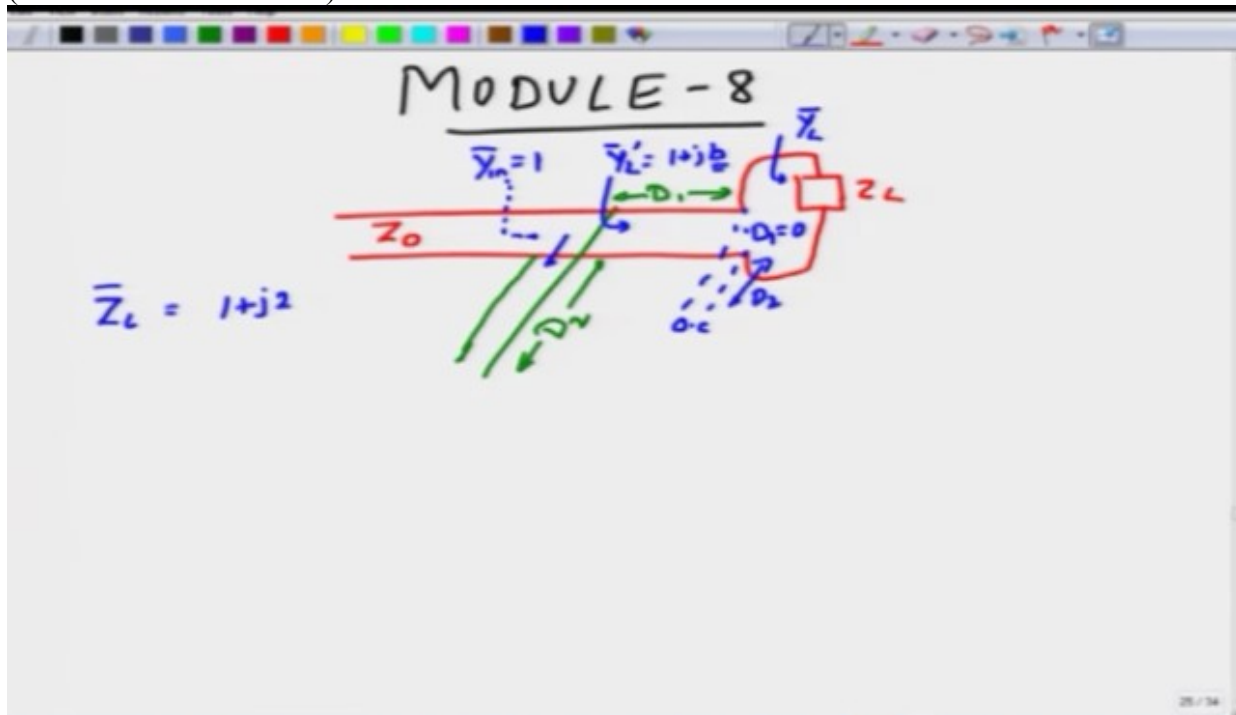


And how do you do that? Well we know that you are going to be moving on the outer circle because an open circuited impedance will be located here but then after transformically to the admittance you are going to start at these point which we called as B, this was point A,

(Refer Slide Time: 05:57)

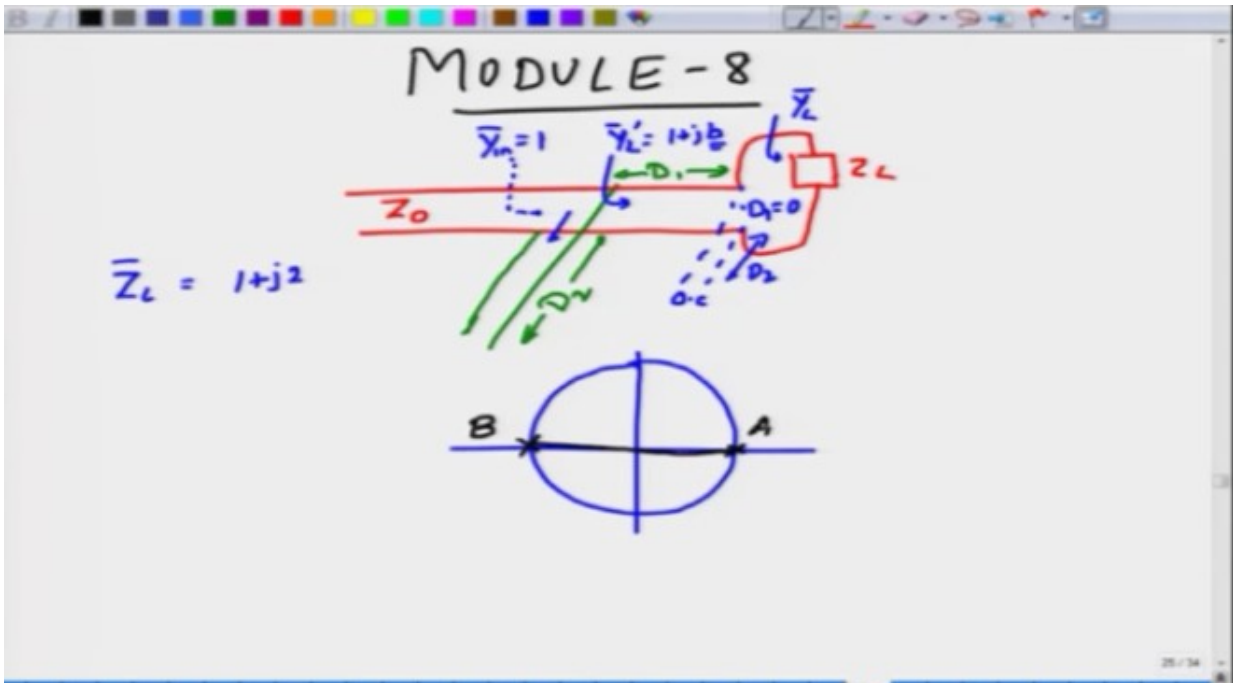

right, A corresponding to the open circuit, impedance B corresponding to the open circuit admittance, okay, so the open circuit admittance is located at B, and then this outer circle you are going to move clockwise, okay over a length D_2 , right such that you get or you land up at $-j2$, right.

(Refer Slide Time: 06:17)

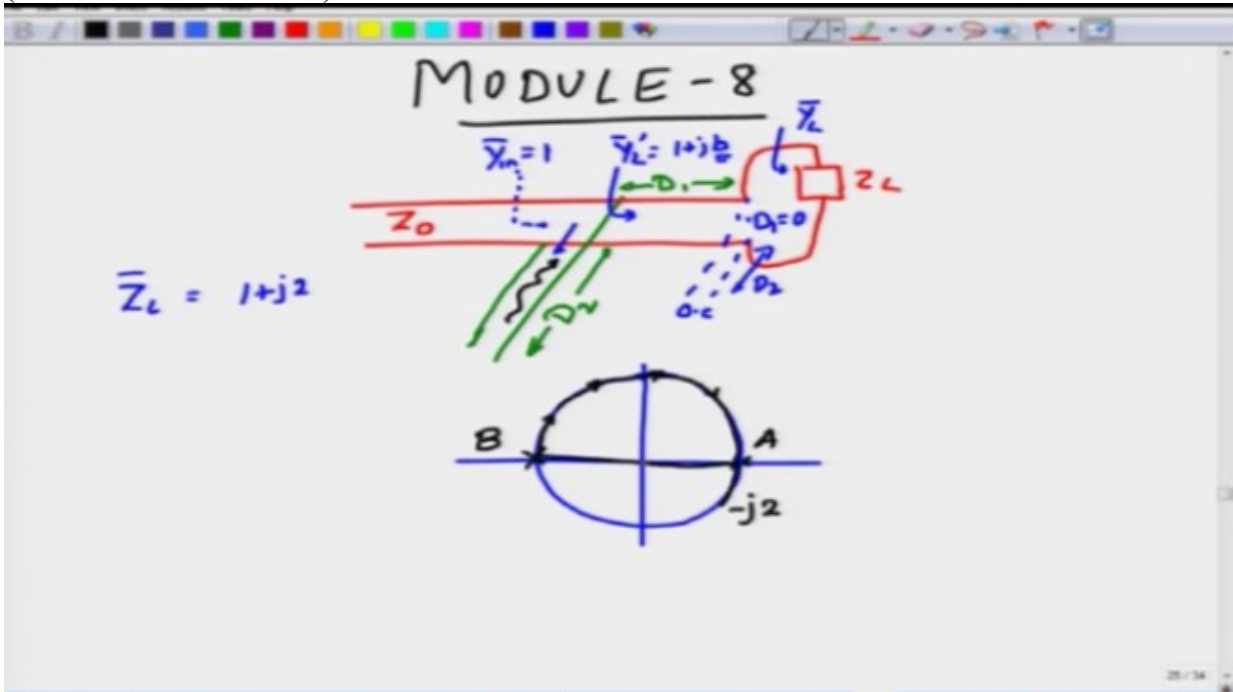


And then you find out how much you have moved, you probably have moved all the way 0.25 anyway to land up to a negative value of J, and then you would have moved some additional distance, okay, so you have moved this distance and what you get is whatever the value, so this

is about you can find this, so whatever the length that you have found, so $0.25 +$ I think this is about 0.11 , so there is a total distance of 0.36 lambda that you have moved, please verify the calculation I may be wrong in one of these numbers, but I do know that B to A distance is 0.25 and then you have to move an additional distance to reach this point which is C which gives you $\bar{Y}_S = -j2$, okay.


Now if this problem seem very simple to you, let's alter the problem here by making the real part to be different than Z_0 , so let us say take the real part to be say 0.5 and then I'll still keep this as $+j2$ the load, normalized load impedance there, so that I can find out what would be the distance D_1 and D_2 .

(Refer Slide Time: 07:21)

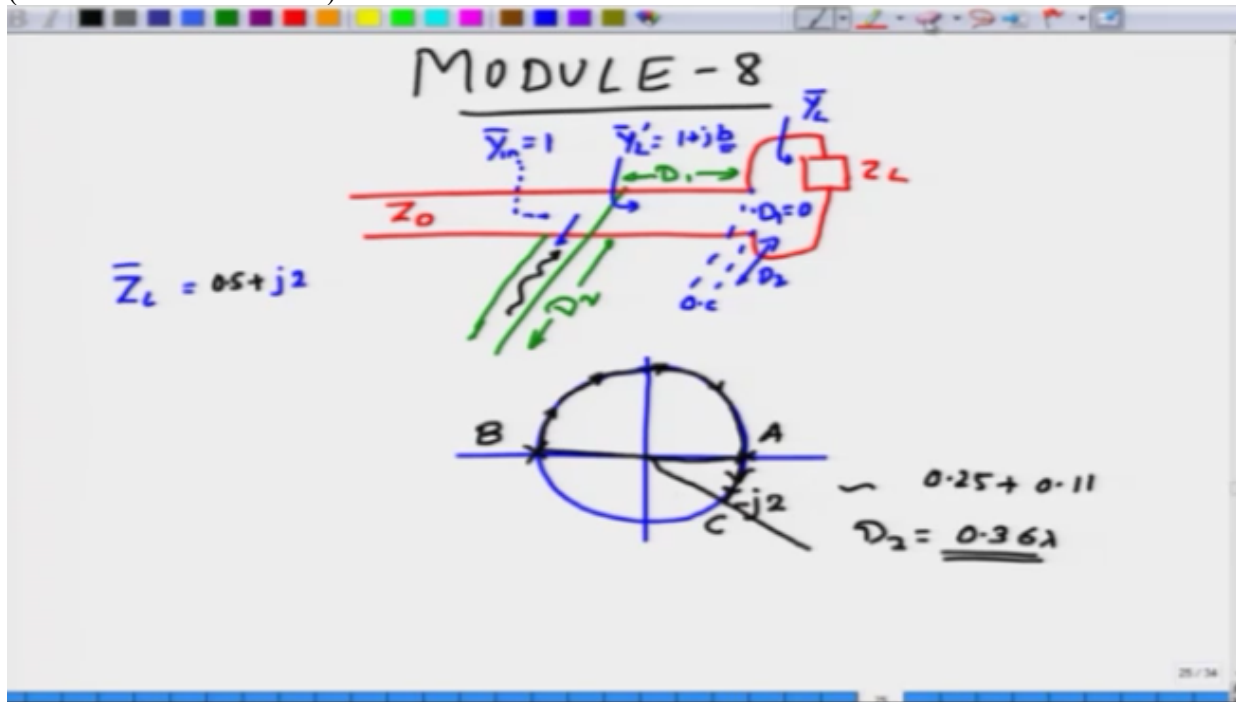


Now of course I can't place it right on the load point itself that is clearly not possible because the real part is not equal to 1 , so I have to keep the stub at a distance D_1 in such a way that after transforming the real part 0.5 would become 1 , and then you have whatever the left over for the susceptance that you need to cancel, okay, so we'll do that again by going back to the Smith chart, but this time our objective is to determine both D_1 as well as D_2 , again this is my skeleton of the Smith chart, this is my unit circle,

(Refer Slide Time: 07:58)

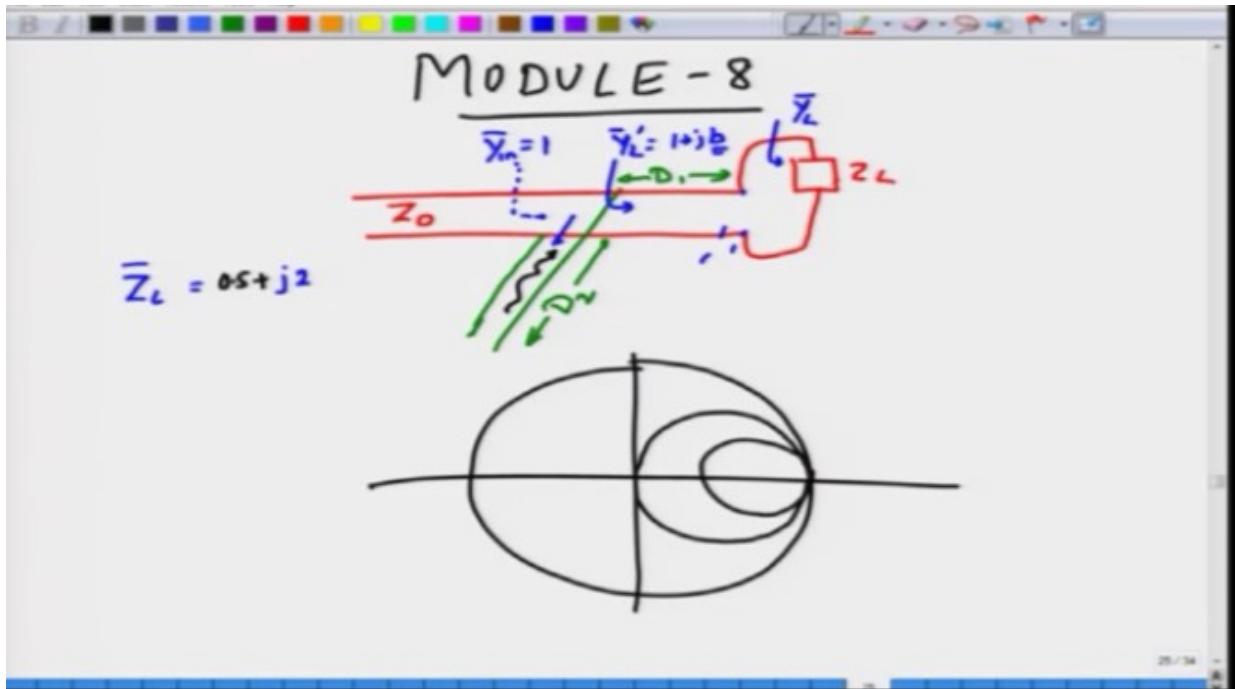


okay, and then I have this other thing, then I have this 0.5 circle, okay.

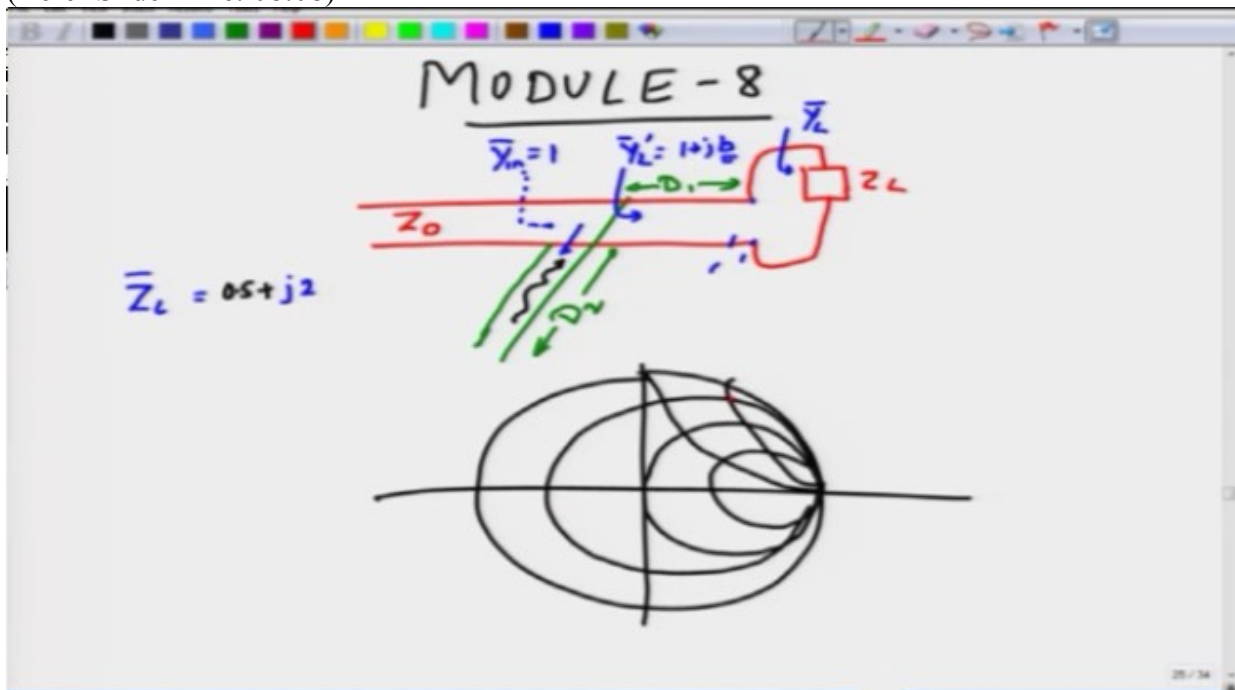And then I need J2 so let me draw one additional arc, so this 0.5 + J2 ZL
(Refer Slide Time: 08:08)




bar will be located somewhere over here, we will call this as A, but then I'm not really working with impedances I need to work with admittance, so I will first draw the constant SWR circle, okay, so this green line is my constant SWR circle, and then I moved to the opposite point here to land at point B,

(Refer Slide Time: 08:31)

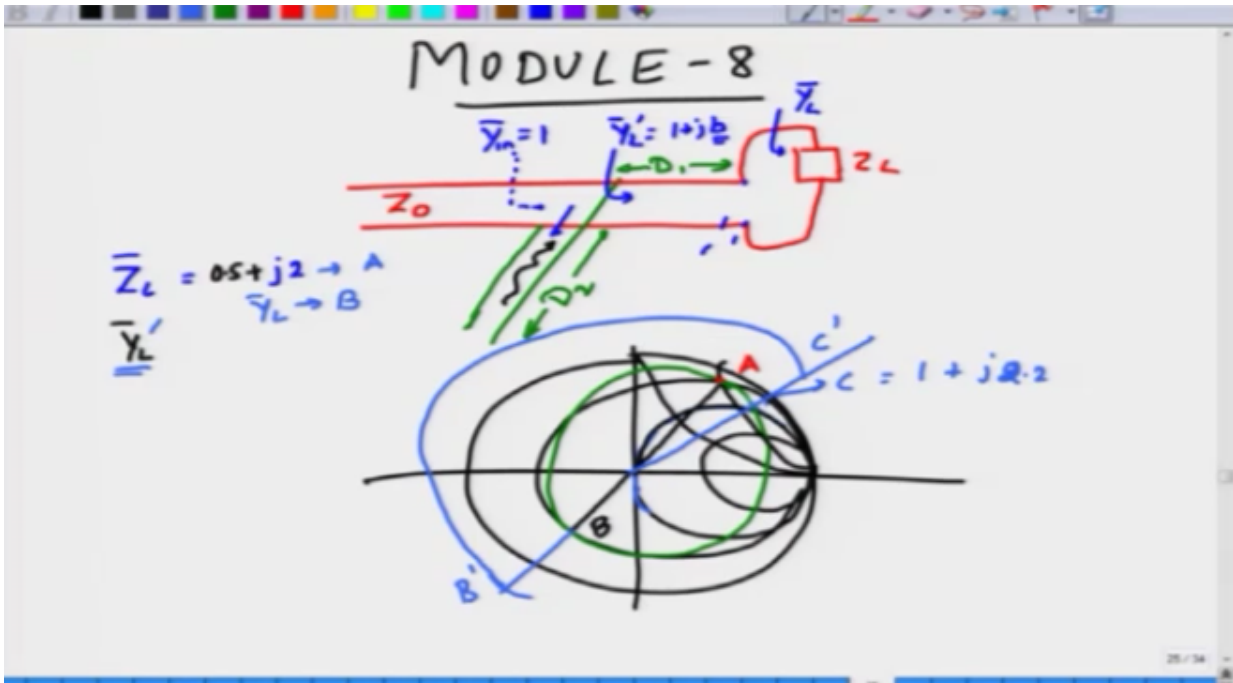

right, so this point was C prime and the intersection of these two points was the point C that we have found out, okay, so this length from B prime to C prime arc length will be given by D1.

Now you could observe an interesting thing as you keep moving along this green line, right, you'll actually land up at one additional cross-section or additional intersection which we can call it as say D, and then D prime the arc length B prime, D prime you know is also another solution which we will call ad D1 prime for the stub position, so you could choose either to place the stub at the arc at B prime, C prime,
 (Refer Slide Time: 10:36)

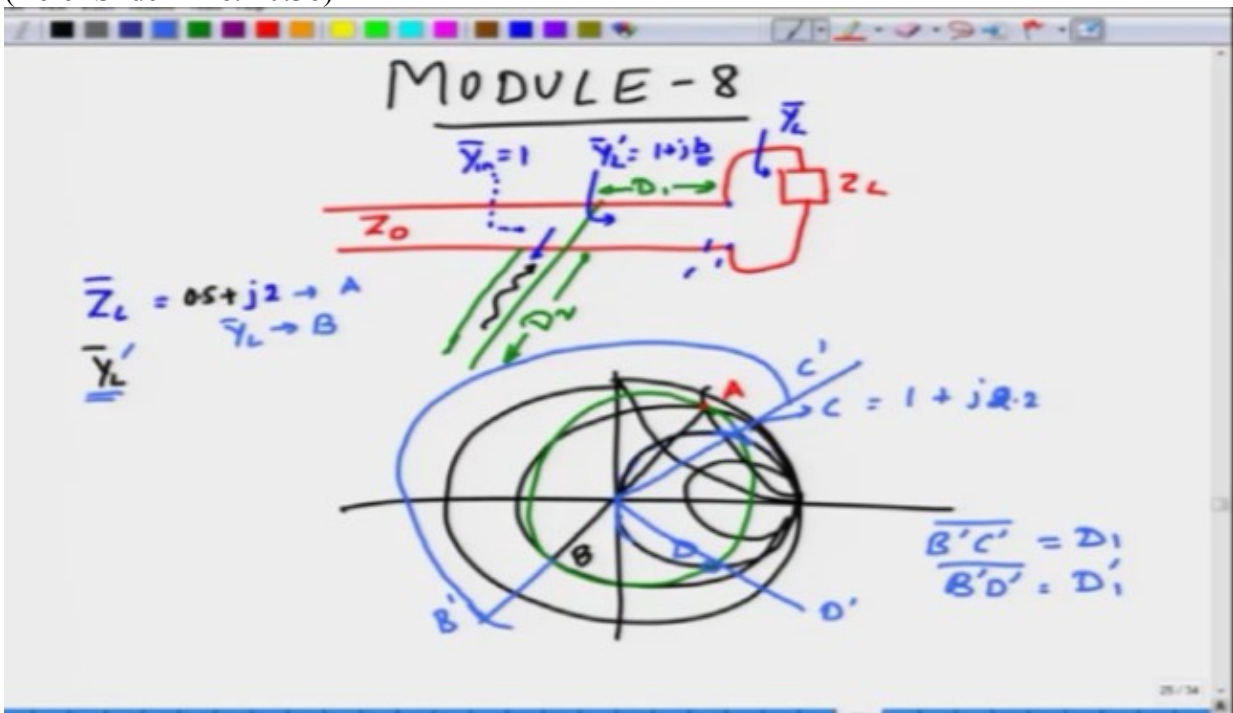


okay where the impedance is of the nature $1 + jB$, some position value of B or you could place the stub at a length $D1'$ where this admittance Y_L' is actually of the form $1 - jB$ something, okay, so both are actually possible and you can pick one of the solutions, so let's arbitrarily pick the solution to be $D1$, you want to place the stub as close as possible to the load that is there, okay, so you don't want to place it too far from the load, because the lines are usually not lossless, they are actually lossy so, the longer the line that you use the distance that you make $D1$, then the chances are there that there is excessive loss accumulated there, so you keep $D1$ you know short, and then after you have placed $D1$ and noted down what is the value of the impedance which in this case or admittance which in this case is roughly say $1 + j2.2$, you can again depending on whether you have an open circuit at stub or a short circuited stub you can start from this point which corresponds to open circuit admittance or this point which corresponds to short circuit admittance and move a certain length such that you make or you get $-jB$ in this case is 2.2 let's say, so you need to simply move on the outer circle and then move appropriately, okay.

And we can also notice that if you started off with a short circuit and you want a negative value of B that is you know admittance to B susceptance to be negative you will be covering a shorter distance then you start with an open circuited stub, okay.


And in fact in most printed circuit boards it is kind of easier to short circuited stubs rather than open circuited stub simply because open circuited means there is a chance for radiation also happening, okay, so this completes our shunt stub matching network, we have seen two cases where the real part is already equal to 1 in which case the stub is located right at the lower itself, but the length is chosen in such a way that the susceptance offered is minus of whatever the real imaginary part of the load Z_L is or the load admittance Y_L is, and if the admittance does not have a real part equal to 1 to begin with, then you have to move the stub length such that you get that real part equal to 1.

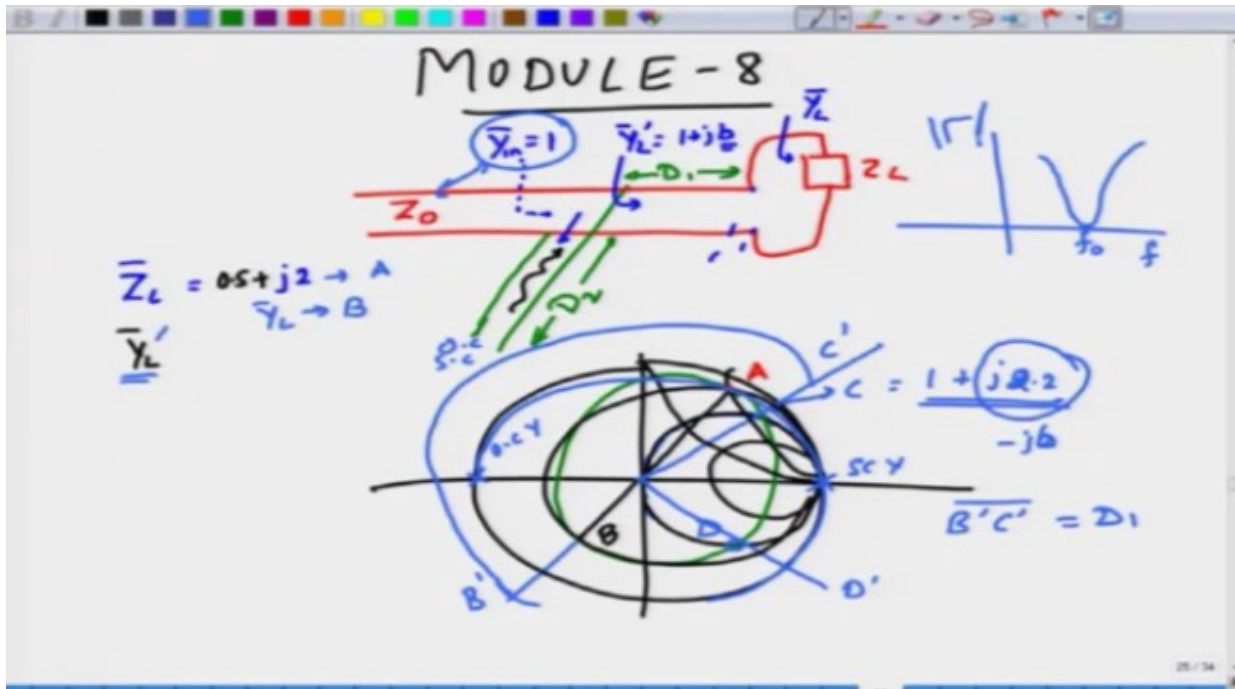And you try and you know use a combination such that you have $D1$ and $D2$ to be as small as possible by it turns out that you can't simultaneously satisfy both of them and it also you know happens that this kind of a matching is not really broadband, meaning that this match is very, very good for a given frequency but as you move away from that frequency of operation, (Refer Slide Time: 13:42)



for example when a pulse is traveling, the pulse spectrum is usually you know non-zero around that frequency where you have designed, right, then in that case what would happen is different frequency components will be slightly seen different values of the you know in equivalent input impedance Y_{in} , meaning that the reflection coefficient will not be zero over a small band, okay, in fact if you plot the magnitude of reflection coefficient between Y_{in} and Z_{naught} for different frequencies we'll see that it will be equal to 0 exactly at the design frequency F_{naught} , but then as we move away magnitude of γ quickly becomes larger, okay.

There are many techniques to make this broadband, okay, there are many techniques to make it even broadband as possible, but that could involve you know having more design parameters and those design parameters means we are going to have more than one stub, so in fact you can actually have another stub placed at a distance, sometimes you can also have a third stub placed and so on and so forth, okay,
 (Refer Slide Time: 14:11)

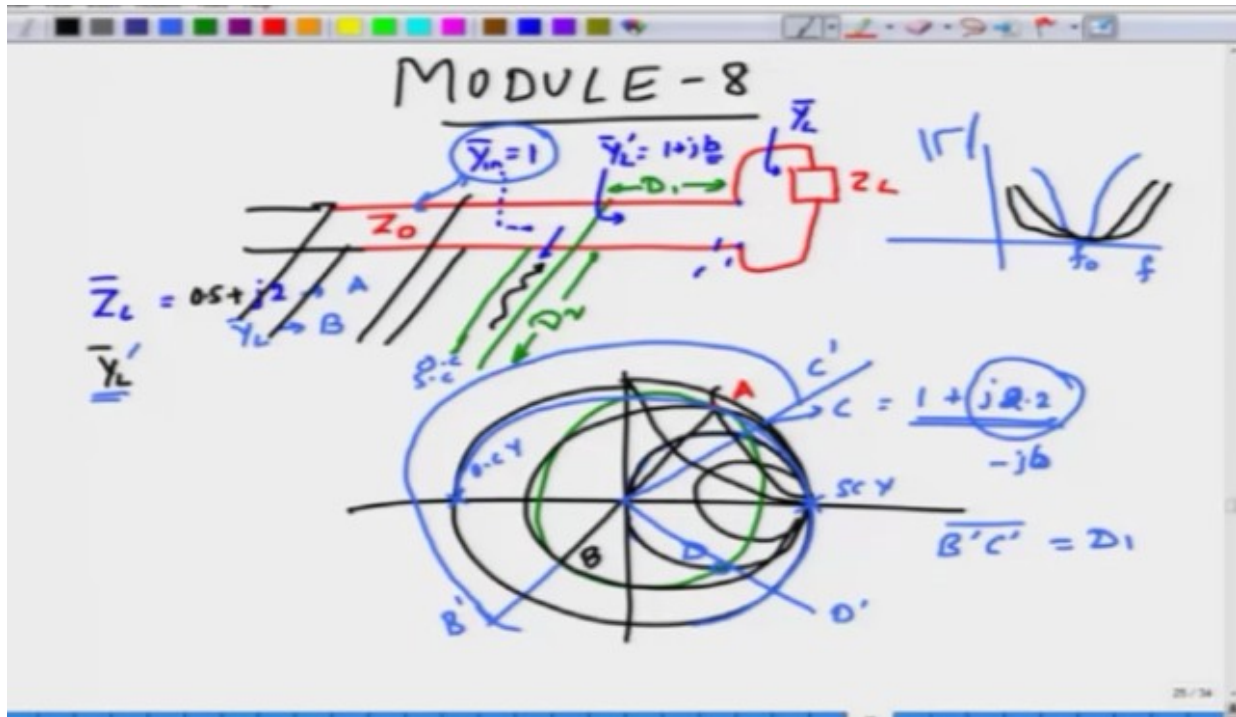

so we are completely not done with impedance matching, we will take up this subject later on when we look at plane waves and you know interaction of plane waves between 2 media, many of the concepts that we have discussed so far will be applied again there as well and those are also very interesting cases where interestingly even for the wave cases we can actually use this Smith chart, you can convert all those problems of uniform plane waves into equivalent transmission line problems and then work with even Smith charts and that is what we are going to do later on. Thank you very much.

Acknowledgement
Ministry of Human Resource & Development

Prof. Satyaki Roy
Co-coordinator, IIT Kanpur

NPTEL Team
Sanjay Pal
Bharat Lal
Ashish Singh
Badal Pradhan
Tapobrata Das
K. K. Mishra
Ashutosh Gairola
Puneet Kumar Bajpai
Bhadro Rao
Shikha Gupta
Aradhana Singh Rajawat
Sweta

**Nipa Sikdar
Anupam Mishra
Ram Chandra
Manoj Shrivastava
Dilip Tripathi
Padam Shukla
Sharwan K Verma
Sanjay Mishra
Shubham Rawat
Santosh Nayak
Pradyuman Singh Chauhan
Mahendra Singh Rawat
Tushar Srivastava
Uzair Siddiqui
Lalty Dutta
Murali Krishnan
Ganesh Rana
Ajay Kanaujia
Ashwani Srivastava
M.L. Benerjee**

**an IIT Kanpur Production
© Copyright Reserved**