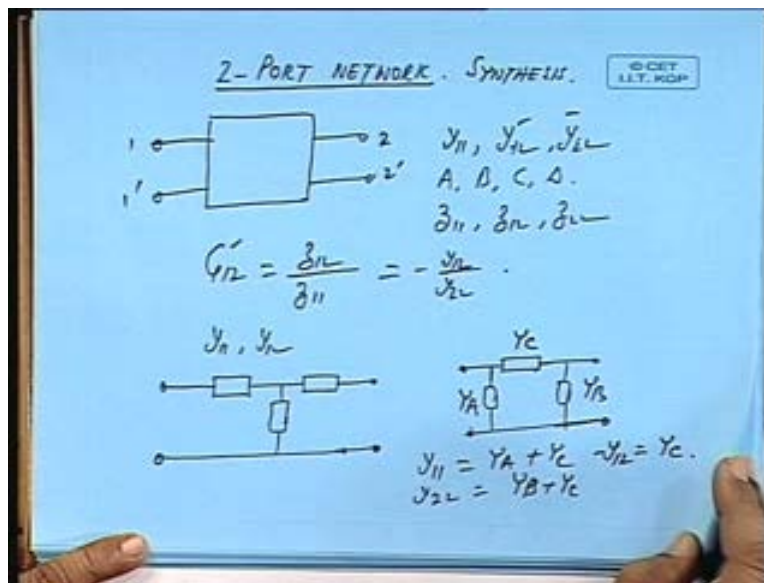


**Networks, Signals and Systems**  
**Prof. T.K. Basu**  
**Department of Electrical Engineering**  
**Indian Institute of Technology, Kharagpur**  
**Lecture - 32**  
**Synthesis of 2 - Port Network**

Good morning friends, today we will be discussing about 2 port network syntheses.

(Refer Slide Time: 01:02)




You know in case of a 2 port you have various specifications now, for a 2 port network  $Y_{11}$ ,  $Y_{12}$ ,  $Y_{22}$  these are the parameters or may be A, B, C, D or Z parameters and so on. These are the 3 commonly used sets sometimes you may be given only a gain function  $G_{12}$  which you know is given by this or minus  $Y_{12}$  by  $Y_{22}$ , so if this voltage by this voltage this is the gain function only the gain function is given then you are asked to realize a network to give that particular gain function all right.

So these specifications can be many of many types unlike 1 port network where we are given either Z or Y(s), Y(s) is just inverse of Z(s). So you have 1 specification here the specifications can be in terms of say  $Y_{11}$  and  $Y_{12}$  or  $Y_{22}$  and  $Y_{12}$ , any 2 can be given or may be just the gain function all right. So how to realize a network to meet these specifications? So before we go into that we just see the network functions how they are related to this 2 port parameters network elements.

Let us take a t network okay or a phi network from a t, you can always find a phi, this is start star to delta or delta to star conversion all right. Normally if you are given the specifications in terms of Z parameters you go for an equivalent t this is easier. Similarly, for Y parameters you go for phi network suppose this is given as  $Y_A$ ,  $Y_B$  and  $Y_C$ . Let us take this first what is  $Y_{11}$ ,  $Y_A$  plus  $Y_C$  very good  $Y_{22}$ ,  $Y_B$  plus  $Y_C$  and  $Y_{12}$  okay minus  $Y_{12}$  is  $Y_C$  okay.

Now these elements these elements  $Y_A$ ,  $Y_B$ ,  $Y_C$  they can be any RLC combinations okay. Let us see  $Y_{11}$  what are the poles of  $Y_{11}$ , the poles associated with  $Y_A$  and with  $Y_C$  will be the poles of  $Y_{11}$ . Similarly, poles of  $Y_{22}$  will be the poles of  $Y_B$  and  $Y_C$  so  $Y_C$  is the common element for the poles of  $Y_{11}$  and  $Y_{22}$  and also minus  $Y_{12}$ , so the common poles in these 3 will be the poles of  $Y_C$ .

(Refer Slide Time: 04:37)

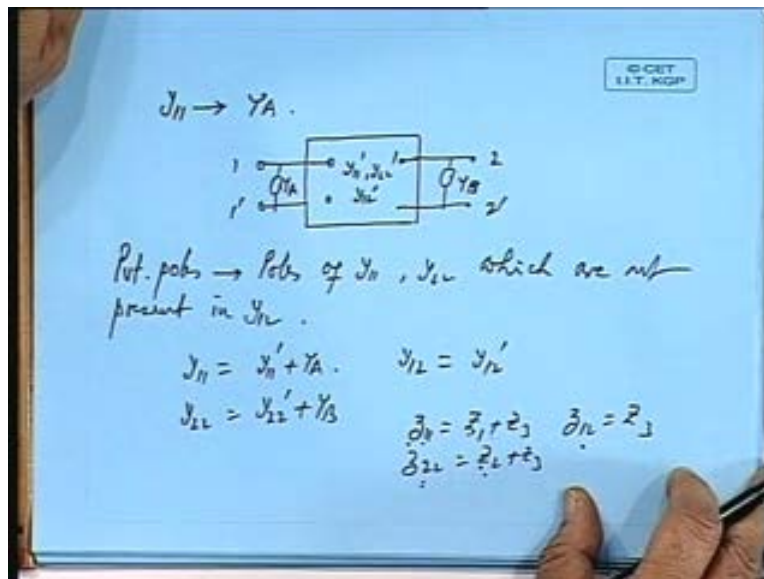


So in  $Y_{11}$  there can be some poles of  $Y_A$  which are not included in the other 2 functions all right. So poles of  $Y_A$  will be present only in  $Y_{11}$  nowhere else, similarly poles of  $Y_B$  will be present only in  $Y_{22}$ . So I can remove these poles still have such poles can be realized as separate elements, I am not given  $Y_A$  and  $Y_C$ ,  $Y_B$ ,  $Y_C$  separately, I am given  $Y_{11}$ ,  $Y_{22}$  and  $Y_{12}$  so out of which I find out the poles which are not present in  $Y_{12}$  but present in  $Y_{11}$ .

Similarly, the poles which are present in  $Y_{22}$  not in  $Y_{12}$ , I call them private poles of the 2 ports private poles of 1, 1 dashed and 2, 2 dashed okay poles of  $Y_{11}$  and  $Y_{22}$  which are not present, which are not present in  $Y_{12}$  okay. So the poles which are present in  $Y_{12}$  will be present in  $Y_{11}$  and  $Y_{22}$  but the converse is not true okay. So if I have a network which is having  $Y_{11}$  dashed  $Y_{22}$  dashed and  $Y_{12}$  dashed as the parameters then  $Y_{11}$  as seen from this side will be  $Y_{11}$  dashed plus  $Y_A$ , any addition of an admittance here will be adding to this value only, is it not. If I have another element another additional admittance here that will be changing only  $Y_{11}$  that will not be affecting these 2, is it not because it is only  $Y_A$  which is getting modified. So  $Y_{11}$  will be this

additional element plus whatever is a  $Y_{11}$  dashed here. Similarly,  $Y_{22}$  will be  $Y_{22}$  dashed plus  $Y_B$  but  $Y_{12}$  will be  $Y_{12}$  dashed is it not that remains unaffected.

Similarly, for the Z elements  $Z_{11}$  will be suppose this I call as  $Z_1, Z_2$  and say  $Z_3$  then  $Z_{11}$  will be  $Z_1$  plus  $Z_3, Z_{22}$  will be  $Z_2$  plus  $Z_3$  and  $Z_{12}$  is  $Z_3$ . So here also you see the poles of  $Z_3$  that is  $Z_{12}$  poles of  $Z_{12}$  will be present in  $Z_{11}$  and  $Z_{22}$  but the converse is not true  $Z_{11}$  and  $Z_{22}$  will have additional poles coming out of  $Z_1$  and  $Z_2$  okay. So if I have a series addition of such elements this is some  $Z_1, Z_2$  suppose this is having  $Z_{11}$  dash  $Z_{22}$  dash and  $Z_{12}$  dash then overall  $Z_{11}$  from this side I should write small z small  $z_{11}$  will be  $Z_1$  plus  $z_{11}$  dash, is it okay.


(Refer Slide Time: 08:53)

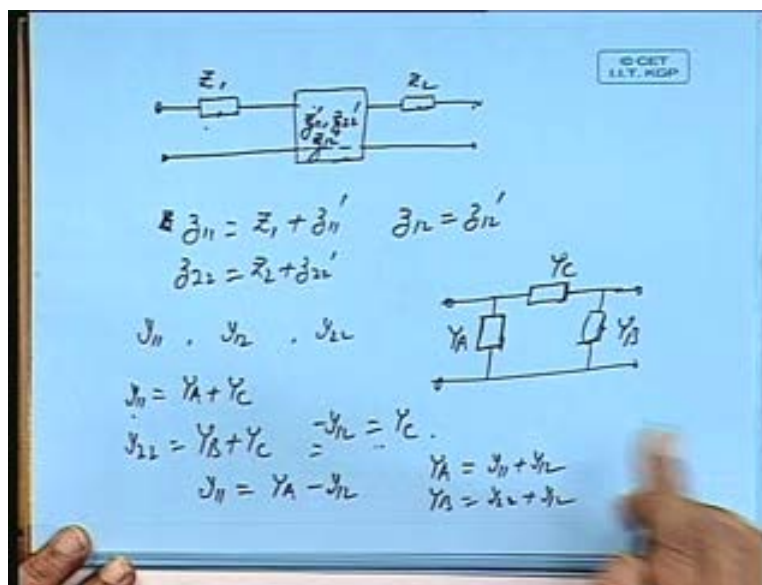

Similarly  $z_{22}$  will be  $Z_2$  plus  $z_{22}$  dash but  $z_{12}$  remains same. So once again the privacy poles of an impedance, so this is the series and shunt separation of private poles. Now let us see what are the requirements for the impedance functions? All right, what are the requirements for the impedance functions to be realized? Now let us take a  $y_{11}, y_{12}, y_{22}$  once again I draw the, now what is the  $y_{11}, Y_A$  plus  $Y_C$ , so this  $Y_A, Y_C, Y_B, y_{22}, Y_B$  plus  $Y_C$  and  $y_{12}$  minus  $y_{12}$  is  $Y_C$  okay.

So  $y_{11}, y_{11}, Y_A$  minus  $y_{12}$  is it all right or  $Y_A$  you can write as  $y_{11}$  plus  $y_{12}$  okay similarly,  $Y_B$  will be  $y_{22}$  plus  $y_{12}$  and  $Y_C$  is minus  $y_{12}$ . Now given any network, given any network you can have a very complex structure of a 2 port network and so all right that can be bridge elements also whatever be the type I can always reduce by repeated star delta conversion, repeated star delta conversion this entire set to either t or a phi, is it not. Now in this repeated star delta conversions what are the elements? How do you calculate the elements of a star delta set? Say in terms of impedances  $Z_1, Z_2$  plus  $Z_2, Z_3$  plus  $Z_3, Z_1$  divided by something all right divided by  $Z_1$  or  $Z_2$  or  $Z_3$  the operations are all positive, there is no subtraction okay.

(Refer Slide Time: 12:18)

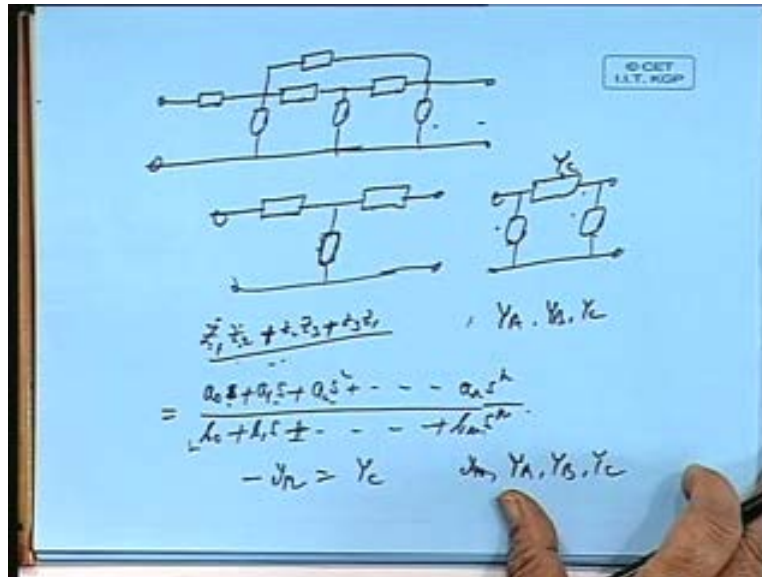

Now  $Z_1, Z_2, Z_3$  these will be R plus L, S plus 1 upon SC or their parallel combinations series combination, so there all having positive signs and these after multiplication also the signs do not change then again you are having additions. So all the elements will be finally added there is no subtraction, there is no chance of a negative sign, is it all right. So all these elements finally  $Z(s)$  or  $Y(s)$  elements here it is  $Y_A, Y_B, Y_C$  or  $Z_A, Z_B, Z_C$  these will be having the forms some  $a_0 s$  to the power  $a_0$  plus say  $a_1(s)$  plus  $a_2(s)$  square and so on divided by say  $a_n s$  to the power  $n$  divided by  $b_0$  plus  $b_1(s)$  and so on.

So  $b_n s$  to the power  $n$  okay these elements  $Y_{AA}$  these will be all positive real functions, so far as  $Y_A, Y_B$  and  $Y_C$  are concerned these 3 elements are positive real after all they are obtained after reduction of some positive real functions, star delta reductions. So this will be having expressions like this. Similarly,  $y_{12}$  minus  $y_{12}$  will be  $Y_C$ , so  $y_{11}$  sorry  $Y_A, Y_B$  and  $Y_C$  are all having positive coefficients of polynomials in the numerator and the denominator. So let us see  $y_{11}$ , what was was our  $y_{11}, Y_A$  minus  $y_{12}$  okay.

So suppose you are given minus  $y_{12}$  as  $a_0$  sorry otherwise I have a small slip, there was a small slip check  $y_{11}$  is  $Y_A$  plus  $Y_C$  okay  $y_{22}$  is  $Y_B$  plus  $Y_C$  all right and  $y_{12}$  minus  $y_{12}$  is  $Y_C$  okay therefore  $y_{11}$  it may be given, let us write the denominator may be some polynomial, numerator can be any polynomial that will be a common polynomial if there is no private poles okay. We can consider a common polynomial for the denominator then this can be say  $a_0$  plus  $a_1(s)$  plus  $a_2(s)$  square and so on,  $y_{22}$  is  $b_0$  plus  $b_1(s)$  plus  $b_2(s)$  square and so on and  $y_{12}, c_0$  plus  $c_1(s)$  and so on okay.

(Refer Slide Time: 15:32)

$y_{11} = Y_A - y_{12}$   
 $-y_{12} = a_0$

$y_{11} = Y_A + y_{12}$   
 $y_{12} = Y_A + y_{12}$   
 $-y_{12} = y_{12}$

$y_{11} = \frac{a_0 + a_1s + a_2s^2 + \dots}{g(s)} \quad a_0, a_1, \dots \geq 0$   
 $y_{12} = \frac{b_0 + b_1s + b_2s^2 + \dots}{g(s)} \quad b_0, b_1, \dots \geq 0$   
 $-y_{12} = \frac{c_0 + c_1s + \dots}{g(s)} \quad c_0, c_1, \dots \geq 0$

(Refer Slide Time: 18:19)

$y_{11} + y_{12} = Y_A$

$a_0 - c_0 \geq 0 \quad a_1 - c_1 \geq 0$   
 $a_2 - c_2 \geq 0$   
 $\vdots$   
 $b_0 - c_0 \geq 0$   
 $b_1 - c_1 \geq 0$   
 $\vdots$

$y_{12} + y_{12} = Y_B \rightarrow b_0 - c_0 \geq 0$   
 $b_1 - c_1 \geq 0$   
 $\vdots$


$y_{11} = \frac{2s + 5}{g(s)} \quad -y_{12} = \frac{s + 1}{g(s)}$   
 $y_{12} = \frac{s + 2}{g(s)}$

So one of the conditions is  $a_0, a_1$  these must be greater than equal to 0 that is what we have seen all of them should be positive similarly  $b_0, b_1$  must be greater than equal to 0,  $c_0, c_1$  etcetera must be greater than equal to 0 all right, what is  $y_{11}$  plus  $y_{12}$ ?  $Y_A$ , is it not,  $y_{11}$  plus  $y_{12}$  is  $Y_A$  is it all right now  $Y_A$  has to be with all positive coefficients. So if I substitute here  $y_{11}$  plus  $y_{12}$  means  $a_0$  minus  $c_0$ ,  $a_1$  minus  $c_1$  all right into  $s$  so that gives me  $a_0$  minus  $c_0$  must be greater than equal to 0  $a_1$  minus  $c_1$  must be greater than equal to 0,  $a_2$  minus  $c_2$  must be greater than equal to 0 and so on okay.

Similarly, by the same logic  $y_{22}$  plus  $y_{12}$  is how much,  $Y_B$  and that also we discussed after a repeated reductions  $Y_A, Y_B, Y_C$  must have all positive coefficients in the numerator, so  $y_{22}$  plus  $y_{12}$  also must be having numerator coefficients as 0. So  $b_1$  minus  $c_1$  is greater than 0,  $b_0$  minus  $c_0$  is greater than 0 greater than equal to 0 and so on, all right. So these are the coefficient conditions to be satisfied when you are given the specifications is it all right. So  $y_{11}$  suppose is given  $2s$  plus  $5$  divided by some denominator,  $y_{22}$  is given  $s$  plus  $2$  divided by same denominator and  $y_{12}$  minus  $y_{21}$  is given  $s$  plus  $7$  by the same denominator. Is it possible to realize this, let us see  $y_{11}$  and  $y_{12}$  the coefficients first coefficient  $5$  minus  $7$  is negative, so it is not possible all right.

So this must be less than 2 if it is  $s$  plus 1 yes, it is possible suppose it is  $2s$  plus 1 then this is all right but this is not satisfied okay. So if you are having the coefficients of the numerator given like this the polynomials are given then by applying this rule you can check whether it is realizable or not, all right whether the network can be realized. So this is known as Fialkow Gerst Condition.

(Refer Slide Time: 21:39)

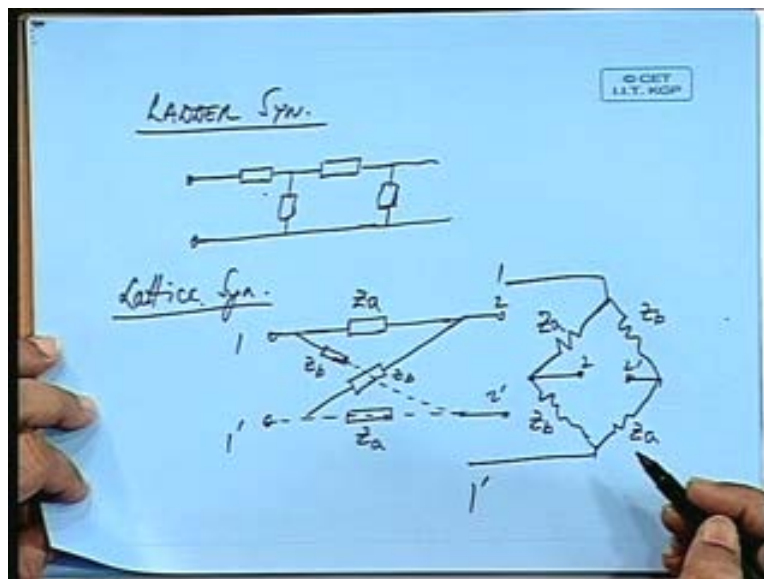


So before going for any synthesis we must see that these coefficient conditions are satisfied. There are 2 ways of realizing a 2 port network, one is Ladder Synthesis that is you try to go for realizing the Os of transmission in steps from one end or there is a there is another one Lattice Synthesis which will be taking up later on that is a very interesting synthesis. It is a structure like this okay if you want you can have repeated block surface, so this is a Lattice network they are  $Z_a, Z_b, Z_b, Z_a$  it is like a bridge basically this is  $Z_a, Z_b$  and you take the output from here, this is 1, 1 dashed and 2, 2 dash this 1 as 1, 1 dashed, 2, 2 dash okay.

We shall see what are the Os of transmission and how to realize them okay. Whenever you are having  $a_0$  somewhere what do you mean by Os of transmission transmission Os means what I

give a signal at the other end nothing is received, is it not. Now in how many ways that can be ensured I give a signal you take a water pipe line all right. In what are different possible ways, the say delivery of water at the other end can be disrupted, very good there is a leakage so water is grounded basically the pipe is grounded the entire pressure is grounded is there any other way of blocking.

So if you have some blockade in the series path or a short circuit in the shunt path then you have a 0s of transmission that means how do you create a 0s of transmission by short circuiting at some frequency suppose at some frequency I find s squared plus 9 in the numerator that means at s equal to  $J_3$ , this s square plus 9 will be vanishing that is  $a_0$  at that particular frequency. So at the frequency I want there should be no transmission of signal and I want short circuit at that particular frequency, no, short circuit means what it should basely is resonance if have a series resonance at s equal to  $J_3$  and that element is put in shunt okay. So you are having an element like this there are many such elements in the ladder I create this element is say an lc combination.

(Refer Slide Time: 25:35)

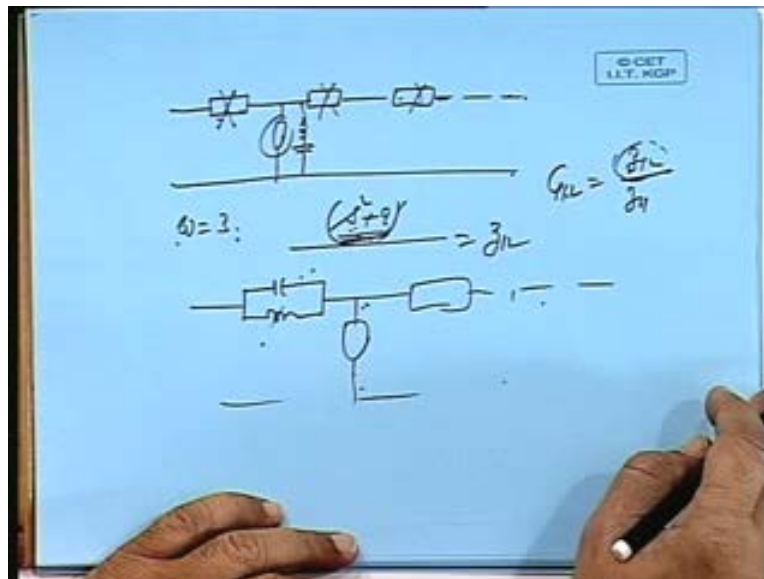


Suppose this is resonating at omega equal to 3 then s squared plus 9 will be giving me omega is equal to 3 this is resonating frequency, this will be the numerator okay. So in  $Z_{12}$  if I have a numerator of this kind s squared plus 9 my target will be to create  $a_0$  in the shunt element such that the elements are having a resonance frequency at omega equal to 3, is it all right or alternatively I open any of these that means there is no transmission after this. So how do I create that, how do I create that at omega equal to 3, now how to create that parallel resonance, anti-resonance.

So if I have an anti-resonance element any of these at that frequency and then there are others then also it can be blocked. So  $a_0$  of transmission can be created 0 of transmission means

because  $G_{12}$  is  $z_{12}$  by  $z_{11}$ , so it is the 0 of this which will be the 0 of this transfer function okay, so output will be 0 at that frequency. So that can be created either by a parallel resonance here or a series resonance is here in the shunt element, is it okay. So you keep on repeatedly removing all the 0s by adjusting these elements okay. So this is the technique of 2 port synthesis when you are given the transmission 0s you convert them into poles and then try to realize the pole any 0 can be realized in terms of a pole, is it not? How to do that?

Suppose you are given  $z_{12}$  how do remove that, how do, how do I remove a pole  $a_0$  you take inverse of that function if it is in the admittance form then you convert it into impedance and then make partial fraction corresponding to that pole remove that okay.

(Refer Slide Time: 28:22)

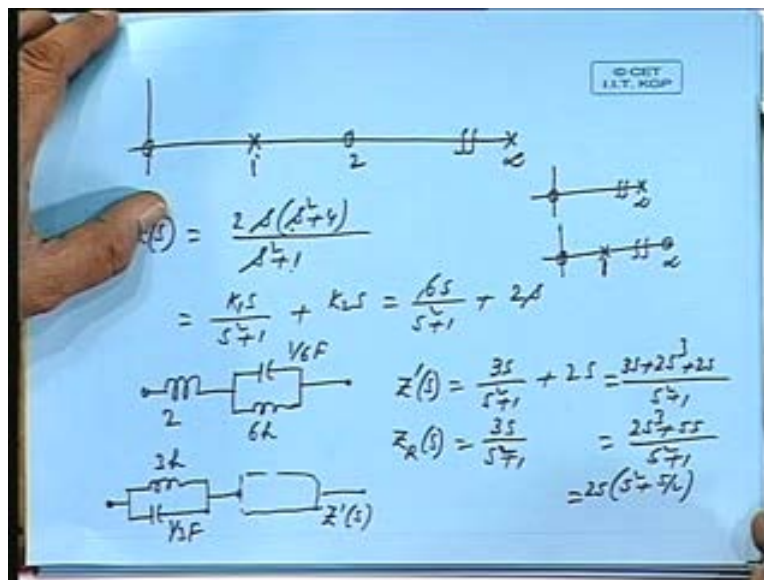

Let us take before we go further let us take a function  $Z(s)$  equal to say any function you tell me it is a 2 into s into s squared plus 4 by s square plus 1 okay I can make partial fractions  $K_1(s)$  by  $S$  square plus 1 plus  $K_2$  into  $S$  okay,  $K_1$  comes out as if I multiply by  $S$  square plus 1 divided by  $s$  and make  $s$  square plus 1 equal to 0. So it will be 3 into 2, 6,  $6S$  by  $S$  squared plus 1 plus  $K_2$  into  $S$ , how much is  $K_{22}$  into  $s$  all right. So that means 2 Henry, how much is this 1 by 6 farad and 6 Henry okay. Now if I remove  $2s$  from here from here if I remove this  $K_2$  totally, if I remove  $2s$  whatever is left over will content only the other pole all right. If I remove this I am left with only  $2s$  now in this the 0s are at 2, 1 and this is a pole, this is a pole 0 configuration. 0 then pole at 1, 0 at 2 and pole at infinity okay.


Now suppose in this I, when I remove this I remove the pole at this one, what I am left it only  $2S$ , a 0 here and a pole here okay for this function if I remove this what will be the pole 0 configuration for 2,  $s_0$  here and a pole here at infinity if I remove this  $2s$  then 0 here, pole at 1 and a 0 here okay. So if I remove this pole totally this 0 also gets eliminated all right. If I remove okay, if I remove this pole, this pole okay means this is having a pole at infinity, is it not, if I



remove the pole at infinity then infinity becomes a 0 and this pole remains where is this pole. So this pole remains at 1 but the other pole has created a 0 here okay.

Now if I do not remove the poles or the poles of either this or that totally if I retain some part of it what happens that means instead of  $6S$  plus  $s$  square plus 1 suppose I take  $3S$  by  $s$  square plus 1 okay. Then I call that balance admittances  $Z$  dashed  $S$  as  $3S$  by  $s$  square plus 1 plus  $2S$  okay and some  $Z$  removed  $S$  is  $3S$  by  $s$  square plus 1 that means 50 percent have removed 50 percent have retained. So if I remove 50 percent of this means what,  $3S$  by  $s$  square plus 1 means allow 3 Henry, 3 Henry and 1 third Farad. Suppose I take out an element like this whatever is left over is  $Z$  dash into  $S$ , is it not what is  $Z$  dash into  $S$ , what will be the poles and 0s of this, poles will remain same I am not disturb the pole what about 0s.

(Refer Slide Time: 34:49)

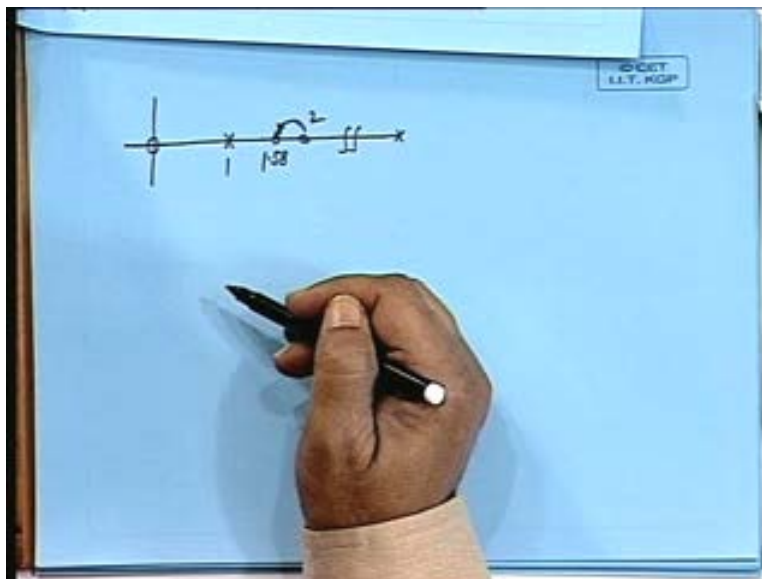

Now this is not totally removed, it will have a new 0 all right, what I have done is I have not totally removed this pole, I have weakened the pole, I have removed the part of that residue residue was  $6S$  all right. So I have taken a part of it, so if I remove a part of that pole that is called part removal of the pole then what do I get in the oral distribution of poles and 0s poles remains as they are they were but what about 0s. So this will be  $3S$  plus  $2S$  cubed plus  $2S$  all right that means divided by  $s$  square plus 1 that means  $2s$  cubed plus  $5S$  in the numerator so  $S$  into if I take  $2S$  common then  $S$  squared plus  $5$  by  $2$ , correct me if I am wrong okay.

So the new distribution of pole and poles and 0s will be 0 at the origin is remaining intact all right, pole at 1 is again appearing because I have not removed it completely, what about this 0, this 0, it is now root over of  $5$  by  $2$ , it has earlier it was at  $2$ , now it has drifted towards this. Pole at infinity that also remains as it is okay. So this 0 at  $2$  has now shifted to root over of  $5$  by  $2$  okay approximately  $1.58$  okay. So if I weaken a pole I can shift  $a_0$  to a desired position I have taken out only 50 percent of this  $6S$ , this I said you I could have taken any percentage and hence

I could have shifted this to a desired location, is it all right. Therefore, by partial removal of a pole I can create a zero at a desired position some of the zeros can be shifted, had there been many other floating zeros means between 0 and infinity, had there been some more zeros they would have all drifted towards the pole all right. The drift will be by different amounts all right.

(Refer Slide Time: 36:19)

© CBT I.I.T. KGP

© CBT I.I.T. KGP

$$z(s) = \frac{2s(s^2+1)}{s^2+1}$$

$$= \frac{k_1s}{s^2+1} + k_2s = \frac{1s}{s^2+1} + 2s$$

$$z'(s) = \frac{3s}{s^2+1} + 2s = \frac{3s + 2s^2 + 2s}{s^2+1}$$

$$z''(s) = \frac{3s}{s^2+1} = \frac{2s^2 + 5s}{s^2+1}$$

(Refer Slide Time: 38:02)

$$= \frac{2s(s^2+1)}{s^2+1}$$

$$y(s) = \frac{(k_1s)}{(s^2+1)}$$


I am not bothered about the drift of all the zeros, I may be concentrating on one zero specially then nearest one, the one which is nearest to this preferably to locate it in a new position and this is

not the only pole there could have been other poles and my desire would have been to shift this to this side then I would have weakened this one, is it all right. So it all depends on what is the 0 wanted that means in  $Z_{12}$  in the transmission I am creating artificial 0s all right by removing the poles partly this is known as partial removal of poles and shifting of 0s okay. So you can weaken either the pole corresponding to this or this that means you weaken the pole here that also you could have seen. Let us see now, instead of  $2S$  if I take  $S$  what happens I remove only one hand inductor and rest of it, I retain.

Now here I have created a 0 in  $Z_1$  dash into  $S$  which is at root  $5$  by  $2$  so this element is having a 0 let me complete this then will go to partial removal of this pole at infinity. So I have got a network like this and then  $Z$  dash into  $S$  is a function which is having a 0 at  $S$  square plus that is at root  $5$  by  $2$  it is having a 0, how do I realize this any 0 you convert it to a pole. So I correspondingly I will take  $Y$  dash into  $S$  which will be giving me  $S$  square plus  $5$  by  $2$  in the denominator okay then there are other factors okay and this one I will write as  $K_1(s)$  by  $s$  square plus  $5$  by  $2$  plus other factors that means  $Y$  dash the admittance is taken as some  $Y_1, Y_2, Y_3$ .

So this entire  $Z$  dashed which was appearing here is now taken as some  $Y_1, Y_1$  which will be corresponding to this all right that means it will be having, this is an LC series element, is it not if  $Y$  corresponds to  $K(s)$  by  $S$  square plus  $\omega$  square that will give you a series LC element okay and then rest of it I will again switch over to  $Z(s)$ . I am not bothered about this part, I am interested only rem in removing that 0, so convert it to a pole that is go to an admittance function then realize that and then again the balance you again invert you will get rest of the elements 1 by 1 you take out the 0s in the shunt elements okay.

(Refer Slide Time: 40:30)

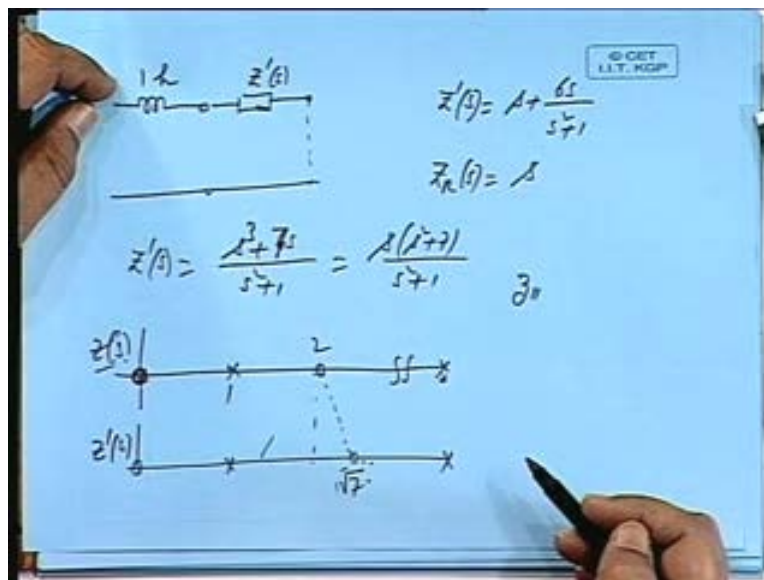


So this will be resulting at root  $5$  by  $2$  so that will be creating the 0 all right by partially removing the pole we can realize this. Let us see if we partially remove the pole at infinity that is let us

take again 50 percent removal just take S. So we have got 1 henry it is Z dash into S now, is s plus 6 S by S square plus 1 and Z removed is just s okay. Now what is Z dash into S, s cubed plus S plus 6S, so s cubed plus 6S divided by s squared plus 1 sorry 7S. So s into s squared plus 7 by s squared plus 1 now what will be the pole 0 location, earlier it was a pole sorry a 0, a pole a 0 and a pole.

Now I have weakened this so under the new situation Z dash into S this was for Z(s), Z dash into S is having 0 once again at the same point, pole at the same point, this pole is also at infinity but here it is earlier it was 2, now it is root 7, now it has drifted to this side. So 0 has drifted towards this pole which has been weakened, so wherever you are weakening the pole the 0s will drift towards that okay. Earlier it was in the other side so the 0 drifted to that side, so depending on the 0 that is given in the transmission, this is corresponding to the transmission 0.

So the 0s are transmission where they are located and what is given in  $z_{11}$  if you know that  $z_{11}$  is at 2 and the 0s required 0 of transmission is at root 7 then I will be weakening this pole first, so that this drift safe all right. If I weakened this pole then it will be drifting to this side I cannot realize this 0 all right. So this is the technique that we follow for ladder development and we want 0 at that particular frequency so what should be the value of that residue that is we have seen only 50 percent removal, what should be the percentage removal? What should be the percentage removal of the residue, percentage removal of the residue. So that we can get the desired location of the 0 okay.

(Refer Slide Time: 43:51)

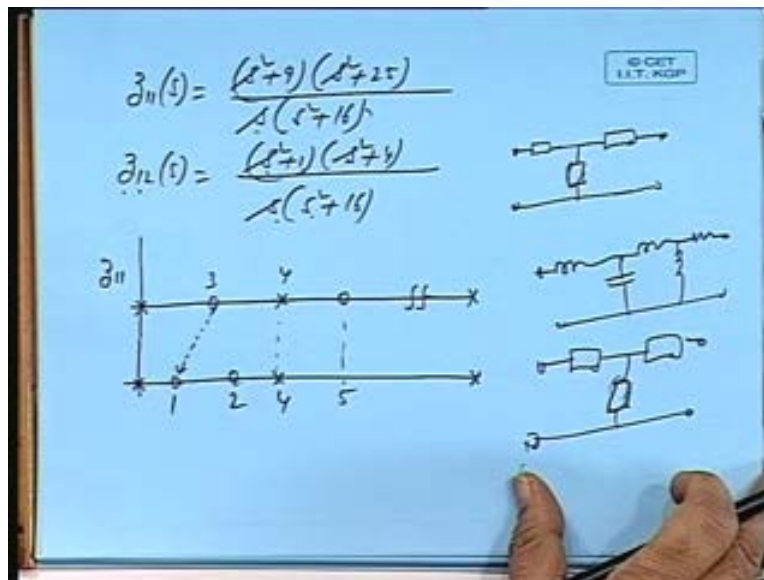

So that is a next question, let us take up an example it will be clear say  $z_{11}(S)$  is given as s squared plus 9 into s squared plus 25 divided by s into s squared plus 16 okay. Let us make a plot of this poles and 0s first and then decide about the shifts, so there are no private poles  $z_{12}$  and  $z_{11}$  are having the same poles all right, if there are private poles remove that first. So poles and 0s

are for  $z_{11}$  is it has is the original 0 pole then 3, 4 okay then not to the scale any way 5 and then at infinity there is a pole, this is  $z_{11}$ ,  $z_{22}$ ,  $z_{12}$  pole, poles are same because there is no private pole. So the poles are identical and then this one is at 1 and then this is at 2.

Now in the transfer admittance, transfer admittance or transfer impedance, there is no hard and fast rule that poles and 0s should alternate, transfer admittances  $z_{12}$ , how much is  $z_{12}$  in terms of  $z_1$ ,  $z_2$ , they need not be okay we will discuss about it later on, see the poles and 0s need not come alternatively, so they need not be positive real functions, they need not be positive real function, is that clear. Any question? They need not be positive real functions how follows us  $z_{12}$  by repeated star delta conversions, you got  $z_{12}$  as this impedance but this need not be a positive real function, this need not be a positive real function.

Only thing is the numerator and denominator coefficient must be always positive when you go for repeated star delta conversions you must get all the coefficients as positive but repeated conversion of star and delta that need not guaranty positive real functions as elements that means the element may not be realizable, element may not be realizable. For example you are having an inductor and capacitor, an inductor, an inductor and resistor and so on. If I reduce it to star or a delta this may give you some  $Z(s)$  it may not be realizable it will be having a function all right with all positive coefficients  $a_1(s)$ ,  $a_2(s)$  squared and so on divided by  $b_1(s)$   $b_2$  square but it may not be a positive real function they may not be able to realize it by RLC, okay it is a very interesting point.

(Refer Slide Time: 49:01)

The image shows a blueboard with handwritten mathematical work. A hand is pointing to the first line of the derivation.

$$Z_n(s) = k_1 s + \frac{k_2 s}{s^2 + 16} + \frac{k_3}{s}$$

$$= k_1' s + Z_n'(s) = \frac{k_2' s}{s^2 + 16} + Z_n''(s)$$

$$Z_n(j1) \text{ or } Z_n(j\omega) = 0$$

$$Z_n'(j1) = 0 \qquad k_1' = \frac{8 \times 24}{15 \times j}$$

$$Z_n(j1) = k_1' \cdot j1 \qquad = -\frac{64}{5}$$

$$\cancel{Z_n''(j1) = 0}$$

So this is very clear from  $z_{12}$  itself here  $s$  squared plus 1 into  $s$  squared plus 4 by  $s$  into  $S$  squared plus 16. So you can see the 0s are coming consecutively coming 2 consecutive 0s and then pole comes, so what should I do I can shift this 3 so these are the values 1, 2, 4 and 5 either I can shift this 0 here or this 0 here. So either you can weaken this or weaken this, is it not. So if you want

to shift this here you have to weaken this that means a part of this residue has to be removed okay so  $z_{11}(s)$  let us break up  $z_{11}(s)$  if you write as  $K_1(s)$  plus  $K_2(s)$  by  $S$  squared plus 16 plus  $K_3$  by  $S$ , I am not really concerned about all these, I am interested only in a partial removal of this.

Suppose I write this as some  $K_1$  dashed  $S$  plus  $z_{11}$  dashed  $S$  that means this is the part removed, this is the part removed and this is what is remaining all right. Now  $z_{11}(s)$ , so  $z_{11}$  either at  $j$  equal to  $\omega$  sorry  $\omega$  equal to 1 that is  $S$  equal to  $j_1$  or  $s$  at  $j_2$  this will be vanished all right sorry, the impedance at that point, impedance sorry impedance at that point  $j_1$  or impedance at  $j_2$  I want this to be 0 for  $z_{11}$ ,  $z_{12}$  for  $z_{12}$  this will be equal to 0, is it not. So  $z_{11}$  dashed,  $z_{11}$  dashed at  $j_1$  if I take it as 1 because I am shifting it here, should be equal to 0 is it not this must be 0. So what is this if I put on this side  $z_{11}$  at  $j_1$  should be equal to  $K_1$  dashed into  $j$ ,  $S$  equal to  $j_1$ . So how much is  $K_1$  dashed calculate from here, is it okay  $z_{11}$  that was given as  $s$  square plus 9 into this thing, so put  $S$  equal to  $j_1$ , so that is 9 minus 18 into 25 minus 1 into 24 divided by 15 into  $j$  okay and this  $j$  is there already.

So that gives me  $K_1$  dashed into  $j_1$  all right  $K_1$  dashed into  $j_1$ , so calculate this how much is  $K_1$  dash comes out as minus 64. Now check whether it should be minus  $z_{11}$   $j$   $\omega$  plus  $K_1$  dash into  $j_1$ ,  $j_1$  is equal to 8 into 24 divided by  $S$  into  $s$  squared plus 1 or 15, is it all right. We are trying to make it at 1 it is a 0, so 1 okay  $K_1$  dash it is let us see whatever be that value minus 64 by now  $j$  into  $j$  will be so it will be plus minus 64 by 5 so that means we will have to add that seems to be some out funny this there made some slip okay.

Let us see the other one I come back to this you also, also think over it why we should get this or what we are trying as  $K_2$  dashed  $S$  by  $S$  square plus 16 into some  $z_{11}$  double dashed  $S$  either remove this part partly, remove this partly then it will be shifting to 2 sorry, sorry, sorry, sorry 3 will be 2, thank you very much that is why this scaling was very very important. So in any case you can weaken this to shift it to either 1 or 2 okay, thank you.

So in that case what will be this one,  $z_{11}$  double dashed at  $j_2$  should be equal to 0, this is  $a_0$  which gives me yes, sorry we are weakening the pole at the origin that is what I am putting  $j_2$ , I am going to write that, that is what I am going to do, this will be  $z_{11}$ . Okay, let us write it here, okay we will continue with this in the next class. Now time is over we will continue with this in the next class, thank you.