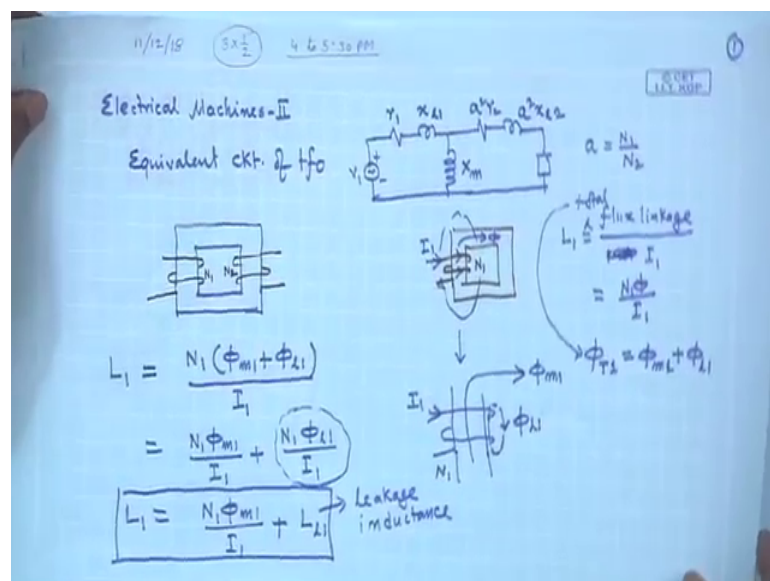


Electrical Machines - II
Prof. Tapas Kumar Bhattacharya
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture – 04
Co-efficient of Coupling Energy Stored in Coupled Coils

So, welcome to this next unit of Electrical Machines II in last three units what we actually did is this one.

(Refer Slide Time: 00:29)




That we tried to find out the equivalent circuit of a transformer from circuit point of view and from the concept of a self and mutual inductances you recall very quickly I will tell that. So, this is 2 coupled coils having turns N_1 and N_2 and then when you pass some current through the coil it produces flux the direction of the flux can be obtained by wrapping your other fingers along the flow of the current and thumb will give you the direction of the flux so, ϕ .

So, when you pass some current through a single coil it produces fluxes which can be broken up into 2 parts. So, one is the flux component which is confined to the core that I call mutual flux and the other flux which will be leakage flux ϕ_{L1} . Suppose coil 1 that is current I_1 then inductance is defined as total flux linkage per unit ampere. So, ϕ_{m1} plus ϕ_{L1} by I_1 in to N_1 gives you the inductance.


This part of the inductance which this flux completes its path through the air gap and this flux causes an inductance of a leakage inductance which is L_{l1} and this is L_1 .

(Refer Slide Time: 02:05)

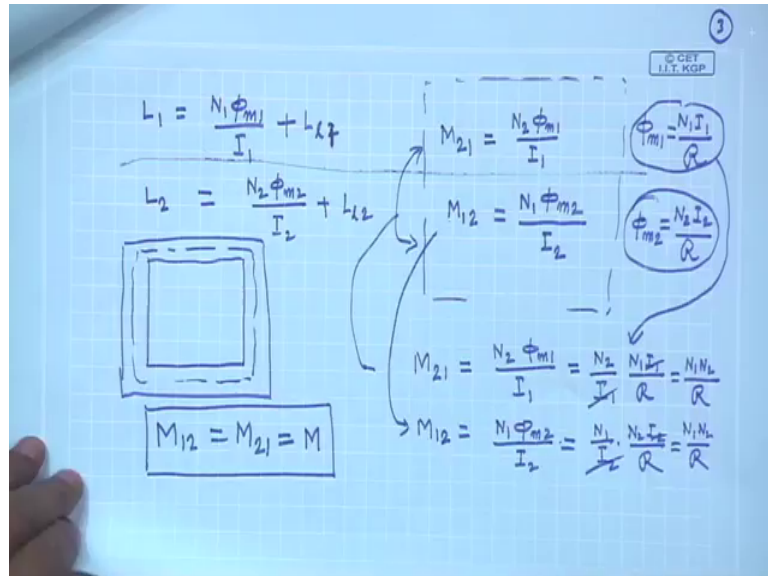

In the same way we did for L_2 and then I showed that M_{21} I defined mutual inductance and mutual inductance whether you calculate it from coil 1 or from coil 2 it remains same M_{12} is equal to M_{21} because, reluctance of the common magnetic circuit is same.

(Refer Slide Time: 02:31)

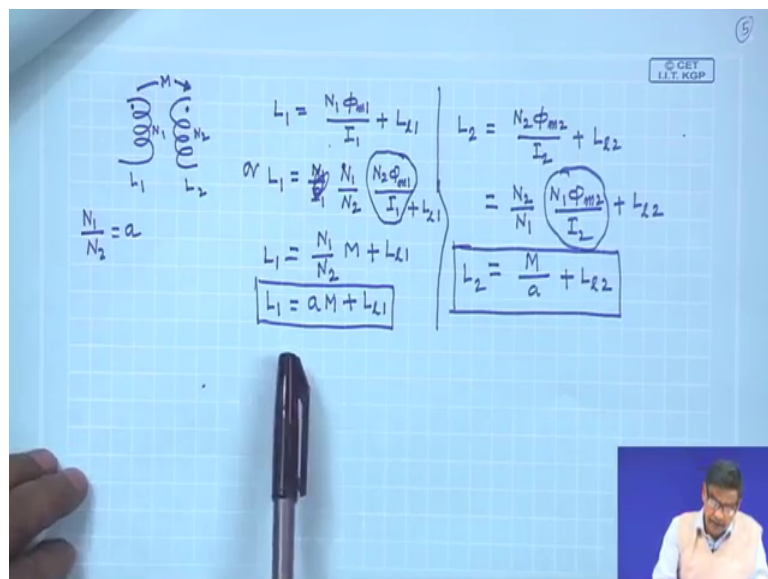

Then the important thing is ultimately we showed that the self inductance of the coil in terms of mutual and leakage inductance comes out to be this L_1 and L_2 is like this.

(Refer Slide Time: 02:49)

$$\text{KVL in p.v.} \quad V_1 = I_1 r_1 + j\omega(L_1)I_1 - j\omega M I_2 \quad \text{--- (1)}$$

$$\text{KVL in sec} \quad *j\omega L_2 I_2 - j\omega M I_1 + I_2 r_2 + I_2 Z_2 = 0 \quad \text{--- (2)}$$

$$L_1 = aM + L_{x1} \quad \text{and} \quad L_2 = \frac{M}{a} + L_{x2} \quad \text{where } a = N_1/N_2$$

$$V_1 = I_1 r_1 + j\omega(aM + L_{x1})I_1 - j\omega M a \frac{I_2}{a}$$

$$\text{or } V_1 = I_1 r_1 + j\omega a M \left(I_1 - \frac{I_2}{a} \right) + j\omega L_{x1} I_1$$

And finally we wrote down the KVL equations from the two sides remembering the fact how to put the dots on these two coils knowing those dots I will be correctly writing the KVL equations with the appropriate polarities of this voltages students often make confusion

But I hope you practices it. so that this will be no problem at all and finally, we found out the equivalent circuit like this here.

(Refer Slide Time: 03:27)

$$\text{1st coil } V_1 = I_1 r_1 + j\omega a M \left(I_1 - \frac{I_2}{a} \right) + j\omega L_{x1} I_1$$

$$\text{2nd coil (Ref. to primary)}$$

$$j\omega (aM + aL_{x2}) \frac{I_2}{a} - j\omega a M I_1 + \frac{I_2}{a} a r_2 + \frac{I_2}{a} a Z_2 = 0$$

$$= j\omega a M \left(\frac{I_2}{a} - I_1 \right) + j\omega a L_{x2} \frac{I_2}{a} + \frac{I_2}{a} a r_2 + \frac{I_2}{a} a Z_2 = 0$$

$$X_m \quad L_2 = \frac{M}{a} + L_{x2}$$


$$L_{x2} = \left(L_2 - \frac{M}{a} \right)$$

And is it not the same equivalent circuit we got from physical considerations of a transformer? See r_1 and this is leakage reactance this is the mutual inductance which we denote by X_m . But in terms of M it is a into a M where a is the number of turns ratios N_1 by N_2 and all the impedances on the secondary side is reflected as a square into $r_2 a$ square into ωl_2 and so, on a square into Z_2 .

I will just ask you to find out the equivalent circuit of the transformer referred to the secondary side, I leave it as an exercise to you that is how this equivalent circuit will look like if I want to draw it with respect to this side 2. Anyway so, we spend some time on this, but I just thought that talking about self inductance and mutual inductance sum two three important points it is better I also say that I am talking about $L_1 L_2 M$.

And then without talking about energy storage and the relationship of $L_1 L_2$ in terms of M it remains somewhat incomplete. So, I what first I will do is this recall that.

(Refer Slide Time: 05:11)

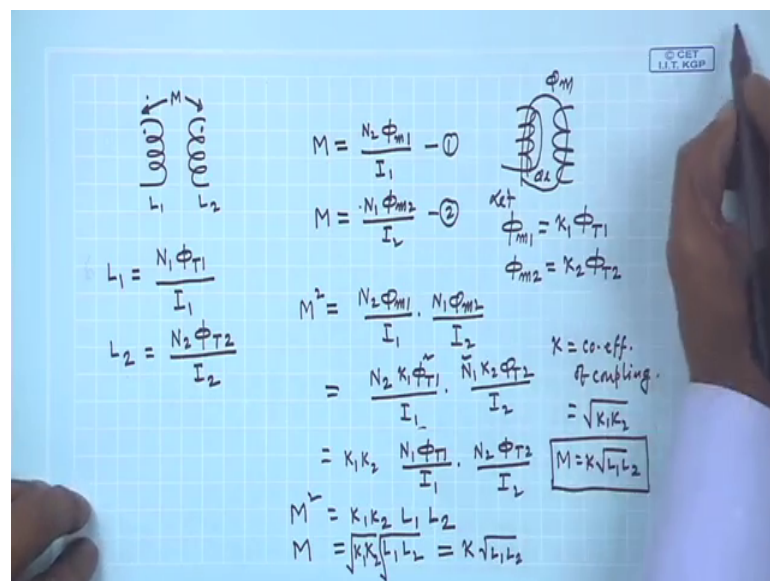

These are the 2 coils having inductances $L_1 L_2$ and this is the mutual inductance M . And we know that M is equal to say M is equal to I can write as $N_2 \phi_{m1}$ by I_1 and this M is also same as $N_1 \phi_{m2}$ by I_2 when the first coil is carrying some current flux linkage per unit ampere and so on.

Now, this fluxes which is mutual flux here this is ϕ_m and these are the leakage flux path ϕ_l . Generally if the coils are very tightly coupled then leakage flux will be little;

in fact, for a transformer coupling should be made very high. So, that most of the fluxes are mutual fluxes and recall that L_1 was defined as N_1 into ϕ_{T1} , what is ϕ_{T1} ? Total flux sum of leakage and mutual flux ϕ_l and ϕ_m divided by I_1 and I_2 was denoted by $N_2 \phi_{T2}$ divided by I_2 .

Now, this mutual flux will be can be expressed suppose let ϕ_m is K_1 into ϕ_{T1} out of the total flux what percentage is your mutual flux? For a transformer it could be 98 percent 97 percent of the total flux leakage flux is little. So, K_1 represents that similarly ϕ_m is K_2 into ϕ_{T2} . Now what I do with these 2 equations? We just multiply them so that it become M square into $N_2 \phi_m$ by I_1 into $N_1 \phi_m$ by I_2 .


Now, you just rearrange the not rearrange now what you do? For ϕ_{M1} it is certain percentage of total flux ϕ_{T1} by I_1 into $N_1 \phi_{M2}$ is $K_2 \phi_{T2}$ by I_2 is not then you write it in this way $K_1 K_2$ you take. And then you write it this terms can be arranged such that it is like this that is you take $\phi_{T1} N_1$ together.

And then $N_2 \phi_{T2}$ by I_2 , but this is nothing, but self inductance. So, $K_1 K_2$ into L_1 and L_2 this is L_1 and this term is L_2 . So, M square is this 1 and this K_1 into K_2 is called coefficient of coupling not really that. So, $K_1 M M$ then will be $K_1 K_2$ square root of that and square root of that. Now, this is expressed as K into root over $L_1 L_2$. So, K is called the coefficient of coupling which is equal to root over $K_1 K_2$.

What is $K_1 K_2$? K_1 is the how Much of this total flux; it is the number fraction maybe 0.95 0.98 for a very tightly coupled coils. And if its value is small it means it is weakly coupled coil if it is 0.5; that means, 50 is mutual flux and 50 percent is leakage flux. Anyway so, this is a relationship which one should know when one is talking about the self and mutual inductances.

The second thing I thought I must touch upon is the energy storage in a mutually coupled coil.

(Refer Slide Time: 10:45)

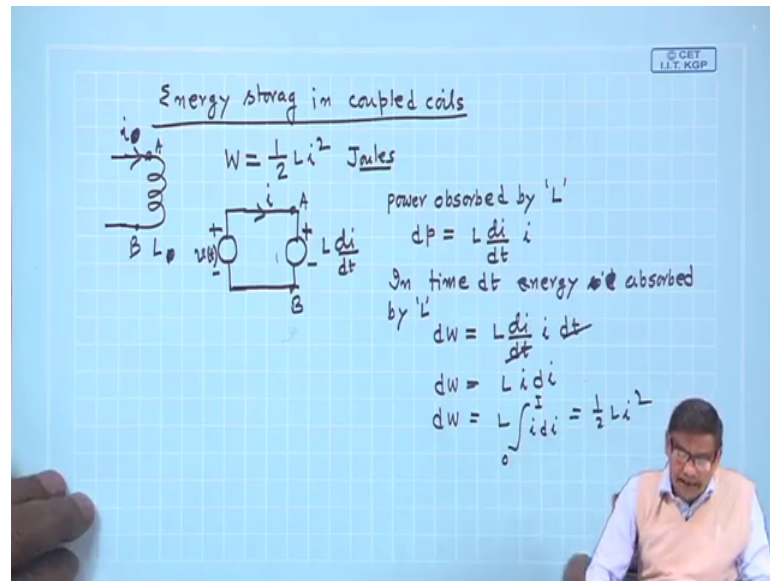

It will take few steps energy storage in coupled coils. The thing is if we have a single coil and it has got self inductance L 1 and this is suppose you are passing some current I 1 through it I because no point in taking telling about L 1 L 2.


Suppose a single coil it has got a inductance l and when it carries a current I we know that energy storage is half Li square so much joules provided l is in henry, I is in ampere and this is denoted by this. So, this is the and how do you get it? Very simply it is like this since this is L this is i . So, as I told you it is better to represent this as a voltage drop.

In this way $l di dt$ is the voltage is not it and here is your say supply voltage which causes this current to flow in this way. Now as you can see with respect to source current is leaving the positive terminal. So, energy or power is supplied by the source and instantaneous power supplied is v into i similarly when you come to this inductor whose terminals are A and B here.

This is also A and B the polarity of the voltage across the inductor this is plus, this is minus $L di dt$ and current is entering through the positive terminal means that it is absorbing power. So, source is delivering and it is absorbing now power absorbed by L is dp is equal to voltage across it into the current i current i . Suppose in time dt energy supplied energy absorbed by L is let us call it dW and it will be $L di dt$ into I into dt this dt you can cancel out because they are not equal to 0, but very small.

So, $L \frac{di}{dt}$ therefore, you are change if you are changing the current from say 0 ampere to some certain ampere I it will be 0 to $I \frac{di}{dt}$ and that gives you half $L I^2$ a very familiar results you know that now let us see what happens how do you calculate the energy storage in a coupled coil.

(Refer Slide Time: 14:43)

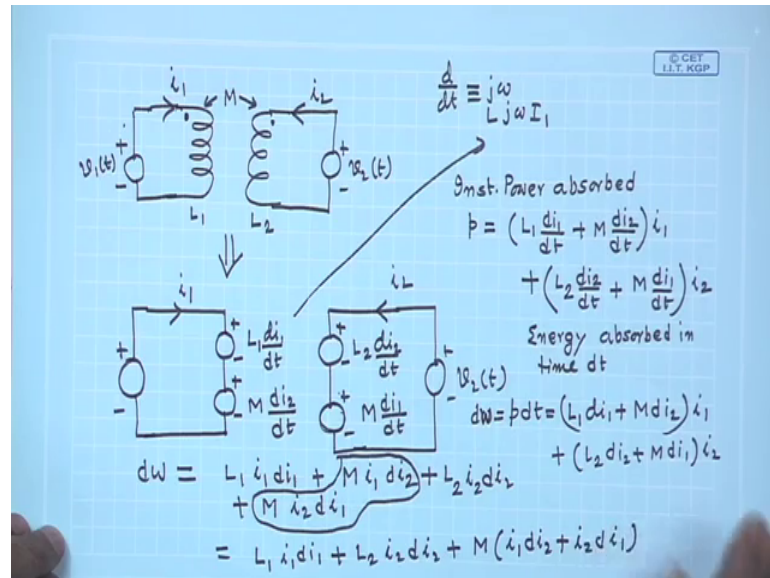

So, we take in the same way these two coils; suppose these are the dots and here I will connect 1 source and let us assume this coils has got negligible resistance almost ideal coil. So, here you connect a source $v_1(t)$ and current absorbed by this coil is i_1 similarly you imagine you have connected another source $v_2(t)$ here and its current direction is like this.

You can choose the current direction in which ever direction you please, but I have just assumed like that i_2 . Now, you see in this system so, these 2 coils are mutually coupled having mutual inductance M and self inductances L_1 L_2 . Now, to understand how energy is observed in it what I will do? I will translate this diagram to because between these two points there will be two sources of emf this is 1 this is another, it will also help you to repeat those steps correctly.

So, for example, here there will be one voltage plus minus i_1 is this current. So, for self inductance this is the source $L \frac{di}{dt}$ is not. Similarly, for the current in the second coil there will be induced emf here and what will be the polarity? Through the dot it is entering. So, dot will become plus that is the upper side; so, this is plus minus $M \frac{di_2}{dt}$.

In our earlier case I assume the supply source to be sinusoidal and then what I did for $\frac{d}{dt}$ you just replace it by $j\omega$ then you will get $L j\omega I_1$ this term. If the supply happens to be sinusoidal, but in time domain this is fine polarity is like this. Similarly for the second coil there will be two source because between these two points self inductance exists and it has got a coupling with the first coil.

So, so, far as i_2 is this direction and this is your supply voltage mind you $M \frac{di_1}{dt}$ plus minus. So, i_2 is entering through. So, this will be $L_2 \frac{di_2}{dt}$ self inductance and plus mutual inductance will be $M \frac{di_1}{dt}$; now we have to decide where to write plus minus. Now see through the first coil i_1 is entering through the dot.

Then because of mutually induced voltage in the second coil it should be $M \frac{di_1}{dt}$ with upper side plus that is the thing. So, once this is correctly drawn then calculations of instantaneous power and from that energy becomes very simple why? See there are now two sources and so, far as this part is concerned current is entered into the positive here power is absorbed and about these two sources also power is being absorbed.

Sources means their inductances; coupled inductances. So, we write instantaneous power instantaneous power absorbed mind you absorbed because both these coils are absorbing power who decides that? Because I have assumed the currents in such a direction polarity of the voltage is given. So, I can make out whether this fellow is absorbing power or not. So, this is plus minus at the voltages current is entering through the plus it is absorbing.

So, so we write instantaneous power will be then voltage across the this coil first coil plus $M \frac{di_2}{dt}$ this is the voltage between these 2 points into i_1 , but this fellow also absorbs power. So, I have to also consider this coil how much power it is absorbing it is $L_2 \frac{di_2}{dt}$ plus $M \frac{di_1}{dt}$ and the current is i_2 this is the instantaneous power.

So, both the sources are as if pumping power into the system the system is L_1 L_2 and M . So, so this is how it looks like then the energy absorbed in time dt which is vanishingly small this calculus type dx dt like that dt . So, it will be in that small time energy absorbed let us write it as dw is equal to pdt . So, multiply with dt and cancel it out. So, it will be $L_1 i_1 \frac{di_1}{dt} + M \frac{di_2}{dt} i_1 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} i_2$. And this we can write it like this as $L_1 i_1 \frac{di_1}{dt} + M i_1 \frac{di_2}{dt} + L_2 i_2 \frac{di_2}{dt} + M i_2 \frac{di_1}{dt}$ this way I can write.

Now, these two terms can be grouped together. So, this is $L_1 i_1 di_1$ and then let me let me write the second last term first that is $L_2 i_2 di_2$ and then this one is $M i_1 di_2 + i_2 di_1$ like this I get it.

(Refer Slide Time: 23:09)

© GET I.I.T. KGP

$$dW = L_1 i_1 di_1 + L_2 i_2 di_2 + M d(i_1 i_2)$$

Total Energy stored when current change from 0 to I_1 in coil-1 & 0 to I_2 in coil 2

$$W = L_1 \int_0^{I_1} i_1 di_1 + L_2 \int_0^{I_2} i_2 di_2 + M \int_0^{I_1 I_2} d(i_1 i_2)$$

$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M I_1 I_2$$

And so dW is $L_1 i_1 di_1$ plus $L_2 i_2 di_2$ and this thing if you look at it carefully this term $i_1 di_2 + i_2 di_1$ can be written as $d(i_1 i_2)$.

So, energy supplied energy stored when current changes from 0 to some current say I_1 in coil 1 and 0 to I_2 in coil 2. In that a particular time interval if current changes 0 to I_1 in coil 1 0 to I_2 in coil 2 then total energy stored will be equal to L_1 this is 0 to $i_1 di_1$ plus L_2 0 to $i_2 di_2$ and plus $M d(i_1 i_2)$.

And what should be the limits? Limit should be 0 to $i_1 i_2$ because this is the differential thing if it is dx limit of x is $i_1 i_2$. So, it was 0 $i_1 i_2$ was 0 initially and finally, it has reached $I_1 I_2$. So, product so, if you calculate this it will be half $L_1 I_1^2$ plus half $L_2 I_2^2$ sorry I_2 square and plus M into $I_1 I_2$. So, the energy stored in a coupled coils when it carries some current I_1 and I_2 is given by this.

So, this in this you need to what I have done is I reviewed very briefly in the last lecture I will request you you pause the videos of the last three units very carefully and try to understand the main points that is how to tackle mutually coupled coils with confidence and today what I have done in this unit is I just highlighted two things.

One is about the coefficient of coupling what does that mean? How they are related that is M can be expressed as coefficient of coupling and $L_1 L_2$ that I have done. And to test complete this is self mutual inductance the energy from the energy point of view I know that if an in a single inductor is carrying some current it stores energy what happens if it is a mutually coupled coils how much energy will be stored in that.

So, I found out that also and remember to do this these are the best way to do given two mutual couple coils $b_1 b_2$ both the sides I am. So, these two sources are pumping power into the system the way I have assumed currents and voltage polarities it means that it is pumping energy. There is no resistance in the coil where that energy is going? That energy is being stored in the magnetic field. And how to get that? Whenever a coil is there it can be represented by two sources after all flux linking is also taking place in the coil $M \frac{d\phi}{dt}$. So, some voltage is induced in the coil this voltage is being balanced by the supplied supply voltage that is different.

But when it is a mutually coupled coils i_1 wherever is entering irrespective of the dot plus will be which side i_1 is entering that we know $L_1 \frac{di_1}{dt}$. Now here comes the importance of dot if i_2 is going like this $M \frac{di_2}{dt}$ will be definitely there another source of emf that, but the polarity of that voltage will be through the dot i_2 is entering.

Here also the dot will become plus that is the upper side will become plus like that I do this and then instantaneous power from instantaneous power you get elemental energy integrate it appropriately to get the final energy stored expression.

Thank you.