

Electrical Machines – II
Prof. Tapas Kumar Bhattacharya
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture – 81
Complete Phasor Diagram and Expression for Complex Power

So, welcome to the next lecture and you know last time we were trying to find out what is the total power delivered by a synchronous generator whose terminal voltage is $V \angle 0$ degree.

(Refer Slide Time: 00:32)

The slide contains the following content:

- Phasor diagram: A circuit diagram showing a voltage source $E_f \angle \delta$ in series with an impedance Z_s . The terminal voltage is $V \angle 0$ and the current is I_a .
- Equations:

$$\vec{A} = A \angle \theta \quad A^* = A \angle -\theta$$

$$\vec{I}_a = \frac{E_f \angle \delta - V \angle 0^\circ}{Z_s \angle \beta} = \frac{E_f}{Z_s} \angle \delta - \beta - \frac{V}{Z_s} \angle -\beta$$
- Text: "Calculate complex power delivered by the source."
- Equation for complex power:

$$\vec{S} = 3 \vec{V} \vec{I}_a^* = 3 V \angle 0^\circ \left[\frac{E_f}{Z_s} \angle \beta - \delta - \frac{V}{Z_s} \angle \beta \right]$$
- Equation for real and reactive power:

$$P_G + jQ_G = \frac{3V E_f}{Z_s} \angle \beta - \delta - \frac{3V^2}{Z_s} \angle \beta$$

And always draw the equivalent circuit like this here, this is E_f and it is generator mode that you also do not forget to write and this is your impedance Z_s and then this is your terminal voltage V and it delivers a current of I_a . And so, this is how I_a can be found out you find out this voltage minus this voltage by Z_s , this will give you current in this direction. And once you get that the complex power delivered by the sources is $3 V I_a^*$ we just did some complex algebra here to get this.

(Refer Slide Time: 01:38)

Calculate complex power delivered by the source.

$$\dot{S} = 3 \bar{V} \bar{I}_a^* = 3 V \angle 0^\circ \left[\frac{E_f}{Z_s} \angle \beta - \delta - \frac{V}{Z_s} \angle \beta \right]$$

$$P_G + jQ_G = \frac{3VE_f}{Z_s} \angle \beta - \delta - \frac{3V^2}{Z_s} \angle \beta$$


$$P_G = \frac{3VE_f}{Z_s} \cos(\beta - \delta) - \frac{3V^2}{Z_s} \cos \beta \rightarrow \text{W}$$

$$Q_G = \frac{3VE_f}{Z_s} \sin(\beta - \delta) - \frac{3V^2}{Z_s} \sin \beta \rightarrow \text{VAR}$$

Now, this of course, will be a complex number and the real power if you write like this the power delivered by the generator real and reactive power I will say that P G real power delivered will be the real part of this and this. So, you find out that $3 E_f V E_f$ by Z_s ; real part of this is cosine beta minus delta very simple. Similarly minus $3 V$ square by Z_s this is also cosine beta; so, real part of this and real part of this.

Similarly, reactive power delivered I will write Q G generator delivers this much reactive power and it will be equal to $3 V E_f$ by Z_s the sin components imaginary part. So, this will be minus I mean sin of beta minus delta and then minus $3 V$ square by Z_s and this will be also sin beta sin beta is that clear. So, this is the a powered real power in watt and this is the reactive power in VAR Volt Ampere Reactor that is delivered by the generator.

(Refer Slide Time: 03:18)

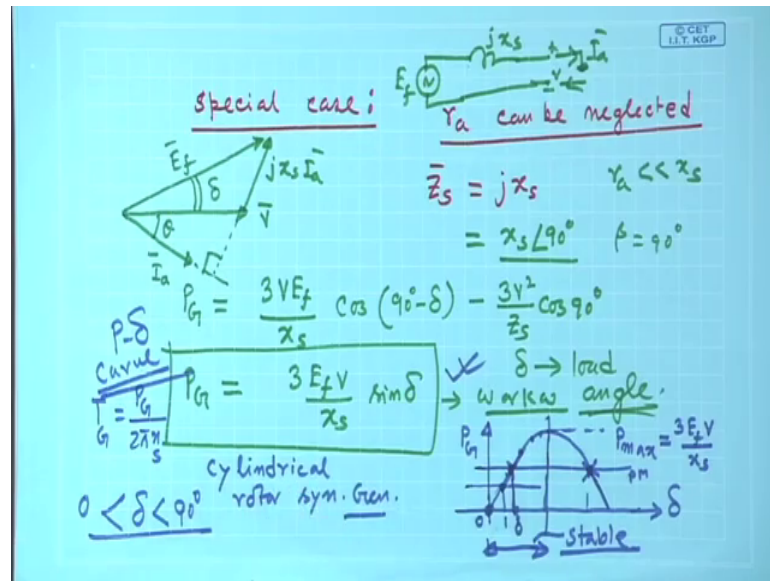

As a special case if: [Soso](#), I am not sure whether you should remember this formula because I do not remember. Anyway for a numerical problem it is better you calculate in this position I get whatever for how many formulas one will remember. But, one thing is certain one special formula is there that one should remember that is a special case.

When we say that r_a can be neglected; r_a can be neglected. If r_a can be neglected; that means, Z_s I am assuming it is Z_s and the reason for this I already told you because of the fact armature resistance r_a is much smaller than x_s . So, that r_a part if you neglect it will be like this.

In this case, then Z_s become $x_s \angle 90^\circ$, is not? So, I will put then for P_G real power output will be equal to $3VE_f / Z_s$ is x_s I will put like this into cosine of beta; beta is than 90° here. So, 90° degree minus delta and then minus $3V^2$ square by Z_s into cosine 90° cosine 90° which will be 0 and this will be equal to $3E_f V / x_s$ synchronous reactance into sin delta that is the thing. This is one of the formula worth the remembering.

What it says that the real power with which we are interested that is watt or kilowatt how much power it is or megawatt how much it is delivering the expression of that it depends upon the excitation voltage, product of excitation voltage and terminal voltage divided by synchronous reactance very easy to remember into sin delta and what is delta? In this case for this particular case, how this phasor diagram will look like? It will be very

simple because in this case I have assumed your equivalent circuit to be E_f your Z_s no r_a . So, jx_s synchronous reactance and here is your V terminal voltage and here is your load current I_a are you getting. So, this is the thing V .

So, in this case, the phasor diagram will look like terminal voltage V that is $V \angle 0^\circ$ and it is delivering suppose lagging power factor current I_a , a load power factor is suppose θ then to V no I_a r_a only thing I_a jx_s you have to add. So, drop a perpendicular here extend this jx_s into I_a it will be here 90° and here is your E_f .

So and here is the angle δ in this case of course, load angle that V is δ . Therefore, the power delivered to the load depends upon the excitation voltage, product of excitation voltage, terminal voltage all are per phase divided by reactance in ohm into $\sin \delta$ where δ is this angle δ as you know is often called load angle sorry. So, this is the expression is that clear. So, this is the thing.

Now, it is the real power mind you this real power whatever is delivering must be coming from the prime mover whoever is driving this, is not? This kilowatt is the real power ok. It is used to buy some consumers. Therefore, this much of power must be supplied by the prime mover. Prime mover in which form energy is spread? If it is a steam turbine we are burning coal; if it is water turbine we are using some potential energy of the water resources; if it is diesel we are burning diesel the amount of coal needed to burn. Now, will become more the moment you start drawing power extract power from the generator or more diesel is to be burned.

So, the amount of real power supplied by the generator decides how much fuel is to be burned to deliver that amount of power. See after all it is a system where I am putting mechanical power and this one. So, this is this similarly I can calculate P_G , but this is most interesting formula. And this curve you can if you sketch it will be like this assign function. These are all for cylindrical rotor synchronous machine cylindrical rotor synchronous generator it will be something like this a sin curve this is δ and this is the real power P_G and this is P_{max} which is equal to $3 E_f$ by x_s ok.

Now, in general when a machine is connected to the infinite bus, V is fixed; you do not have any control over V terminal voltage. However, you can play with E_f to increase the level of power if you increase this P_δ curve will be something like this we will discuss this after sometime, but this is the thing. Now, what is the torque axis? Torque is

nothing, but power I know; in this case there is no copper loss taking place, as if there is no loss in the armature circuit. Whatever power is outputted that much power is drawn in from the mechanical side and a balance operating point will be obtain somewhere here, is not? And speed is always constant.

So, steady electromagnetic torque; electromagnetic torque developed by the machine will be P_G and this is the torque in synchronous what you can say straight away, ~~but~~ But if you divide by that $2\pi n_s$ where, n_s is in a rps you will get the electromagnetic torque developed by the machine. And I will say the prime mover torque is must be also same, but in the opposite direction.

When the machine is operating under no load condition operating point will be here 0. Go on increasing the load, the value of delta will come in at this point it will operate here, at this point it will operate here like that. Can it operate here? Suppose, load is such that delta is this much. So, power and torque is synonymous in case of synchronous machine when you are considering steady state operation ok. Therefore, it is operating at this some delta at this point suppose.


Now, I find there are two operating point. You can easily show that this operating point will be not a stable operating point, why? Because a slight disturbance around this point in delta suppose rotor advances a beat you will find that this is prime mover thing prime mover torque. You will see it will the torque will decelerate the motor just like that and it will come to stop.

So, up to delta equal to 90 degree, this is the stable operating point. Like the induction motor I explain it can be also explained in this. So, P_δ curve is most important curve of a synchronous machine, neglecting r_a , it becomes much simpler like this. And between so, delta general varies between 0 to 90 degree. Of course so, that it does not go near to the delta critical value which is 90 degree because if delta becomes more than 90 degree it will enter into unstable zone and you will not be able to operate this synchronous machine in the unstable zone.

Therefore, delta must be in between 0 to 90 degree typical values of delta may be 10 degree 5 degree 20 degree it should be in this linear zone preferably and well below this unstable zone. So, anyway this curve P_δ curve it is often called is very much useful P_δ curve understood. Therefore, I will come to this curve slightly later once again if I

have done the motor phasor diagram, but the fact is that a very simple expression of power delivered by the synchronous generator if it is operating at some load angle δ can be easily computed provided you know the excitation voltage as well as the terminal voltage ok.

(Refer Slide Time: 15:24)

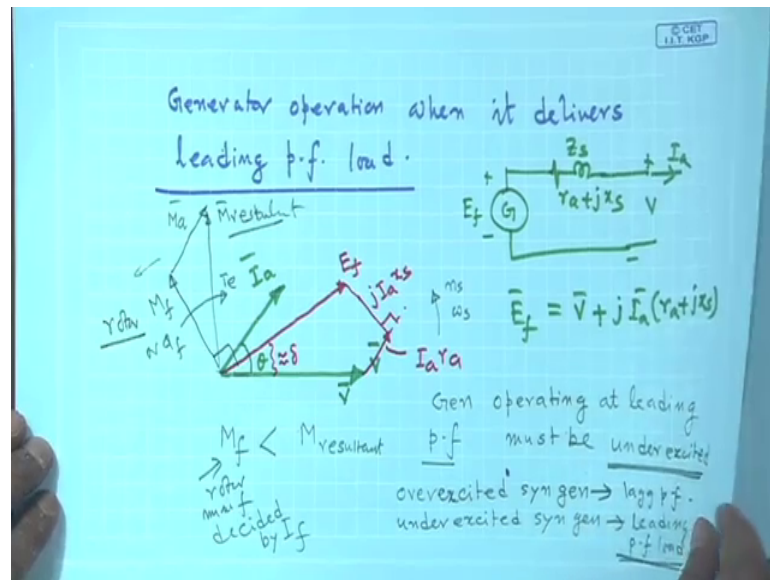

Now, suppose I will just draw for generator operation, I will draw the phasor diagram. Generator operation when it delivers when it delivers leading power factor load; leading power factor load it will be like this. So, how I am drawing generator plus, minus, here is the E_f , here is your Z_s . I will now draw for this whole thing Z_s . This is r_a plus jx_s and this is your terminal per phase voltage V and I am saying it is delivering a leading current.

Now, let us see how to draw phasor diagram. So, this is V and it is leading current. So, suppose this leading current with respect to V is this is I_a follow me carefully, but this equation is true E_f is equal to your terminal voltage plus jI_a into r_a plus jx_s , is not? So, this is what I will do. So, V plus $I_a r_a$ I will add this is small and then to this I must add $jI_a x_s$ such that this angle is ninety degree and this length is much higher than this fellow. So, $jI_a x_s$ I am not breaking up jx al and x ar and then, you will get E_f .

You see this is this one is your V green one terminal voltage green V and armature current. This is the power factor angle of the load, that is there and this angle between these two will be close to the δ E_f and because V will be equal to E_r we have seen

[FL]. Now, where is your ϕ_f ? ϕ_f is here perpendicular to this red line here will be your ϕ_f or M_f or ϕ_f is not this will be M_f and where is your resultant field?

M_f this is the rotor field; mind you, M_f this is the rotor field which induces E_f then M_f plus your M_a is along this line. So, M_f plus M_a and this will be your M_r , M resultant because M_r do not say it is resultant field. The notations I have used in case of synchronous machine is rotor field is E_f net field is M_r sometimes I am writing, but it is resultant field M_r because M_f plus M_a this is M resultant.

In which directions all the phasors are running? In this direction suppose n_s or ω_s in electric radial ampere second all phasors are moving. In which direction electromagnetic torque is developed it is the rotor field, it is advanced with respect to the resultant field. Therefore, electromagnetic torque must be this way consistent in case of generator operation. Electromagnetic torque is in opposite direction of rotor. All phasors are moving with speed n_s in this direction and this is the thing, but in this case you know to one thing this M_f it depends upon field current excitation. M_f length of M_f will be less than M resultant that is this one resultant action.


And then what should I call? I will call a generator operating action at leading power factor; leading power factor must be under excited. Why under excited because field current decides M_f and that field mmf rotor mmf decided by rotor current, decided by I_f is less than m resultant you can easily see if it is leading power factor and therefore, it must be under excited.

Therefore, we conclude that a synchronous machine operating as a generator if it is delivering leading power factor load then it will be operating as under excited mode. Under-excitation, over-excitation the idea of that if you have this complete phasor diagram you conclude that whether this rotor field M_f compare the length of the rotor field and the resultant field. If the rotor field length is less than the resultant field it must be under excited we call it. In case of lagging power factor load we have seen that it will be over excited.

So, a synchronous generator if it is over excited it must be supplying a lagging power factor load. So, over excited synchronous generator over excited earlier we have seen that over excited synchronous generator supplies lagging power factor; lagging power

factor load. Under excited synchronous generator will supply leading power factor load, is that clear? Therefore, this is how this can be done.

(Refer Slide Time: 23:33)

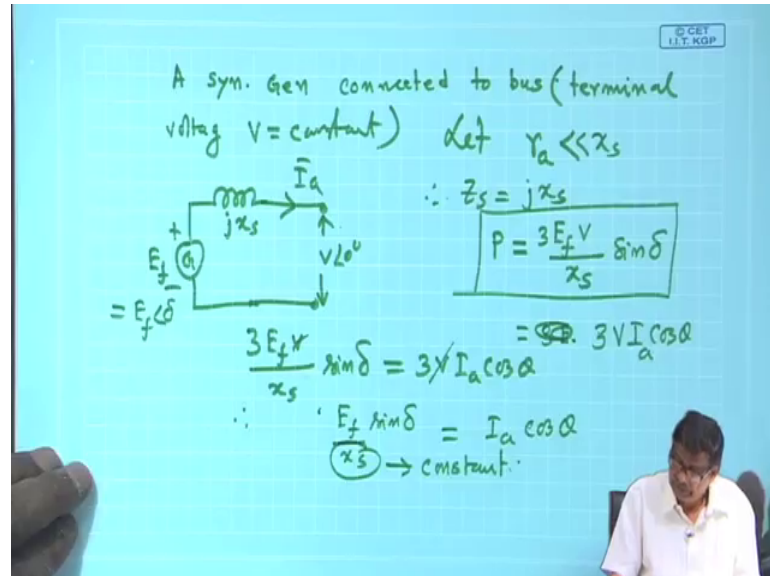


Now, what I will do whatever time is left that we will see we will consider now asynchronous generator; a synchronous generator connected to infinite bus connected to bus; means terminal voltage V is constant I cannot change that. And let for simple understanding of the what is going on the phenomena that I am going to discuss it will be much easier because after all r_a is very small compared to x_s .

Therefore, Z_s is equal to only jx_s pure reactance. So, under this condition just this is the generator mode this is plus minus E_f and here is your bus V which is 0° and it is delivering a current I_a and this is jx_s is not and under this condition we know power delivered by the generator and this E_f is $E_f \delta$.

So, always take the terminal voltage which is constant as your reference, so, 0° . So, P is equal to we have already seen $E_f V$ by $x_s \sin \delta$ very simple relationship ok. So, this is the thing, but it is also true this real into 3, per phase it was like that. It is also true this thing is $3 E_f V$ no. $E_f 3 V I_a \cos \theta$, is not? So, what I am telling is $3 E_f V$ by $x_s \sin \delta$ must be equal to also $3 V I_a \cos \theta$ from the power factor of the load angle between V and I_a I could also calculate the real power output and that must be same as this why not same quantity is we have connected. So, it will be like this of which

you note that then it will be from both sides V goes and the x_s is constant. So, it will be $E_f \sin \delta$ by x_s is equal to $I_a \cos \theta$. x_s and E_f suppose x_s is constant.

(Refer Slide Time: 27:03)

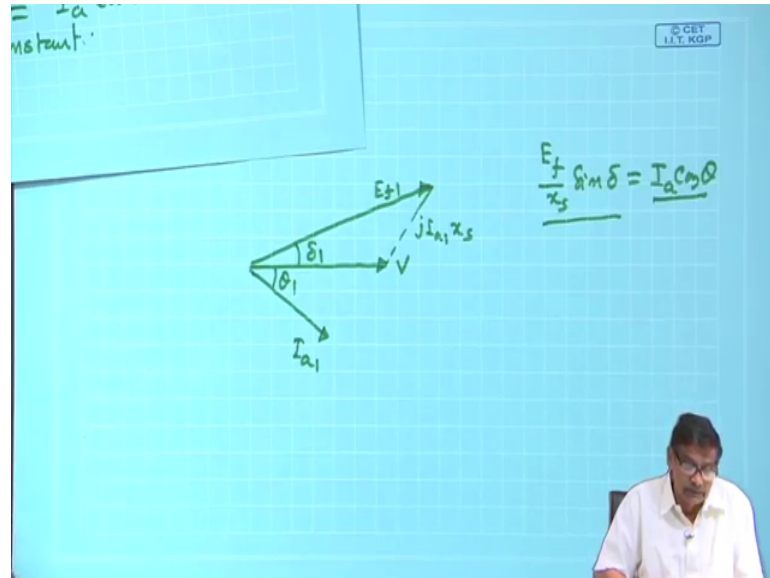

Suppose, the machine is operating at lagging power factor then I will draw it only one thing I will tell and then today I will conclude. It is very, but get the idea this is a post terminal voltage V . Suppose, the generated is operating at some power factor angle θ_1 delivering a current of I_a , is not? So, this is and where is your E_f ? V plus $j I_a x_s$ this will be your excitation, E_f and what is the load angle? δ_1 .

So, we have seen that $E_f \sin \delta$ is equal to $I_a \cos \theta$. Suppose, the real power I am not going to change because they I told you real power means how much fuel you are consuming. I am keeping that fixed I will not allow it to change. It means that whatever real power I am pumping into the system which is held constant and I am not going to change that which we will ensure that output power is also constant in this lossless machine armature copper loss is also not there. Therefore, this conditions must be satisfied.

Anyway, we will continue with this discussion next time. But, please go through this derivation part on your own; this algebraic manipulation in this fashion. Very quickly you can do it. Use calculator you can also try some numerical problems from your books etcetera.

Thank you.