

Electrical Measurement And Electronic Instruments
Prof. Avishek Chatterjee
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 14
Ammeter – II

In this video we are going to talk about multi range ammeters and range changing of ammeters ok, suppose ok. So, before that let me define a term.

(Refer Slide Time: 00:39)

Multi-range ammeters

FSD (Full scale deflection) current

Suppose I have a PMMC meter with FSD current = 10 mA, internal resistance of the coil = 99Ω = R_m

We can connect a shunt resistance to the meter to increase its range

Suppose we want to increase the range of measurement to (0-100mA)

This means the pointer should go to the extreme right when the current is 100mA

100mA should flow through R_s and 10mA should flow through the meter.

$$100_{mA} = I_m = I \times \frac{R_s}{R_s + R_m} = 100_{mA} \times \frac{R_s}{R_s + R_m}$$

$$10(R_s + R_m) = 100 R_s$$

$$R_m = 10R_s - R_s = 9R_s$$

$$R_s = \frac{R_m}{9} = \frac{99\Omega}{9} = 11\Omega$$

So, the term is called FSD a current of ammeter, FSD stands for Full Scale Deflection current ok. So, by this we mean the current that will cause the pointer to move to the extreme; extreme; extreme right hand side extreme position so, that current is called the FSD current. So, if I have a meter the current that so, the current I that causes this pointer to move to the extreme on maximum value ok. So, at this position that current is called the full scale deflection current or FSD current of an meter.

Now suppose I have an PMMC meter with FSD current equals say 10 milliampere and say the internal resistance of the coil is also known to be say take it 99 ohm as an example ok. So, now, if I connect this meter and pass 10 milliampere current through this. So, if I pass I equals 10 milliampere then the pointer will come to the extreme right position here. So, therefore, on this scale I can mark this point as 10 milliampere, this side I can mark as 0 milliampere 0 0 ok. So, this is the 10 milliampere marking on the scale.

Now suppose I want to measure current which is say 100 milliamperes or which is close to say 1 ampere, now can I measure that current with this meter, what will happen if I pass 100 milliamperes current through this meter. Firstly, the pointer will of course, get to its maximum possible position and will get stuck. So, if this is my 10 ampere region 10 ampere marking then if I pass 20 ampere 20 sorry milliamperes current then also the pointer will come here, if I pass 30 milliamperes current then also the pointer will come here, because the pointer cannot move any further.

The meter can also get damaged because of excess current that is a different issue, but also we cannot measure more than 10 milliamperes current directly with this meter, but we can do small alteration in this meter. So, that we can easily measure 100 milliamperes or 1000 milliampere currents with this meter any value of current greater than 10 milliamperes we can measure.

So, what is that alteration so, we have to connect a shunt resistance. So, suppose you want to increase the range of this meter we have to connect a shunt resistance. So, we can connect a resistance in parallel in shunt to this meter. So, we can connect a shunt resistance to the meter to increase its range how?

Because if I connect a parallel path to this meter with suitable resistance or conductance then it is possible that when I pass say 100 milliamperes current through this say if I pass 100 milliamperes current, then maybe a most of it maybe 90 milliamperes will pass through this parallel branch and only 10 milliamperes will pass through the meter and the 10 milliamperes current is good enough for measuring with this meter.

So, we can bypass we can give a parallel route for the excess current to flow through this shunt resistance. Now what should be the value of the shunt resistance or this parallel resistance? So, if I call this R_s , what should be the value of R_s ? Suppose we want to increase the range of measurement to 0 to 100 milliamperes. So, with the actual meter we were able to measure only 10 milliamperes ok, because only with 10 milliamperes current the pointer goes to the extreme right, but now we want to measure currents between 0 to 100 milliamperes it is a larger range. So, then what should be the value of this shunt resistance.

So, basically this means the pointer should go to the extreme right when the current is 100 milliamperes. But the pointer goes to the extreme right when this current is 10 milliamperes;

that means, 90 milliamperes current must be bypassed through this branch R_s . So, therefore, actually we will have so, here the total current will be 100 milliamperes, but only 10 milliamperes is flowing through the meter and remaining 90 milliamperes should flow through this parallel path ok. So, 90 milliamperes should flow through R_s and 10 milliamperes should flow through the meter ok.

So, now, if we know that the internal resistance of this meter is call this is 99 ohm is given call it R_m a meter resistance or call it R_m , m for meter. So, this is the meter resistance and this is R_s and the total current is 100 milliamperes. So, we can write that I_m that is this current meter current only 10 milliamperes. So, this will be given as I this is I 100 milliamperes multiplied by according to the current divider rule we can write

$$I_m = I \times \frac{R_s}{R_s + R_m}$$

$$I_m = 100 \times \frac{R_s}{R_s + R_m}$$

$$10(R_s + R_m) = 100R_s$$

$$R_m = 9R_s$$

$$R_s = 11 \text{ ohm}$$

So, with this value of R_s we can change the range of this meter to 100 milliamperes from 10 milliamperes. Now let us take another example let us continue this problem ok.

(Refer Slide Time: 11:45)

$R_s = \frac{R_m}{9} = \frac{99\Omega}{9} = 11\Omega$

Q. What will be the range of measurement if we choose $R_s = 1\Omega$

$R_m = 99\Omega$

FSD = 10 mA

$V_{AB} = 10\text{mA} \times R_m = 10\text{mA} \times 99\Omega$

$I_s = \frac{V_{AB}}{R_s} = \frac{10\text{mA} \times 99\Omega}{1\Omega} = 990\text{mA}$

$I = I_m + I_s = 10\text{mA} + 990\text{mA} = 1000\text{mA} = 1\text{A} \rightarrow \text{meter range.}$

The diagram shows a meter with internal resistance R_m and a shunt resistor R_s connected in parallel. The total current I splits into I_m through the meter and I_s through the shunt. The voltage across both is V_{AB} .

So, what if so, what will be the range of measurement if we choose say R_s equal to 1 ohm ok. So, now, this is my meter and we know R_m meter resistance is given to be 99 ohm we are connecting a 1 ohm resistance in parallel so, what will be the range of measurement ok? So, now, the full FSD current is given to be 10 milliamperes for this meter it is given here so; that means, when this current is 10 milliamperes the pointer will reach its maximum position extreme right side ok.


And if this current is 10 milliamperes then what is the voltage between these two points call this A and B. So, V_{AB} will be equal to this current 10 milliamperes multiplied by R_m meter resistance which is 10 milliamperes multiplied by 99 ohms so, this will be the voltage between these two points. So, therefore, what will be this current call this I_s shunt current then I_s will be V_{AB} voltage divided by R_s which is known to be 1 ohm. So, this we can write 10 milliamperes multiplied by 99 ohms. So, this is V_{AB} divided by R_s ; R_s is given to be 1 ohm ohm ohm cancels. So, I_s becomes 99 into 10 990 milliamperes so, this is the shunt current.

Now what is this current I ? I is nothing, but this current 10 milliamperes call it I_m meter current plus I_s this is the shunt current so, this is I_m ok. So, this will be 10 milliamperes plus 990 milliamperes is equal to 1000 milliamperes or 1 ampere ok. So; that means, when this current is 1 ampere the meter indicates full scale deflection; that means, the meter range is now or turn to 1 ampere so, this is the meter range ok. So, this is how we can

change the range of an ammeter and therefore, we can actually if you have a meter with FSD current 10 milliampere we can measure any current larger than 10 milliampere by using suitable shunt resistance.

Now suppose you all have seen maybe in your lab ammeters which has multiple range which has say multiplied terminals and depending on the range of current that you want to measure you connect the wires all across the suitable terminals or it may have some knob with which you can change the range of measurement, how is that done.

(Refer Slide Time: 15:49)

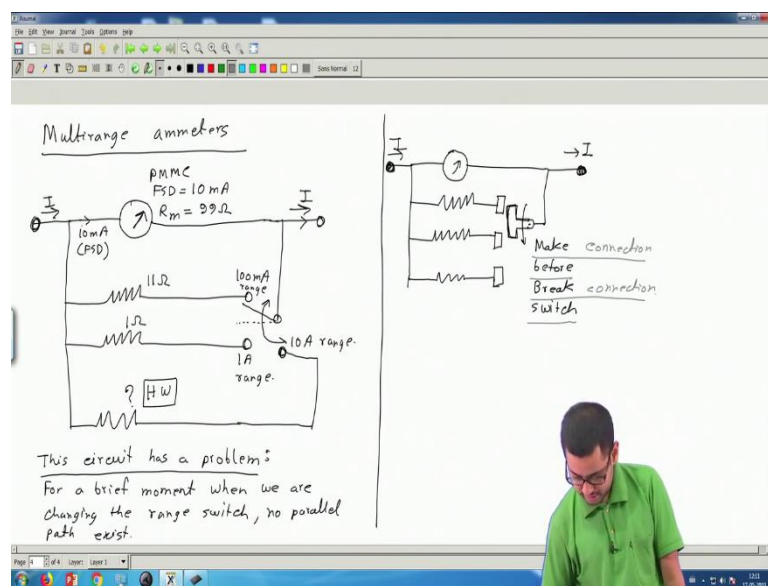

Basically so, let us talk about multi range ammeters ok. So, what we can do we can take meter say this is a PMMC meter with FSD say equal to take the same value as before 10 milliampere and R_m meter resistance or call resistance equal to 99 ohm. Now if we connect say 11 ohm resistance ok, then as we have seen when this current is 10 milliampere; that means, we have full scale deflection then this current becomes 100 milliampere.

And if you had used at different resistance so, let me disconnect it and let me connect say different resistance and say if this is 1 ohm then when this. So, if I connect this like this, then when this is 10 milliampere this will be 1000 milliampere or 1 ampere so, this will within 1 ampere. So, now, we can use a switch to change between this resistances so, what we will do, we will take a switch which you can either connect to this resistance or this resistance and depending on where you connect your mail at range of the meter will

change. So, if I connect it here so, this is this point I mark it as 100 milliamperes range and this point this position is for 1 ampere range so, this is a multi range ammeter ok.

So, we and we can connect more resistances if we need higher ranges. So, if I need say another range of say 10 ampere what will be the value of this resistance ok. So, let me put this as an small exercise for you or homework, find out the value of this resistance if I want to have a 10 ampere range so, this is multi range ammeter.

Now we can have another type of a circuit for multi range ammeters, because this circuit has a small problem what is that problem. The problem is suppose I am measuring some current which is flowing which is I and I and then during the measurement I find that the chosen range is not suitable therefore, I am changing the position of this switch ok.

So, let me draw this here so, I can change the position of this switch. So, I can connect it here or here or here, but you see that when I change the range say I change the range from here to here 100 milliamperes to 1 ampere. Then for a brief moment when the key is moving when the key is here the this is connected neither to this resistance nor to this resistance. So, this path is completely open so there is no parallel path for a brief moment when I am changing the switch position. So, for a brief moment when we are changing the drain switch no parallel path exist.


So, therefore, this path gets disconnected for a brief moment and then the entire current should or must flow through the meter through the meter only and this current maybe is a of a higher value than the FSD current or the allowable current through the meter and then the meter may get damaged, because for a brief moment there is no parallel path ok. So, the meter may get damaged due to high current in this brief a brief period of time ok.

So, one solution is this so the solution is very simple one solution is this if I so, use a different type of switch which is called a make before break switch. So, these two are the terminals of the meter through which the unknown current I should entered and leave. And now see that the switch is so, that it when it is connected to this it is ok, but then when I am changing from here to here, this will touch this resistance first before it disconnects from this is a switch ok.

So, this is schematic diagram so, basically this is a flat I mean longer switch. So, that this touches the new resistance first before getting disconnected from the previous resistance.

So, this is called a make before break switch ok. So, we can say also so, this is like make connection before break connection switch. So, this is one solution so, this is a one solution. Another solution is called art on shunt so, let me so, another solution another circuit which is like this.

(Refer Slide Time: 25:35)

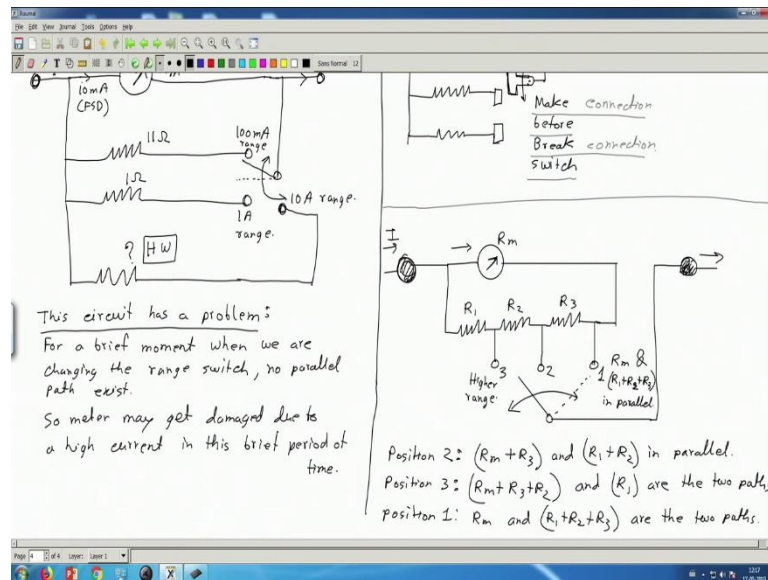

So, if I have my meter with internal resistance R_m I will connect a set of resistances like this and then so, now. So, I have a set of resistances call them R_1 R_2 R_3 this as registers R_m this is the meter the call resistance and I have a switch this can connect either to this terminal or to this terminal or to this terminal. So, this is a switch and this is the final inlet and outlet of the meter.

So, now say if I connect the switch to position 1 call this position 1 if the switch is here ok, then the current that enters I will get distributed in 2 hubs, one goes through the meter like this ok. So, it comes like this and goes out another half goes through the set of resistances R_1 R_2 and R_3 and then goes out so, now, we have so, for this position we have R_m and R_1 plus 2 plus R_3 in parallel ok. So, part of the current goes through this 3 resistances and the part goes through the meter ok, now this is for position 1.


Now for position 2 so, for position 2 if I connect this switch here; so, I have this R_m and R_3 in series so, part of this current goes through R_m and R_3 like this ok, R_m then R_3 like this and part of the current goes through R_1 and R_2 and then out ok. Then so, for position 2 I have R_m and $(R_m + R_3)$ and $(R_1 + R_2)$ in parallel this is a position 2 and

for position 3 see if I connect this switch here then I have R_m , R_3 and R_2 in one path and R_1 in the other path ok. So, I have $(R_m + R_3 + R_2)$ this is one path and R_1 alone so, these two are the 2 paths ok.

So, let me also write for position 1. So, for position 1 we have R_m alone and 1 2 3 together so, these 2 are the 2 parts ok. So, you see that if I connect this meter to position 3 then the shunt path or the parallel path parallel to the meter is of a lowered resistance value compare and this or the other path meter path has $(R_m + R_2 + R_3)$. So, if I connect it here more current is bypassed so for position 3 more current is bypassed from the meter.

So, this is a higher range so, position 3 is higher range and position 1 if I put this switch here then the shunt resistance is now higher $(R_1 + R_2 + R_3)$ compared to R_m which is alone ok. So, this for this position more current goes through R_m less comparatively less current goes through the parallel path. So, this will be a lower range. So, this is the lower range.

(Refer Slide Time: 31:57)

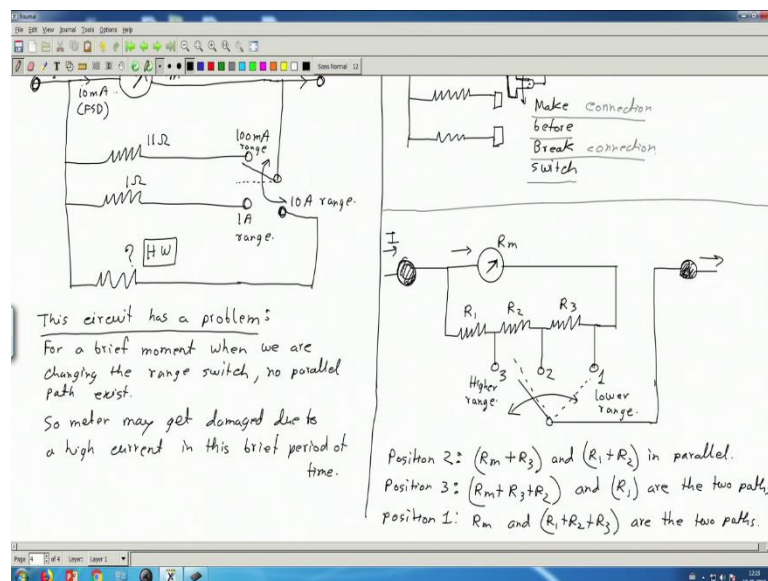

Now so, this is another arrangement and observe that when I change the position of the switch ok. Then even if the which is say somewhere in between it is not connected to any other of terminals no problem I am no problem from the perspective of the meter, because then the circuit is completely open there is no path for this current to flow at all. So, the meter can never get excess current unlike this situation where if the switch is here it is not touching any of the parallel paths then all the excess current will flow through the meter.

In this case the circuit is broken completely so, the current I will stop when the switch is here between two terminals and therefore, excess current does not flow through the meter. So, from the perspective of meter the meter is more safe so, this is called at an shunt and so, this is another arrangement one can have and one can compute the values of these resistances depending on the required ranges. So, we will take a problem in a tutorial class where we will calculate the values of this ranges of this of the values of the resistances to get suitable ranges ok.

Thank you.