

Electrical Measurement And Electronic Instruments
Prof. Avishek Chatterjee
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 61
Schmitt Trigger (Contd.)

Hello and welcome. We are studying frequency meter, digital frequency meter and so, it essentially counts the number of rising edges or falling edges of a square or rectangular wave, within a pre specified time and if the input signal is not square, then we have to convert it into a square or rectangular wave. Like a sine wave, or triangular wave, is required to be converted into a rectangular wave, before we can count it and for that we need a Schmitt trigger.

Because, we could have used comparator, but comparator will not work if the signal is noisy, but Schmitt trigger will work that is what we have seen, we have seen what a Schmitt trigger does, I mean what is its function, but we have not discussed the circuitry or how a Schmitt trigger is made. So, we will discuss that today using op-amps ok.

(Refer Slide Time: 01:42)

Frequency meter: Schmitt trigger

Schmitt triggers are "wrongly" connected non-inverting or inverting amp.

If at any moment $V_p < V_N$ then $V_o \uparrow$

Therefore $V_N (= \frac{V_o R_1}{R_1 + R_2}) \uparrow \downarrow$

Thus the (gap between V_p & V_N) $\downarrow \downarrow$

It will happen that V_o will increase to a such an extent that the gap between V_p & V_N will be almost zero (Which is called virtual short)

Non-inverting amp.

Note: Op-amp will try to increase its V_o towards $+V_{sup}$ if $V_p > V_N$

See that for $V_p - V_N \approx 0$
 $-V_{sup} < V_o < V_{sup}$
 else if $(V_p - V_N) \geq 0$
 then $V_o = \pm V_{sup}$

So, if you recall once we have mentioned that Schmitt triggers are wrongly connected amplifiers, non-inverting or inverting amplifiers. So, let us see how it works. So, let us start with a non-inverting amplifier. So, this is a non-inverting amplifier, where

a fraction of the output voltage V_o , a fraction of the output voltage is fed back to the inverting terminal or minus terminal and here you give the input call it V_i .

So, input is here and if I call this as say R_1 and R_2 then this voltage which is fed back is of course, $\frac{V_o R_1}{R_1 + R_2}$ this is nothing but the current which flows in this branch multiplied by R_1 is the voltage across this resistance which goes back here.

Now, this is non-inverting amplifier ok. Now, let me just tell you a small observation about the this circuit. So, we know that the op-amp increases it is output voltage towards the positive supply value, if this input; that means, V_P call it V_P call it V_N , if this voltage is higher than V_N , then op-amp will increase it is output towards the positive supply value. So, this is the positive supply voltage and this is the negative supply voltage the rule err note.

So, this has also seen in static characteristic that op-amp in will increase will try to increase, it is output V_o towards V_{supply} positive V_{supply} if V_P is greater than V_N . So, what happens? If, you give say a positive voltage here ok, which is higher than say V_N whatever the value of V_N is at this moment. If, you give a voltage here, which is higher than the value of current value of V_N , then it will increase it is output towards the V_{supply} and if this is increasing then of course, this voltage will also increase, because this voltage is nothing, but V_o multiplied by some constant so; that means, this V_N will also increase.

Therefore, the gap between V_P and V_N will reduce. And, if the gap between V_P and V_N is reducing is going towards 0, then the op-amp will not require to increase it is output towards supply voltage V_{supply} ok. So, so, let me just continue this note ok. So, if at any moment say V_P is greater than V_N ok, then V_o increases towards the positive supply voltage.

So, with this symbol with this short hand I mean V_o increases goes up ok. And, if this goes up then you see this value is V_N , which is same as a fraction of V_o ok.

So, therefore, V_N which is same as a fraction of the output voltage also increases right and thus the gap between V_P and V_N reduces ok. So, gap between V_P and V_N reduces and it will happen that op-amp will increase, it is output V_o to such a extent. So, that the gap between V_P and V_N is almost 0 ok. And, it will happen that V_o will increase to such a extent that the gap between V

V_P and V_N will be almost 0 will be almost 0. In fact, this is what is called virtual shorting between V_P and V_N ok. So, this which is so, which we called before which is called virtual shorting ok.

So, a summary of the story is that, if ever V_P is higher than V_N , then op-amp will increase its output until and unless this point this potential is almost equal to V_P ok. And, then at that value of V_o the op-amp will stay happily ok. Because, then V_P and V_N are equal almost equal and you know that from the static (Refer Time: 09:57) characteristic from an from the ideas almost idea is static characteristic. If, V_P and V_N is almost close to each other; that means, this is V_P minus V_N , if this is close to 0, then output V_o will remain can remain anywhere between these two ranges that is V_{supply} and minus V_{supply} ok.

So, just see that for $V_P - V_N$ close to 0, V_o lies between plus minus V_{supply} ok. So, let me rather write minus V_{supply} less than V_o less than V_{supply} ok. So, this is in this small region, else if $V_P - V_N$ is slightly greater I mean significantly greater than 0. So, if this is sufficiently greater than zero; that means, it is outside the resolution than then, then V_o is equal to plus or minus V_{supply} depending on whichever is higher ok.

So, here what we observe that we are still you once again, because this is very important that if ever V_P is higher than V_N , then output will increase until and unless this potential is almost equal to this potential, when these two will be almost equal then add that value of V_o op-amp will stay happily ok.

(Refer Slide Time: 12:09)

So if $V_p > V_n$ op-amp increases V_o until $V_n \approx V_p$
 if $V_p < V_n$ » decreases V_o » $V_n \approx V_p$

Note at any moment if $V_n < V_p$ then $V_o \uparrow$
 Therefore, $V_p (= \frac{V_o R_1}{R_1 + R_2})$ will \uparrow
 So |gap between V_n & V_p | will increase
 leading to $V_n \ll V_p$
 Then V_o decrease more
 So $\left\{ \begin{array}{l} V_o \text{ will reach to } -V_{sup} \text{ (saturation)} \\ V_o \text{ " " " } +V_{sup} \text{ (saturation)} \end{array} \right.$

Non-inverting amp.
Schmitt trigger.
 V_o can be either
 $+V_{sup}$ OR $-V_{sup}$

So, what is (Refer Time: 12:11) in if V_p is greater than V_n op-amp increases V_o until V_n is almost equal to V_p . Similarly, similarly very similarly if we see this circuit once again, if ever this potential is lower than V_n ok, if ever this potential is lower than V_n . So, in this same statements we can write with a different color, that if at any moment V_n is less than V_n then output will decrease ok.

So, I am writing with a different color and therefore, this value will also decrease. and thus what will happen once again the gap between this V_p and V_n will also decrease because if this is lower than V_n , then output will decrease therefore, V_n will also decrease and thus V_n will come closer to V_p ok.

So, here I write with the red color, if V_n not, V_n ; V_p is less than V_n then op-amp decreases V_o until once again V_n and V_p are almost equal. This is how it works? Ok. So, this is how the equilibrium establishes? You can try to increase this voltage op-amp will also try to increase this voltage and thereby make these two equals.

Similarly, if you try to decrease this voltage op-amp will also decrease this voltage and thereby will make V_p and V_n equal. This is how a how one can understand this non-inverting amplifier.

Now, let us see what will happen, if we change this plus and minus terminals. So, instead of connecting this to plus I connect it to minus and here I connect it to plus. So, then I should also call this, V N and this as V P this circuit is no longer non-inverting amplifier ok. This is called a Schmitt trigger ok. So, how will it work?

So, now, you note that what will happen if say ever $V_N > V_P$ at any moment. So, at any moment if say V N is greater than V P ok, this potential is greater than this potential, then output will decrease towards minus the V supply, then V o decreases towards negative supply voltage ok.

Now, this potential is decreasing. Therefore, what will happen to this potential which is coming from here ok. So, this is not N this is P. This is a fraction of output potential divider rule. So, therefore, V P which is same as $\frac{V_O R_1}{R_1 + R_2}$ will also decrease because V o is decreasing right.

So, if ever this so, we started with the assumption V N is higher. So, if ever this value is higher, then V P will decrease. So, if V N is higher V P will decrease that is what will happen then the gap between V N and V P will increase further. So, gap between V N and V P so, this gap will increase. So, leading to V N becoming more and more greater than V P, because V P is decreasing.

Therefore, V N will become more and more larger compared to V P because V P is decreasing right. So, this gap increases. And, if this gap increases then output will decrease further. So, then V o decreases more and this way it will continue to happen. So, if I start with that V N is slightly. So, this greater than is slightly greater than, slightly greater than V P, but due to this chain reaction you can say loosely speaking. Due to this chain reaction the gap between V N and V P will be more and more V N will become larger compared to V P as time progresses and V o will keep going down towards minus V supply, how long until and unless it hits minus V supply.

So, V o will reach to minus V supply; that means, it will saturate, you know from the static characteristic output cannot go below minus V supply. So, therefore, it will go to only minus V supply. Similarly, if I start with the assumption that V N is ever slightly less than ok. So, let me write it with a different color, if ever V N is slightly less than V P, then V o output will increase and if the output is increasing then this will also increase resulting into that and to the fact that the gap between them will increase further, it will continue to increase. So, this will remain same ok.

So, here then I should write this will become more and more less than and ok. And, in that case V_o will reach to plus V supply, once again saturation ok. So, when you say read this note read all the red colored things together or you read blue colored things together ok.

So, this in this circuit we observe that output will either go to positive saturation or it will go to negative saturation, positive V supply or negative V supply. So, V_o can be either plus V supply or minus V supply, that is the only two stable value that the output can take ok. Now, let us see so, let us continue with this circuit ok.

(Refer Slide Time: 22:19)

Example : $R_1 = R_2 \Rightarrow V_p = \frac{V_o}{2}$
 $V_{sup} = +15V$
 $-V_{sup} = -15V$

If $V_i = 10V$

$(V_o = +15V)$? NO if $V_o = 15V$ then $V_p = 7.5V$ So $V_N > V_p$ $\Rightarrow V_o -ve$ NOT POSSIBLE	$(V_o = -15V)$? YES if $V_o = -15V$ $V_p = -7.5V$ $V_N > V_p \Rightarrow V_o$ is $-ve$ POSSIBLE
$(V_o = +15V)$? YES $V_p = 7.5$ $V_p > V_N$ POSSIBLE whether $V_o = +15$ OR -15 will depend on the previous history	$(V_o = -15V)$? $V_p = -7.5V$ $V_p < V_N$ POSSIBLE

$V_i = V_N = 5V$

$V_o = \frac{V_o}{R_1 + R_2} \times R_1$

Non-inverting amp.
Schmitt trigger.
 V_o can be either $+V_{sup}$ OR $-V_{sup}$

So, now let us take some concrete example. So, let us take an example say $R_1 = R_2$ right. Therefore, this V_p will be half of V_o right. And, say this V supply is equal to say plus minus 15 volts plus 15 volt and minus V supply is equal to minus 15 volt right these two are plus minus 15 volt.

Now, if I write V_i input equal to say 10 volt, what will be the output. So, input is 10-volt output what will be the value of output. So, you know output can be either plus V supply or minus V supply. These are the only two stable values we have seen this in many different through many different logics ok.

Now, let us see is it possible that V supply is equal to plus 15 volt, because it can be only plus 15 or minus 15 let us see whether this plus 15 is correct answer or not ok. So, let us check question.

So, if V_o equal to plus 15, then V_P equal to half of that ok, then if $V_o = 15$ volt, then V_P is 7.5 volt ok. Now, this 7.5 volt is here, which is less than, V_i which is 10 volt.

So, $V_N = V_i > V_P$. So, output must be negative, output cannot be positive. If, $V_N > V_P$ then output cannot be positive. So, the answer is no, this is not possible ok. Now, so, let us check can the output be equal to minus 15 volt yes is it possible let us check.

So, if it is if $V_o = -15$ volt, then $V_P = -7.5$ volt and then V_N , which is 10 volt ok. V_N is 10 volt is greater than V_P fine and if $V_N > V_P$ then V_o should be negative ok. So, V_o should be negative yes V_o is negative. So, this is possible answer is yes. So, this is possible. So, this is the answer, but this is not possible, because in this case when V_N becomes V_P this implies output should be positive, but sorry output should be negative, but output is positive. So, this is not possible ok. So, this is the answer.

Now, let us take another case where input is V_i or which is same as $V_N = 5$ volt ok. Now, let us ask is $V_o = 15$ volt possible ok. Let us check, then if V_o is 15 volt, then V_P is 7.5 and in this case $V_P > V_N$, because V_N is 5 volt. So, output should be positive. So, it is possible yes.

So, output can be plus 15 volt ok. So, this is possible, this is correct. Now, let us check is it possible that V_o is equal to minus 15 volt is it possible ok, let us check. If, V_o is minus 15, then V_P should be minus 7.5 and then V_P is less than V_N , because this is 5 volt and this is minus so, this is less than.

So, output should be negative and yes, the output is negative. So, this is also possible, surprisingly this is also possible you see. So, both are possible both are correct answer. So, this is possible, this is also possible. So, output can take both the values plus 15 or minus 15, when the input is 5 volt, but the output cannot take two values at the same time. So, which value will it take that will depend on the previous history ok.

So, so, whether V_o equal to plus 15 or minus 15 will depend on the previous history ok. Now, I request you pause the video at this moment or even close it and think about it what is happening I mean there are two answer possible just think and convince yourself for a while and then come back ok.

(Refer Slide Time: 30:05)

ANS: V_o becomes +ve on when $V_N (=V_i) < V_P$
 \Rightarrow to make V_o (+ve) we have to decrease V_N or V_i
 How much to decrease?
 $V_o = -V_{sup} \Rightarrow V_P = \frac{-V_{sup} R_1}{R_1 + R_2}$
 therefore V_N should be lower than V_P or lower than $\frac{-V_{sup} R_1}{R_1 + R_2}$
 $V_i = V_N < \frac{-V_{sup} R_1}{R_1 + R_2}$ ($\frac{-15V}{2}$ when $V_{sup} = 15$ & $R_1 = R_2$)

Schmitt trigger.
 Q Suppose at any moment $V_o = -V_{sup}$ & we can change V_i . What value of V_i will make $V_o = +V_{sup}$?

So, now this is our Schmitt trigger. Let us ask a question. So, the question is suppose at any moment $V_o = +V$ supply, V_o can be either plus V supply or minus V supply. So, let us assume $V_o = +V$ supply at any moment. And, we are changing the input we can change the input ok. So, we can change V_i and we want to make $V_o = -V$ supply. So, the question is what value of V_i will make $V_o = -V$ supply so, this is the question of.

So, now answer so, first observation is that if I want to make a V_o negative, when can it be negative it can be negative only, if this value is higher than this value right so; that means, I have to increase V_i ok. So, let us write V_o becomes negative only when V_N , which is same as V_i in this circuit is greater than V_P . So; that means, to make V_o negative we have to increase V_N or V_i we have to increase V_N or V_i ok.

Now, how much what is the minimum value of V_N or V_i , which will surely make I mean which will make a output negative ok. So, now, how much to increase the answer is as follows? So, you just observe that V_o equal to plus V supply therefore, this point is at a value V supply multiplied by this factor.

So, V_P this value I can write $V_P = \frac{V_o R_1}{R_1 + R_2}$, now V_o we know is equal to V supply. So, here we write V supply right. So, this is V_P and we have to make V_N higher than V_P . So, therefore, V_N

should be higher than or at least slightly higher than V_P or which is same as higher than, $\frac{V_{supply} R_1}{R_1+R_2}$ because this is the value of V_P ok.


So, $V_N > \frac{V_{supply} R_1}{R_1+R_2}$ ok. So, this is what we have to do we have to increase V_N , which is same as V_i higher than this value. If, we increase this higher than this value ok, then the output will become negative. So, for example, if I take this equal to plus 15 and $R_1 = R_2$ then this becomes 15 volt by 2 when V_{supply} is 15 volt and $R_1 = R_2$ for example, ok. So, this is the condition, this is the boundary condition where the output will change I have to increase input by this amount ok.

Now, similarly you can ask the same question that if at any moment the output is negative, how can I make it positive ok. So, let me ask the completely opposite question, copy next page paste ok. So, now, let me ask the completely opposite question that suppose at any moment V_o is negative ok; and we can change V_i the and what value of V_i will make V_o positive ok.

So, answer will be again similar V_o becomes positive only when $V_N < V_P$. So, to make V_o positive we have to decrease V_N or V_i . Now, how much to decrease? So, you just observe that once again this is equal to minus V_{supply} . So, this is minus V_{supply} . So, you have to make V_N should be lower than V_P and; that means, lower than this value ok, this value ok. And, if this is minus 15 volt then this is minus 15 that is as is as it is so, now, what happens let us see. Let us go to the next slide ok.

And, so, let us see how the input and output changes ok.

(Refer Slide Time: 37:32)

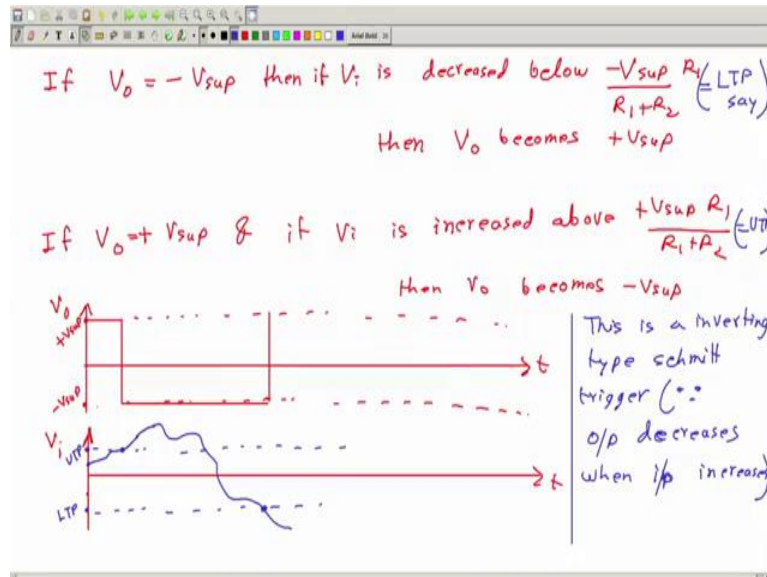

So, if output is equal to is negative, then V_i less than this if V_i is decreased, then if V_i is decreased below this $-\frac{V_o R_1}{R_1 + R_2}$ am I right, yes. If, it is decreased below this then V_o becomes then V_o becomes plus V supply. Similarly, if V_o is plus V supply and if V_i is increased above $\frac{+V_o R_1}{R_1 + R_2}$, then V_o becomes negative ok.

So, suppose let me draw the some timing diagram like this, this is time versus V_o and this is time versus V_i ok. Now, V_i say let us say let us assume that V_o is initially plus V supply, this is plus V supply and this point is minus V supply ok. And, let us call this point on the V_i line is equal to this ok. So, this let me just give you the name ok, because I cannot write this big expression in the small space. So, let me give it a name let me just give it a name LTP call it LTP and this you call as UTP, lower trigger point and upper trigger point ok.


So, here I write this UTP and here I write LTP. The value of LTP is same as this and value of UTP is same as this. Now, you see that if the output is positive and if you increase V_i above UTP ok. Say, if you increase V_i from some initial value we do not know what the initial value is. So, may be here if you increase it, increase it and cross this point, then the output will become negative. So, at this point output will become negative and then it will stay negative as long as you keep the input here or actually as long as you keep it above LTP ok.

But, if you bring the in input below this value; that means, this value like this here at this point output will become positive again. So, this is how it works? This is exactly like a Schmitt trigger right. This is the upper trigger point of a Schmitt trigger lower triggers point of a Schmitt trigger.

The only observation is that it is a inverted Schmitt trigger you can call, because when you see input increases output decreases and here input decreases output increases. So, this is this is a inverted or inverting type Schmitt trigger, since output decreases when input increases ok.

So, this is called a inverting type Schmitt trigger. And, one small fact we have started this by changing the plus minus sign of a non-inverting amplifier. So, if you start with a non-inverting amplifier and change the plus minus sign it becomes a inverting amplifier, inverting Schmitt trigger. So, start from non-inverting amplifier and change the plus minus sign, it will become inverting amplifier just you can note this point ok.

(Refer Slide Time: 43:40)

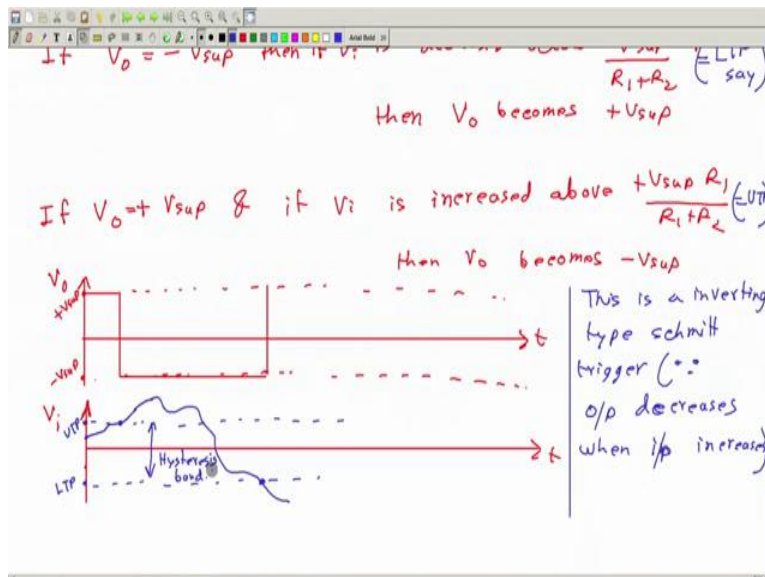

And, this is otherwise just like a Schmitt trigger only thing is that it is a opposite, but there is still a upper trigger point, there is still a lower trigger point and this is the hysteresis band hysteresis band or hysteresis gap. So, this is like a Schmitt trigger, but it is inverted ok.

So, now let us quickly see another type of Schmitt trigger, which is non-inverting type.

(Refer Slide Time: 44:21)

Non-inverting schmitt trigger

Inverting amp

Do the stability analysis yourselves **HW**

Schmitt trigger.

HW Due to chain reaction V_o goes to $+V_{sup}$ or $-V_{sup}$. These are the only two stable values that V_o can take.

$$V_p = \frac{V_i R_2 + V_o R_1}{R + R_2}$$

So, now non-inverting Schmitt trigger ok. And to make the circuit what we have to do we have to start from a inverting amplifier and change the plus minus sign ok. So, we will start say from a inverting amplifier minus plus give a negative feedback, this is R_2 , R_1 , I ground it this is the input, this is what this is inverting amplifier ok.

Before proceeding I request you that you do a stability and equilibrium analysis of the circuit on your own I just tell you very quickly that if ever say this, this is V_N this is V_P , if ever say you increase V_i which will cause V_N to increase ok. So, if ever I just give some symbols, if V_i is increased then of course, V_N will also increase because V_N is some sort of average of this V_i and V_o . So, if you increase V_i then output then V_N also increases and if V_N increases this is at 0, if V_N is trying to increase output will try to decrease right, because negative input is increasing. So, output will decrease.

Now, if output is decreasing this will cause V_N to go down right. So, you are increasing V_i and op-amp is decreasing V_o . And, therefore, you are trying to increase V_N op-amp is trying to decrease V_N . So, op-amp will increase it is output until and unless V_N is again brought back to the same value as V_P , which is 0 volt ok.

So, I am not writing these details things which I did for the previous 1 due to lack of time, you do it yourself if you need any help I will be happy to assist you no problem ok. So, do this stability analysis yourselves homework ok. So, now, let us start with this inverting amplifier and let us switch this plus minus signs ok. So, I will make this plus with a different color to highlight it and this minus ok. So, now, I should also call this as V N and this as V P right. So, this will become a Schmitt trigger a Schmitt trigger ok.

Now, I request you that you do the stability analysis or equilibrium analysis of this circuit on your own, because we already have done that for the previous circuit. So, I will not write it in detail, but I will just briefly mention. See at if at any moment, if say V P is let me first it is it, say if at any moment V P is higher than V N. Then, what will happen then the output will increase if V P is higher, then output will increase which will cause the V P increase further. Because, V P depends on V o like this,

$$V_p = \frac{V_i R_2 + V_o R_1}{R_1 + R_2}$$

So, if I have V P higher output will increase ok. If, output increases here V P increases further, and if V P increases output will increase even further, and then due to this chain reaction loosely speaking, informally speaking, due to this chain reaction output will keep increasing and will go to positive supply voltage ok, plus V supply. Similarly, if V P is lower at then V N at any moment, then output will decrease which will cause V P to decrease further and with this chain reaction output will go to minus V supply ok.

So, homework you just convince yourself thoroughly that due to chain reaction V o goes to plus V supply and or minus V supply and these are the only two stable values that the output can take that V o can take ok; and so, output can take only these two values. Now, I will request you to play another small game the game is like this.

(Refer Slide Time: 51:03)

Inverting amp
Do the stability analysis yourselves **HW**

Schmitt trigger.
Due to chain reaction V_o goes to $+V_{sup}$ or $-V_{sup}$. These are the only two stable values that V_o can take.

$$V_p = \frac{V_i R_2 + V_o R_1}{R_1 + R_2}$$

V_i	Is $V_o = +15V$ possible	Is $V_o = -15V$ possible
0	?	?
5	?	?
-5	?	?
10	?	?
-10	?	?

So, you take say different values of input make a table like this V_i you choose the value of V_i as 0 volt, 5 volt, minus 5 volt, 10 volt, minus 10 volt etcetera and ask is $V_o = +15$ volt possible yes or no ask this question ok, for all these given values. Similarly, ask is $V_o = -15$ volt possible see is it possible or not and we will see that for some input only 1 output is possible and for other input both outputs are possible ok. Let us see it is a nice fun it is a nice game you just play with this ok, like we did for the previous circuit this time you do it yourself ok.

(Refer Slide Time: 52:12)

Schmitt trigger.

Suppose $V_o = -V_{sup}$.
How can we make $V_o = +V_{sup}$ by changing V_i ?

ANS: To make $V_o > 0$
we need $V_p > V_n$
so we have to increase V_p

$$V_p = \frac{V_i R_2 + V_o R_1}{R_1 + R_2}$$

So we have to increase V_i
How much?
at least $V_p > V_n = 0$

$$\frac{V_i R_2 + V_o R_1}{R_1 + R_2} > 0$$

$$\Rightarrow V_i R_2 + V_o R_1 > 0$$

$$\Rightarrow V_i > -\frac{V_o R_1}{R_2} = \frac{+V_{sup} R_1}{R_2}$$

$V_i > \frac{V_{sup} R_1}{R_2}$

$V_i > 7.5$ if $R_2 = 2R_1$ & $V_{sup} = 5$

Now, let us ask a question that suppose so, the question is suppose V_o is negative at some moment and we can change V_i . So, the question is how we can make output positive by changing input V_i . How can we make $V_o = +V_{sup}$ by changing V_i this is the question of. So, let us see what is the answer?

So, first question is do we have to increase V_i or decrease V_i . The answer is we have so; we want to make output positive, when can the output be positive only if $V_p > V_n$. So, we have to increase V_p ok. And, we can increase V_p by increasing V_i ok. So, to make V_o greater than 0, we need V_p greater than V_n ok.

So, we have to increase V_p right. And, how can we increase V_p ; by increasing V_i , because V_p is nothing but $\frac{V_i R_2 + V_o R_1}{R_1 + R_2}$ ok. So, we have to increase V_i , because if V_i increases then V_p increases, but how much at least as much. So, that V_p becomes higher than V_n and V_n is equal to 0. So, at least V_p should be greater than slightly greater than V_n which is same as 0 ok.

Now, V_p is this. So, let us write $\frac{V_i R_2 + V_o R_1}{R_1 + R_2}$ this should be greater than equal to 0 and from this we this goes away. So, from this we can write $V_i R_2 + V_o R_1 > 0$ from which we write $V_i > -V_o R_1 / R_2$. Now, in case of V_o we can write the current value of V_o which is same as minus V_{sup} this is the current value.

So, it becomes minus minus plus plus $V_{supply} R_1/R_2$ ok. So, this is the condition V_i should be greater than this is the boundary value if I increase $V_i > V_{supply} R_1/R_2$ then output will go to positive value ok. So, this is the condition. So, you can take an example like this is equal to 15 volt and say $R_2 = 2 R_1$ then we have to increase $V_i > 7.5$ ok.

So, like $V_i > 7.5$ if R_1 if $R_2 = 2 R_1$ and $V_{supply} = 15$ volt ok. So, this is an example you can take ok. Similarly, you can ask the same question that if V_o is negative sorry if V_o is positive then what should you do to make it negative ok. So, copy next page paste.

(Refer Slide Time: 57:18)

$$R_2 V_i + R_1 V_o < 0$$

$$\Rightarrow V_i < \frac{-V_o R_1}{R_2} = \frac{-V_{sup} R_1}{R_2}$$

$$LTP = \frac{-V_{sup} R_1}{R_2}$$

Schmitt trigger.
 Q Suppose $V_o = +V_{sup}$.
 How can we make $V_o = -V_{sup}$ by changing V_i ?
 ANS To decrease V_i
 To make $V_p < 0$

So, if this is positive how can we make it negative? So, you see that to make it negative we have to bring this value down lower than 0 and that is possible by bringing V_i down sufficiently. So, answer we have to decrease to decrease V_i now how much at least we have to make it make V_p equal to or sorry less than 0 volt ok.

So, we have to make it V_p to make V_p less than 0 volt which implies V_p is nothing but once again $\frac{V_i R_2 + V_o R_1}{R_1 + R_2} < 0$ from this you can write $V_i < \frac{V_i R_2 + V_o R_1}{R_1 + R_2}$, which is same as let us put the current value of V_o . So, we have to bring it down $V_{supply} R_1/R_2$ ok. So, this is the boundary condition $V_i < V_{supply} R_1 / R_2$. If, you bring it below sorry minus there is a minus there is a minus this minus ok, if you bring it down below this then the output will change ok.

So, very quickly so, this value I will call as lower trigger point LTP = -Vsupply R1/ R2.

(Refer Slide Time: 59:41)

Schmitt trigger.

Suppose $V_o = +V_{sup}$.
How can we make $V_o = +V_{sup}$ by changing V_i ?
ANS: To make $V_o > 0$ we need $V_p > V_N$ so we have to increase V_p

at least $V_p > V_N = 0$

$$\frac{V_i R_2 + V_o R_1}{R_1 + R_2} > 0$$

$$\Rightarrow V_i R_2 + V_o R_1 > 0$$

$$\Rightarrow V_i > -\frac{V_o R_1}{R_2} = \frac{+V_{sup} R_1}{R_2}$$

$V_i > \frac{V_{sup} R_1}{R_2}$ (UTP)

$V_i > 7.5$ if $R_2 = 2R_1$ & $V_{sup} = 5$

$\Rightarrow \frac{R_2 V_i + R_1 V_o}{R_1 + R_2} < 0$

And, this value I will call upper trigger point.

(Refer Slide Time: 59:52)

Schmitt trigger.

Suppose $V_o = +V_{sup}$.
How can we make $V_o = -V_{sup}$ by changing V_i ?
ANS To decrease V_i To make $V_p < 0$ This is a non-inverting schmitt trigger

$\Rightarrow \frac{R_2 V_i + R_1 V_o}{R_1 + R_2} < 0$

$$\Rightarrow V_i < -\frac{V_o R_1}{R_2} = \frac{-V_{sup} R_1}{R_2}$$

$V_i < \frac{-V_{sup} R_1}{R_2}$

$LTP = \frac{-V_{sup} R_1}{R_2}$

Graph showing V_i and V_o vs t . V_i has UTP and LTP levels. V_o has V_{sup} and $-V_{sup}$ levels. Note: V_o increases when V_i increases.

So, now you can do a timing analysis take time versus V_i and time versus output, output can be either V_{supply} or $-V_{supply}$ and V_i on V_i axis mark these two values LTP, which is this and

UTP, which is the negative of this so, this is the UTP. So, mark these two points (Refer Time: 60:33) start with the assumption say output is initially positive here and then input is changing ok.

So, the input is changing when will the input when will the output becomes negative to a for the output to be negative, you have to bring the input below lower trigger point. So, say here it goes down below lower trigger point then the output at this point will go to minus V supply.

And, then say input is again changing when will it make the output positive, the moment when the input goes above upper trigger point. So, say here. So, here output will become positive ok. So, this is how it works and you just see this is just like a normal Schmitt trigger, when input decreases, output decreases, if input increases output increases.

So, this is not a inverting Schmitt trigger this is a normal Schmitt trigger non-inverting Schmitt trigger. So, this is a non-inverting Schmitt trigger. Since, you observe that output increases when input increases and vice versa if input decreases output also decreases. So, this is a non-inverting Schmitt trigger, although we have just started this from an inverting amplifier. So, if you start with an inverting amplifier and switch the plus minus sign it will become a non-inverting Schmitt trigger ok.

Thank you.