

Analog Electronic Circuits
Prof. Pradip Mandal
Department of Electronics and Electrical Communication Engineering
Indian Institute of Technology, Kharagpur

Lecture - 24
Common Emitter Amplifier (Part A)

Dear students, welcome back to our NPTEL course on Analog Electronic Circuits.

(Refer Slide Time: 00:30)



Myself Doctor Pradip Mandal from E and EC Department of IIT Kharagpur. So, today's topic of our discussion it is Common Emitter Amplifier. So, this is a basic amplifier and many of the concepts need to be getting cleared in this amplifier. Some of the prerequisites we already have covered, which are necessary to understand and appreciate the operation of the common emitter amplifier. So, according to our overall plan let us see how we are into the overall plan.

(Refer Slide Time: 01:18)

Page 41

Flow of Discussion (Bottom-up) – Building blocks

- System/ Sub-systems (for specific application)
 - Modules (performing specific tasks)
 - Building blocks (having specific characteristics)
 - Components (devices/circuit elements)
- Week 3:
 - Amplifier models (equivalent circuits):
 - voltage amplifier, current amplifier,
 - trans-conductance amplifier and trans-resistance amplifier.
 - Cascading of multiple amplifiers.
 - Common emitter (CE) amplifier
 - operating principle, biasing, analysis and design.
 - Common source (CS) amplifier
 - operating principle, biasing, analysis and design.

So, in the overall flow, we are in week 3 and in the previous day we have discussed about the amplifier models, voltage current amplifier trans-conductance, trans impedance and so and so. And, then we also have a plan to cover cascading multiple amplifiers, but we will be covering after we consider some of the practical circuits like common emitter amplifier and common source amplifier.

So, today's main discussion here it is the common emitter amplifier and it is a working principle, biasing scheme, then analysis, may be some part in case if time permits we can cover some design also today or maybe next day. But, I must say that so far whatever the topics we have covered namely the device model and then methodology of analyzing non-linear circuit, then the notion of small signal and large signal model of the BJT and maybe MOS, those concepts it will be frequently used.

In fact, while we have explained about this small signal model of BJT or MOS. We have discussed some extent about the operating principle of the CE amplifier. So, we may not be going detail of or rather we will not be repeating, whatever we have discussed in the circuit operation, rather our primary focus it will be on biasing and then the corresponding analysis.

(Refer Slide Time: 03:16)

CONCEPTS COVERED

Concepts Covered:

- Operating principle
- Biasing: *Fixed bias*
- Analysis: *Operating point and Small signal*
- Issue in *Fixed bias CE amplifier*

The slide features a dark blue background on the left with the text 'CONCEPTS COVERED' in yellow. The main content area is yellow with a blue border. A presenter is visible in the bottom right corner. The Windows taskbar is visible at the bottom of the screen.

So, what are the concepts we are going to cover today? It is the we will start with the operating principle of CE amplifier, but again as I said that we will not be going very deep into that. And, then main thing is that the biasing of CE amplifier.

In this course primarily we will be covering 2 types of biasing of BJT amplifier; one is fixed bias and, then subsequently you will see that, what may be a better option. And, then in the

fixed bias CE amplifier we will see that, how we find the operating point and then how do we get the small signal model and small signal analysis.

And, then we will be covering the what are the issues are there particularly a very common issue it is called D c operating point is very sensitive to beat our transistor. So, as a result in case if you are replacing a transistor by another one having different beta then it is operating point completely gets shifted elsewhere, or in if the beta may not be changing due to replacing the device it may be due to temperature effect.

And, due to maybe higher temperature beta will increase and then that directly affects the operating point of the common emitter amplifier. So, that issue we will be discussing and then we will be giving a pointer what may be a better option or the solution of that problem ok.

(Refer Slide Time: 05:09)

Basic operation of CE amplifier

- **Normally, it is considered as a Voltage Amplifier**
 - Input is fed at the Base node
 - Output is observed at the collector node
 - Both, input and output signals are voltage

The diagram shows a common emitter amplifier circuit. The base is connected to ground through a biasing network. The collector is connected to Vcc through a resistor Rc. The output is taken from the collector. Handwritten annotations include 'I/P' at the base, 'O/P' at the collector, and 'Vout' with 'DC + AC' next to it. A small video inset shows a man speaking.

So, yeah so, what we have the CE amplifier again we will be just touching the basic operation, but before that I must say that, whenever we call the common emitter amplifier. the input it is fed at the base of the BJT and then output it is observed at the collector node. So, you can see that the input we are feeding here and then output we are observing at the collector node.

And, whenever you are considering signal at the input and output terminals normally, the signals we are considering in the form of voltage. It is possible to consider input signal in the form of current as well, so likewise output also can be considered as current ah. So, this same CE amplifier it may be considered as the current amplifier or trans conductance amplifier or trans impedance amplifier, depending on our specific interest, but predominantly unless otherwise it is stated this CE amplifier it is considered as voltage amplifier.

So, what does it mean is that as I said that both input and output signals are voltage. So, whatever the analysis will be doing now is basically from considering that the signal will be will be feeding in the form of voltage. Namely, the signal source resistance thevenin equivalent resistance we want it should be as small as possible, and while we will be observing the output we may not be loading the circuit by any you know load at the output and namely parallel resistance at the output. So, that it need to be taken care.

And, now let us see how we proceed at the input you can see that the while we are feeding the signal, it is also accompanying a DC voltage. And, while you are observing the output this output may be having a DC part as well as the AC part.

So, probably the AC part we can extract we can block the DC by a capacitor or the output, but typically getting a signal source having a appropriate or having a meaningful DC voltage is most of the time it is not possible and feasible. So, whatever the input port we are considering here namely the signal small signal source in series with DC voltage and that DC voltage should be appropriate for the BJT, may not be you know you should not be expecting.

So, it is of course, it is having some practical circuit. So, we will be covering we will be discussing about the practical circuit. And, also the voltage amplifier parameters and any voltage gain and input resistance, those parameters values are very strong function of the bias condition or the operating point of the transistors. So, designing one amplifier it is very important to consider the biasing concepts, how we get the operating point.

(Refer Slide Time: 09:01)

CE amplifier as Voltage amplifier

- Both, input and output signals are voltage
- Important parameters A_v , R_o and R_{in} are dependent on Q-point

The diagram illustrates a common-emitter (CE) amplifier configured as a voltage amplifier. It shows an input signal source V_s with a series resistor R_s connected to the amplifier's input resistance R_{in} . The amplifier is represented by a diamond symbol with a voltage gain A_v and an output resistance R_o . The output is connected to a load resistor R_L , producing an output voltage V_{out} . A graph on the right shows the output voltage V_{out} as a sine wave over time t . A handwritten note "Voltage Amp" points to the amplifier symbol.

So, let us go little detail of that so, in the next slide we will be discussing that, but here as I say that since you are looking for the circuit as a as a voltage amplifier. Typically, this is a small signal model of the voltage amplifier right.

And, as we can see that this is the boundary of the amplifier. it consists of open output voltage gain A_v . Then also it is having output resistance R_o and then the input resistance of the amplifier, which we have discussed about the these three parameters and significance of

these three parameters in voltage amplifier model. And, these three parameters of course, they are very strong function of the operating point right.

So, this is one important point that while we like to get a voltage amplifier having a good steady gain, we need to keep the DC operating point appropriate. In addition to that, since we are feeding the signal here, signal it is voltage. So, at the input the signal it will be voltage form, which may be having the main equivalent resistance called R_s .

So, likewise at the output while we will be observing the corresponding output, we need to consider only the signal part. And, when you consider signal it is expected that in case if we are connecting in any load, the this load should not be directly affecting the operating point of the circuit.

Otherwise, this load may change the operating point and then indirectly they may change these signal parameter yeah. So, we need to be careful while we are fixing the operating point of the circuit or the biasing of the circuit need to be properly taken care.

(Refer Slide Time: 11:21)

Page 8/11

Basic operation of CE amplifier

- **Basic Operation**
 - Base node must have a d.c. voltage
 - Collector node voltage must be sufficiently high
 - Biasing is an important aspect keeping transistor in active region

So, what we are considering now practical circuit biasing circuit. So, what we have it is the requirement wise as I said that the input, we do have signal which is riding over a DC voltage. In this case we are calling this is V_{be} . So, likewise at the output we do have a DC voltage, so we need to remove those things.

So, just now what I was telling that the to have meaningful operation of the amplifier, we need to keep this transistor in active region of operation right; so active region of operation. So, for that we require a meaningful DC voltage that supposed to bias the base to emitter junction in forward bias condition.

And, likewise at the output it should be having sufficient DC voltage, so that while at the output we do have a signal and the instantaneous output voltage should be sufficiently high even in this critical case, when the signal it is going to the minima.. Even then this junction

base to collector junction should remain reverse bias condition. Otherwise, there will be huge distortion at the output.

So, it is very important that the operating point should remain constant. So, that the gain should be remaining constant and the second thing is that the DC voltage here should be appropriate. So, that the base emitter junction is getting forward biased. And, whatever the bias you do have here for that the DC current, which is DC current collector current flowing through the transistor, which is incidentally flowing through this R_C , then whatever the voltage we are getting here namely $V_{C E}$, that should be so, this is the $V_{C E}$ that voltage should be sufficiently high.

So, that while the signal it is riding over that the instantaneous voltage, even in this critical condition the transistor remains in active region of operation. So, on the what may be the practical circuit let us look into that. So, as I said that biasing is very important.

(Refer Slide Time: 14:10)

Page 12/11

Practical circuit to bias CE amplifier – Fixed bias

- D.C. voltage at the base is defined by V_{CC} , R_B and B-E diode
- Capacitor at input port blocks d.c. voltage of the input signal source
- Capacitor at output port blocks the d.c. at collector node to extract only a.c.

The diagram illustrates a fixed-bias common-emitter (CE) amplifier circuit. It features a DC supply V_{CC} connected to the base of the transistor through a resistor R_B and to the collector through a resistor R_C . The emitter is connected to ground through a bypass capacitor. An input signal source V_s is connected to the base through a coupling capacitor. The output is taken from the collector through another coupling capacitor, with the output voltage V_{out} measured across it. Two graphs are shown: the input graph plots V_{in} against time t , showing a sinusoidal wave; the output graph plots V_{out} against time t , showing an inverted and amplified sinusoidal wave.

So, let us look into the input port, so what you are talking about the ah whatever the equivalent circuit we can see here. And, then after that we will see the output port circuit here.

(Refer Slide Time: 14:30)

CE amplifier – Fixed bias (contd.)

• Circuit at Input port

The diagram illustrates the input port of a CE amplifier with fixed bias. It shows the base resistor R_B connected to V_{CC} and the base-emitter junction. A B-E diode is connected between the base and emitter. The input signal V_s is applied through a source resistance R_s . The equivalent circuit at the input port shows the B-E diode replaced by a DC voltage $V_{BE(on)}$ and a series resistance r_E . The base current I_B is calculated as $I_B = \frac{V_{CC} - V_{BE(on)}}{R_B + r_E}$. The collector current I_C is $I_C = \beta_F I_B$. The output voltage V_{out} is taken from the collector terminal.

So, the input port if I consider, here you can see at the input port we do have we do have this R_B , which is connected to base terminal of the transistor, and base to emitter terminal we do have a diode forward bias diode. So, equivalently I can say that we do have R_B in series with diode. Of course, this diode it will be slightly different kind of normal diode, namely this junction though it is forward biased, but most of the collector currents are coming from the emitter junction. So, as a result the level of current flow here it will be less.

However, if I consider the current and voltage characteristic of this diode ah; obviously, it will be having the exponential relationship. So, for this analysis definitely we can consider this is similar to a normal diode. Now, this diode can be replaced by its equivalent circuit, which is shown here, which is having a DC voltage in series with on resistance of the diode.

The on resistance of the diode here we are representing by r_{pi} it is primarily coming from the π model of the BJT, but for the time being you can consider it is on resistance of a diode and this resistance it is very similar.

Now, once you have say supply voltage and this circuit connected the DC voltage coming here, it is I can say that V_{BE} . So, we can say this DC voltage it is V_{BE} on plus r_{pi} multiplied by this current, whatever the current we do have here call say I_B , I capital B. And, this I_B on the other hand it can be obtained by considering this loop. So, that is V_{cc} minus V_{BE} on divided by R_B plus r_{pi} .

Practically this resistance it is very high in the range of few 100s of kilo ohms to maybe mega ohm. And, r_{pi} on the other hand it is very small; it is value it will be in the range of few kilo ohms only. So, since this is 100s of kilo ohms and this is kilo ohm so, you may ignore this part then from that you can consider the I_B and from that you can find what will be the DC voltage coming. And, that DC voltage it is this DC voltage.

Note that this base current as well as this r_{pi} , typically it is very small. So, this part it may be very small compared to V_{BE} on. So, we can say that this DC voltage it is very close to V_{BE} on, but slightly higher. So, once we have the DC voltage obtain there next thing is that the capacitor ah it is helping for the signal to feed in.

So, we do have this coupling capacitor, signal coupling capacitor, which is coming from in the original circuit there. And so, this signal; signal frequency we assume that it is sufficiently high compared to the cut-off frequency defined by this C and the equivalent resistance coming there, or you may say that the value of this capacitor it is sufficiently large, so that the signal it is directly coming to this point.

So, at this point if you observe the voltage, instantaneous voltage it is having a DC on top of that it is having the small signal. So, it is equivalently it is making a small signal riding over the DC voltage; So, it is riding over the DC voltage.

So, earlier we are having this simple stimulus at the base v_s , but of course, it is an ideal v_s model. Practically, this is how it is obtained by combination of this R_B and C , we are getting a voltage here which is having a meaningful DC and on top of that we are successfully feeding the small signal v_s .

So, we will be seeing that what may be the equivalent circuit of this one later where small signal equivalent circuit, where we may short this capacitor and then this DC voltage you can consider it is the AC ground, and then this DC voltage you can drop. So, for AC signal will be practically will be having this R_B and this r_{π} and then this signal it is also coming.

Since, we are not considering any Thevenin equivalent resistance here this resistance it is 0. So, as a result this voltage it will be for AC signal it will be directly V_C . So, just now what I said is that for this is the total signal total circuit and for small signal on the other hand at the base, we do have only the v_s coming there and then this is the base node. And, at the base node we will be having this corresponding r_{π} which is connected to ground.

And, then of course, we do have the R_B ; R_B also there, but since this R_B as I said it is very high, we may ignore. And, then we do have the DC voltage here which is of course, the AC ground. And, so, that is what the voltage it is coming to the base terminal.

In case if we have v_s ; so, the signal here it will be across this r_{π} it will be same as v_s , but in case if I consider a practical source resistance say R_s , then of course, the voltage here it will be slightly different. So, in that case these two resistances we can map into equivalent input resistance together and these two together practically it is coming r_{π} only and then this r_{π} . So, this r_{π} it is and then R_s they will define what is the voltage coming here from the signal source.

So, to further conclude what will be having at the base, we do have for small signal at the base will be having the v_s having a source resistance R_s . And, then the base to ground node resistance, this resistance it is it is parallel connection of R_B and r_{π} , but we can say this is r

pi. So, this model will be using whenever we will be talking about the small signal analysis. So, at the base that is the equivalent circuit we do have at this point.

Now, let us look into the output port of the circuit, let draw the corresponding the equivalent circuit. To start with we will be going for the large signal first and when you consider large signal this I_B whatever the I_B it will be flowing here, after multiplying with beta F we do have I_C here. So, this I_C it is coming from this I_B after multiplying with beta F.

So, we have to be we are assuming that this circuit once it is decided. Next thing is that so, which means that the I_C it is also getting decided, then we can see what is the corresponding voltage coming here. So, let us look into the output port in the next slide.

(Refer Slide Time: 23:50)

CE amplifier – Fixed bias (contd..)

• **Circuit at Output port**

The slide illustrates the output port of a CE amplifier with fixed bias. It features three main components:

- Circuit Diagram:** Shows a common-emitter amplifier with a base resistor R_B , a collector resistor R_C , and a load resistor R_L . The input signal V_s is applied to the base. The output voltage V_{out} is taken across the load resistor R_L .
- Graph:** A plot of the output voltage V_{out} versus time t , showing a sinusoidal waveform. The peak-to-peak voltage is labeled V_{CE} .
- Equivalent Circuit:** A detailed circuit diagram showing the collector node connected to V_{CC} through R_C and to the load resistor R_L . The collector current I_C is shown as the sum of the quiescent current I_C and the signal current i_c . The output voltage V_{out} is shown as the sum of the quiescent voltage V_{out} and the signal voltage v_{out} . Handwritten annotations include:
 - $V_{out} = V_{CC} - R_C(I_C)$
 - $V_{out} = V_{CC} - R_C(i_c)$
 - $I_C = I_C + i_c$
 - $i_b = \frac{V_s}{R_{in}}$
 - $i_c = \beta i_b$
 - $I_C = \beta I_B$

So, at the output port what we are expecting that voltage here it will be like this it is shown here, it is having a DC voltage called say V_{CE} incidentally, this is V_{CE} or you may call this is V_{out} . So, this level we can say V_{out} on top of that we do have the small signal. So, we do have the small signal here.

So, now this small signal of course, we can extract by as I said by placing this capacitor. So, we will see that part, but initially the DC part, what we have it is we do have R_c connected to V_{cc} and then we do have the collector to emitter voltage. So, we do have the collector to emitter current I_c . So, this I_c it may be having both DC part. So, this I_c may be having 2 currents; one is DC part I_C . And, then also the small signal part, small i_c right.

Then this I_c as I said that it is βI_B whereas, the small signal part here whatever the small signal we are seeing here, this is also βi_b . So, this β it is slightly different from β_F it is called large signal β in forward direction, this is called a small signal current gain β , but practically we may consider both are equivalent, but you need to be careful there they are not exactly same. On the other hand the small signal current here it is this β multiplied by i_b and this i_b it is essentially it is coming from the v_s divided by r_{pi} .

So, we will see this it is shown, but just to see that the current flow here it is having DC component and the small signal component, then we do have if I consider the voltage at this point. So, voltage at this point we do have DC part, it is generated by this DC current R_c and V_{cc} . So, we do have this V_{OUT} , just now what we said is V_{OUT} , which is V_{cc} minus R_c multiplied by I_C , which is of course, βI_B . In addition to that we also have a small signal part so, we may call small v_{out} .

So, what is that it is for that small signal this is ground and so, we can say this is ground and the i_c current is flowing here. So, we may say that this is minus R_c multiplied by i_c and this i_c as I said that this is βi_b and on the other hand this part it is $\beta_F I_B$ ok.

So, now we do have both the DC part and the AC part together that gives us this signal, so, instantaneous signal. Now, by placing the capacitor here, by placing this capacitor here we are removing this DC part and at the output what we see it is only this part.

So, if you are observing the signal here what we will see that it is a small signal with respect to ground; so, with respect to ground. And, we call this is small v small out right. Now, if I combine this information together we can get the small signal equivalent circuit.

(Refer Slide Time: 29:12)

CE amplifier – Fixed bias (contd...)

- Small signal equivalent circuit(s)

The diagram illustrates the small signal equivalent circuit of a common-emitter (CE) amplifier with fixed bias. It shows an AC voltage source V_s connected to the base of a BJT. The base-emitter junction is represented by a diode and a resistor r_{π} . The base current is labeled i_b . The collector is connected to a resistor R_c and the output voltage V_{out} is taken from the collector. The collector current is labeled $I_c = ?$. The emitter is connected to ground. A smaller inset diagram shows the full fixed-bias circuit with V_{cc} , R_b , R_c , and a coupling capacitor.

So, in the next slide we can look into the corresponding small signal side equivalent circuit. But let me take a break and then we will be discussing in detail on this one.