

**Analog Electronic Circuits**  
**Prof. Pradip Mandal**  
**Department of Electronics and Electrical Communication Engineering**  
**Indian Institute of Technology, Kharagpur**

**Lecture – 79**  
**Differential Amplifier: Analysis and Numerical Examples (Contd.)**

(Refer Slide Time: 00:26)




The image shows a slide from an NPTEL online certification course. The slide has a yellow background with a blue and teal geometric design on the left side. At the top, there are two logos: the IIT Kharagpur logo on the left and the NPTEL logo on the right. Below the logos, the text reads: "NPTEL ONLINE CERTIFICATION COURSES", "Course Name: *Analog Electronic Circuits*", "Faculty Name: *Dr. Pradip Mandal*", and "Department : *Electronics and Electrical Communication Engineering*". The topic is listed as "Topic: *Differential Amplifier: Analysis and Numerical examples (contd.)*". The slide is displayed on a computer screen, with a Windows taskbar visible at the bottom.

So dear students, welcome back to our NPTEL online certification course on Analog Electronic Circuits. Myself Pradip Mandal from E and EC Department of IIT, Kharagpur. Today's topic of discussion it is continuation of Differential Amplifier.

In the previous lecture, we have completed analysis and today we will be talking about numerical examples. So, the concepts we are planning to cover it is the following.

(Refer Slide Time: 00:59)

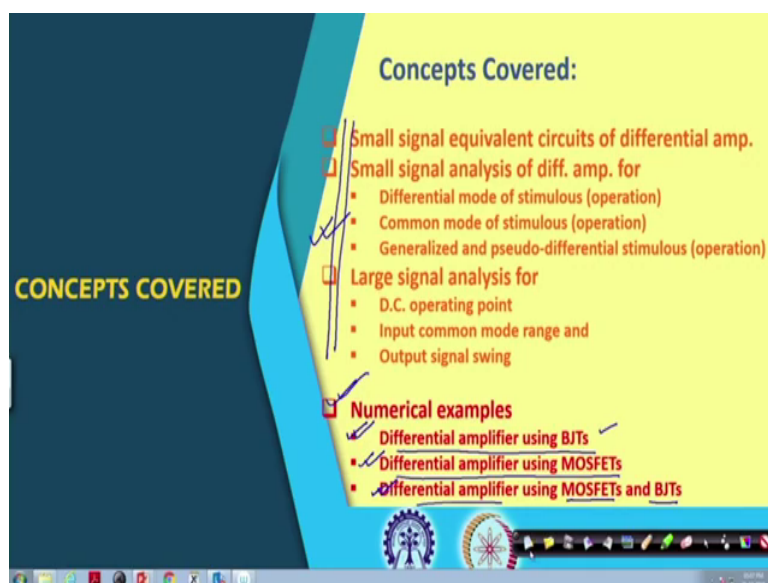

As I said that, the analysis part it is done in the previous 2 lectures, and we are going to talk about numerical examples, and we do have primarily differential amplifier using BJT then we do have differential amplifier using MOSFET and then also we do have another example where we do have the differential amplifier, we do have both types of transistor MOSFET as well as BJT.

So, this differential amplifier having BJT's it will be having different perspective; namely, the DC operating point and then small signal parameters, then differential mode gain, common mode gain and then going to the input range and output swing.

So, almost every aspects it will be covered with this example. Similarly, here also, we will be covering most of the aspects and then in the third example, we shall try to see that how the

performance can be enhanced by replacing one of the passive element namely, the tail resistor by active device to enhance the performance ok.

(Refer Slide Time: 02:32)

**Numerical example: Differential amplifier realized by BJTs**

- $\beta_1 = \beta_2 = 100$ ;  $V_{BE(on)1} = V_{BE(on)2} = 0.6V$ ;  $V_{A1} = V_{A2} = 100V$ ;
- $V_{CC} = 12V$ ;  $R_{C1} = R_{C2} = 5.2\text{ k}\Omega$ ;  $R_T = 1\text{ k}\Omega$
- $C_{L1} = C_{L2} = 100\mu\text{F}$

➤ For  $V_{BEC} = 2.6V$ , Find:

- Operating points of transistors
- Output d.c. voltage
- Values of small signal parameters of transistors
- Output swing (distortion free output signal)
- Differential mode gain
- Common mode gain

$I_{C1} = I_{C2} \approx 1\text{ mA}$

So, we do have differential amplifier realized by BJT. So, this is the circuit we have discussed before and you may recall that in our most of our analysis we used to split this resistor  $R_T$  into two identical elements in parallel. And the intention of that was to get more insight of the circuits particularly, to see how the differential signal and common mode signal they are getting propagated from primary input port to the primary output port.

Now, but then actual circuit of course, we do have only one tail resistor. So, the analysis we have done there where this  $R_T$  it was split into 2 identical part and then if you connect the emitter of the 2 transistors together, then this circuit and that circuit they are essentially same.

So in our discussion now, most of the time we will be using this tail resistor it is connected together. So, here how we do have the different device parameters namely, for BJT's we do have beta. In this case, this beta may not be having much of use, but for the sake of completeness we are keeping the parameter.

And then we do have the  $V_{BE}$  on of both the transistors 0.6. In fact, we are considering Q 1 and Q 2, they are identical and then we also have the early voltage of the 2 transistors equals to 100 volt. And then we do have the supply voltage equals to 12 volt and then the loads R C 1 and R C 2, both are equal; and they are equal to 5.2 kilohm and the tail resistor it is 1 kilohm.

Then, load capacitance for this example it is not mandatory, but just to say that we may consider high frequency signal also and then we can consider that the load is also balanced namely the load here C L 1 and C L 2 they are in this case they are both are equal to 100 pico Farad.

Now to start with, we do have this DC voltage given to us which is 2.6. In fact, this DC voltage should be sufficiently high, so that Q 1 and Q 2 should be in active region. And on the other hand this DC voltage should not be too high otherwise, Q 1 and Q 2 may enter into saturation region.

So, here we have picked up the value of this DC voltage well within its range, allowable range. So, with this 2.6 of V INC, let us try to find the operating point of the transistors. And of course, we have considered Q 1 and Q 2, they are identical. So, how do you proceed? First of all, for DC analysis we can ignore the AC signal part and then we may say that we do have 2.6 volt here and also 2.6 volt here at both the base terminal of Q 1 and Q 2.

Now, if I consider  $V_{BE}$  on drop of 0.6, then we do have the emitter voltage DC wise it is 2 volt. Now R T equals to 1 kilohm. So, the current flow here it is 2 divided by 1 k, so that is 2 milliamper. And under quiescent condition, in absence of the small signal, this 2 milliamper

current it is equally getting divided into 2 halves, one for the left branch and another one is for the right branch. So, 1 milliampere current it is flowing through Q 1 likewise, for the Q 2.

Now, we assume that of course, this is the emitter current 1 milliampere. So, we assume that the base current is very small. So, we can say that the collector current of transistor 1 as well as transistor 2 both of them we can well approximate by 1 milliampere. Now we do have 6 volt here sorry, we do have 2.6 volt here we do have 2 volt here, and now we do have 1 milliampere current is flowing through this resistor which is having a value up to 5.2 kilohm.

So, the drop across this resistor it is 5.2 volt. So, the voltage at the collector DC voltage at the collector it is 12 volt minus 5.2. So, that is equal to 6.8. So, we can say that now we obtain the operating point and then also we obtain the DC voltage. DC voltage it is same here also 6.8 volt ok.

(Refer Slide Time: 08:55)

**Numerical example: Differential amplifier realized by BJTs**

- $\beta_1 = \beta_2 = 100$ ;  $V_{BE(on)1} = V_{BE(on)2} = 0.6V$ ;  $V_{A1} = V_{A2} = 100V$ ;
- $V_{CC} = 12V$ ;  $R_{C1} = R_{C2} = 5.2\text{ k}\Omega$ ;  $R_T = 1\text{ k}\Omega$
- $C_{11} = C_{12} = 100\text{pF}$

For  $V_{BNC} = 2.6V$ , Find:

- ✓ Operating points of transistors
- ✓ Output d.c. voltage
- ✓ Values of small signal parameters of transistors
- ✓ Output swing (distortion free output signal)
- ✓ Differential mode gain
- ✓ Common mode gain

*O.Swing:*

$-V_c = 6.8 - 2.3 = 4.5V$

$+V_c = 12 - 6.8 = 5.2V$

$V_{in,d} = ?$

$V_{in,c} = ?$

$I_{C1} = 1\text{ mA} \Rightarrow \frac{q}{\beta_1} = \frac{1\text{ mA}}{100} = \frac{1}{100}\text{ mA}$

$r_{\pi 1} = 100 \times 26 = 2.6\text{ k}\Omega$

$r_{o1} = \frac{V_{A1}}{I_{C1}} = \frac{100V}{1\text{ mA}} = 100\text{ k}\Omega$

$A_d = \frac{g_m R_c}{26} = \frac{5.2 \times 10^3}{26} = 200$

$A_c = \frac{-g_m R_c}{1 + g_m (2R_T)} = \frac{-200}{1 + \frac{2000}{26}} = -2.566 \approx -2.6$

$V_{o,d} = V_{o,c}$

$V_{o,c} = 2.6V$

$V_{o,d} = 2.6V$

So, to summarize the DC operating point, we do have 2.6 volt is the base voltage and then at the emitter. So here also, it is 2.6 volt and at the emitter we do have 2 volt. Then, voltage here it is 6.8 volt and here also it is 6.8 volt and the collector current in both the transistors they are equal and they are 1 milliamperes right.

So, that gives us the operating point of both the devices. In fact, you can calculate what is the VCE and ensure that Q 1 and Q 2 both are in active region of operation. In fact, we do have sufficient headroom.

So, in case if you have say VCE is at is 0.3 volt. So, this voltage it can come down as low as 2 point; so, this voltage it can go as low as 2.3. So likewise, so we do have a swing here with respect to DC voltage it is 6.8 minus 2.3. So, that is equal to 4.5. So, the negative side swing it is 4.5.

So, the output showing; so, negative side it is 6.8 minus 2.3 volt, alright. So, that is considering VCE voltage it is equal to 0.3 and that is equal to 4.5 volt. So, likewise for positive side for positive side the voltage here it can go towards the supply voltage. So, here we do have 12 volt DC and then the DC voltage at the output it is 6.8.

So, the positive side on the other hand it is 12 minus 6.8. So, that is equal to 5.2 volt. So, we do have fairly good swing. So, which means that whatever the DC voltage we do have, over that DC voltage we can have very nice signal swing. So, the circuit operating point it is very good. So, 6.8 volt is the DC level.

So, now we obtain the output swing. So, we obtain operating point, we obtain the DC voltage; now, next thing is the small signal parameter of transistors. So, we do have the collector current  $I_C$  equals to 1 milliamperes, and that gives us  $g_m$  equals to 1 milliamperes divided by 26 millivolt, if I consider thermal equivalent voltage, it is 26 millivolt.

So, that is equal to 1 by 26 mho and then  $r_{\pi}$  equals to  $\beta$  divided by  $g_m$ . So, that is 100 multiplied by 26; so, that is equal to 2.6 kilohm. And then output resistance  $r_o$ , so, that is

equal to early voltage divided by  $I_C$ . So, this is equal to 100 divided by 1 milli. So, that is giving us 100 kiloohm.

So, we assume that this 100 kilo ohm it is much higher than this passive load  $R_{C1}$  and  $R_{C2}$ . So, that gives us the small signal parameter. In fact, for the other transistor parameters are also same corresponding to whatever the parameter we obtain for  $Q_1$ . So, now we obtain the small signal parameters of both the transistors. Next thing is we need to find the small signal gain namely, a differential mode gain and common mode gain.

So, the differential mode gain  $A_d$  equals to  $g_m$  into  $R_C$  and this is equal to  $R_C$  it is 5.2 and  $g_m$  is equal to  $1/26$  and this is of course, it is kiloohm. So into 10 to the power 3 so, that is equal to 200 and the common mode gain on the other hand it is  $g_m$  into  $R_C$  divided by  $1 + g_m$  into  $2R_T$  alright .

And so, in the numerator we do have 200, just now we have calculated and then we do have a  $1 + 2000$  divided by 26. So, this is equal to how much? 2000 divided by 26; I do have calculator for me. So, 2000 divided by 26 is equal to 77 plus 1 and the denominator and so that, reciprocal of that, multiplied by 200 is giving me 2.566 and so and so.

In fact, if you ignore this 1, you will be getting this is equal to 2.6. Of course, it is having a minus sign, alright. So, we do have the differential mode gain of 200 and then we do have the common mode gain; common mode gain is basically approximately it is minus 2.6.

So, now next thing is that once we feed the signal, once we feed the small signal namely,  $V_{in1}$  and then  $V_{in2}$  based on this differential mode gain and common mode gain, we will be getting the signal at this point namely, at  $V_{o2}$  and then  $V_{o1}$ . And to get the individual signal first of all, based on this  $A_d$  and  $A_C$  as you have done for the macro model based numerical example.

To get the individual signal first thing is that, we need to see what is the differential input, and then what is the common mode input, and then we multiply this differential and common mode component of the input by their respective gain to get the  $V_{od}$  and  $V_{oc}$ , and from that we

can find what will be the individual signal. So, keeping the operating point same, let we find what will be the corresponding output for a given set of V in 1 and V in 2.

(Refer Slide Time: 17:48)

**Numerical example: Differential amplifier realized by BJTs**

- $\beta_1 = \beta_2 = 200$ ;  $V_{BE(ON)1} = V_{BE(ON)2} \approx 0.6V$ ;  $V_{A1} = V_{A2} = 100V$ ;
- $V_{CC} = 12V$ ;  $R_{C1} = R_{C2} = 5.2 k\Omega$ ;  $R_T = 1 k\Omega$
- $C_{L1} = C_{L2} = 100pF$
- $V_{INC} = 2.6V$
- For  $v_{in1} = 0.01 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$
- Find:  $v_{in2} = -0.01 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$

Handwritten notes on the slide:

- $V_{in-d} = v_{in1} - v_{in2} = 0.02 \sin\left(\frac{2\pi}{T} \cdot t\right)$
- $V_{in-c} = \frac{v_{in1} + v_{in2}}{2} = 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$
- $V_{o-d} = 6.8V$
- $A_d = 200$
- $A_c = -2.6$
- $V_{o-d} = (200 \times 0.02) \sin\left(\frac{2\pi}{T} \cdot t\right) = 4 \sin\left(\frac{2\pi}{T} \cdot t\right)$
- $V_{o-c} = (-2.6 \times 0.2) \sin\left(\frac{2\pi}{4T} \cdot t\right) = -0.52 \sin\left(\frac{2\pi}{4T} \cdot t\right)$
- $V_{o1} = 6.8 - 0.52 \sin\left(\frac{2\pi}{4T} \cdot t\right) + 2 \sin\left(\frac{2\pi}{T} \cdot t\right)$
- $V_{o2} = 6.8 - 0.52 \sin\left(\frac{2\pi}{4T} \cdot t\right) - 2 \sin\left(\frac{2\pi}{T} \cdot t\right)$

So, in the next slide what we have it is, so, we are keeping the operating point same. Namely, we do have V INC equals to 2.6. So, this is equal to 2.6 volt and that gives the whatever the operating point we obtain and we know that DC voltage wise V o DC equals to; so, that is 12 minus 5.2, so, that is 6.8, right.

And also, we have calculated the A d equals to 200 and A C on the other hand, it is minus 2.6 now here we do have the v in 1 and v in 2 and if you see here, the this part similar to our numerical examples associated with the macro model v in.



So, this 2 if I consider, so, this is giving us  $v_{in d}$  equals to; so,  $v_{in d}$  equals to  $v_{in 1}$  minus  $v_{in 2}$ . So, that is equal to  $0.02 \sin 2\pi \text{ by capital T into small t}$ . On the other hand, if I consider the common part namely, if I take the average of the 2 inputs; so that gives us the common mode input  $v_{in c}$ . So, that is equal to  $v_{in 1}$  plus  $v_{in 2}$  divided by 2 and that is equal to  $0.2 \sin 2\pi \text{ by 4 T into t}$ .

So, we do have the common mode component and we do have the differential mode component here and we do have the differential mode gain and common mode gain. So, from that we can get  $v_{o d}$  equals to, so, this 200 multiplied by 0.02. So, that gives us 200 multiplied by  $0.02 \sin 2\pi \text{ by capital T into small t}$ . So, that is equal to  $4 \sin 2\pi \text{ by capital T into small t}$ . So, that is the differential output.

So likewise, we can calculate the common mode common mode output  $V_{o c}$  equals to minus 2.6 into this common mode part  $0.2 \sin 2\pi \text{ by 4 T}$ , it is having different frequency. So, this is equal to how much? This is  $0.52 \sin 2\pi \text{ by 4 T into small t}$  of course, with a minus sign.

So, now we have obtained the differential and common mode component. So, the individual signal now, we can say that say  $V_{o 1}$ , it is having the DC part 6.8 volt DC and then, we do have the common mode part. So, that is minus  $0.52 \sin 2\pi \text{ by 4 capital T small t}$  and then it is also having half of the differential part. So, that is equal to plus  $2 \sin 2\pi \text{ by capital T into small t}$ .

So likewise, if you see the other output  $V_{o 2}$ ; so, that is also having DC of 6.8 and then the common mode part minus  $0.52 \sin 2\pi \text{ by 4 T into small t}$  and then minus  $2 \sin 2\pi \text{ by capital T into small t}$ . So, that gives us the complete output. So, we can see here the this is the; this is the common mode part. So, this part and this part they are common mode and then we do have the differential part, here and here.

And if you compare if you compare the common mode part and differential part, it is almost that differential part if I see, individual signal-wise and if you take the particularly the

differential output, at differential part it is quite large. In fact, almost 8 times higher. So, this part it is almost 8 times higher than the common mode part.

However, if you see at the input if you compare the differential part which is 0.2 and then common 0.02 rather and common mode part it is 0.2. So, here on the other hand, the common mode part it was 10 times higher.

Which indicates that the whatever the signal we are receiving here, that may be getting affected by significantly I should say affected by unwanted signal having an amplitude which is 10 times higher than the desired signal, differential signal.


And through this differential amplifier which is having differential mode gain, it is much higher than the common mode gain and that is why at the output we are getting the desired signal almost having 8 times higher amplitude than the unwanted component unwanted component is this common mode component, right. So, that is the basic motivation.

Now, next thing is that how do we see the signal? Particularly, if I consider how the common mode and differential mode signal it is getting propagated.

(Refer Slide Time: 26:23)

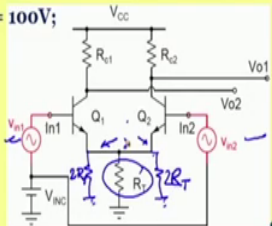**Numerical example: Differential amplifier realized by BJTs**

- $\beta_1 = \beta_2 = 200$ ;  $V_{BE(on)1} = V_{BE(on)2} \approx 0.6V$ ;  $V_{A1} = V_{A2} = 100V$ ;
- $V_{cc} = 12V$ ;  $R_{C1} = R_{C2} = 5.2 k\Omega$ ;  $R_T = 1 k\Omega$
- $C_{L1} = C_{L2} = 100pF$
- $V_{INC} = 2.6V$
- For  $v_{in1} = 0.01 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$   
 $v_{in2} = -0.01 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$
- Find:
  - >  $v_{o,d}$  and  $v_{o,c}$
  - >  $v_{o1}$  and  $v_{o2}$



The slide also features a Windows taskbar at the bottom with various application icons and a system tray showing the time as 10:10 AM on 2/12/2021.

Particularly, you may recall in the analysis we used to split the this resistor into 2 parts, and we use to claim that this 2 R T and this 2 R T we used to split them and then we used to see that the signal here and signal here it was propagating differently for common mode part and differential part.

And now here, at the input the stimulus it is having both differential as well as the common mode part.

(Refer Slide Time: 27:20)

### Numerical example: Differential amplifier realized by BJTs

- $\beta_1 = \beta_2 = 200$ ;  $V_{BE(ON)1} = V_{BE(ON)2} \approx 0.6V$ ;  $V_{A1} = V_{A2} = 100V$ ;
- $V_{CC} = 12V$ ;  $R_{C1} = R_{C2} = 5.2 k\Omega$ ;  $R_T = 1 k\Omega$
- $C_{L1} = C_{L2} = 100pF$
- $V_{INC} = 2.6V$ ,
- For  $v_{in1} = 0.01 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$
- $v_{in2} = -0.01 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$
- Find:
  - $V_{o1}$  and  $V_{o2}$
  - $V_{o_d}$  and  $V_{o_c}$

So, in case if you in this actual circuit if you split these 2 resistors and we like to see what other things are happening, namely, with this kind of signal what is the signal amplitude you are getting at the emitter and the output. So again, we are keeping the same operating point, only thing is that the  $R_T$  it has been split into 2 parts, identical parts  $2 R_T$  and also here we have opened it, here we have opened it.

Now in this case, if we open it and if we are keeping the same stimulus namely,  $v_{in1}$  and  $v_{in2}$  then what happens? First of all, if you see once you do have a split here, identical split here and then even though we are applying the same 2.6 volt here, the operating point it is remaining same, but left and right half they are completely isolated.

So here again, if you see the operating point here, the DC voltage it 2.6 and the voltage coming here it is 2 volt and now  $2 R_T$  having  $R_T$  equals to 1 k, this current it is 1

milliampere. So, that gives us the emitter current 1 milliampere and then the collector current is also very close to 1 milliampere.

So, we can say that the and this 1 milliampere it is flowing through  $R_C$  1 creating a drop of 5.2 volt since its value it is 5.2 k. So, the voltage here again it is 6.8. So, with this spilt of course, the as expected the operating point is not getting changed.

So, the corresponding small signal parameter namely  $g_{m1}$  and  $g_{m2}$ , they remain same and both of them are equal to  $1/26$  mho and  $r_{\pi}$  of the 2 resistors transistors they are remaining 2.6 k and then  $r_{o1}$  equals to  $r_{o2}$  they are equal to 100 k.

Now, if I am having this parameter and then I do have a signal  $v_{in1}$  coming here. So, what do you expect? That the left half it is completely isolated. So, just by analyzing this left part we can calculate what may be the signal coming here and the signal coming here, ok. So, let me clear the board and then let me write those signals expression.

(Refer Slide Time: 30:27)

**Numerical example: Differential amplifier realized by BJTs**

- $\beta_1 = \beta_2 = 200$ ;  $V_{BE(on)1} = V_{BE(on)2} \approx 0.6V$ ;  $V_{A1} = V_{A2} = 100V$ ;
- $V_{CC} = 12V$ ;  $R_{C1} = R_{C2} = 5.2 k\Omega$ ;  $R_T = 1 k\Omega$
- $C_{L1} = C_{L2} = 100pF$
- $V_{INC} = 2.6V$ ,

For  $v_{in1} = 0.01 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$

$v_{in2} = -0.01 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$

Find:

- >  $V_{o1}$  and  $V_{o2}$
- >  $V_{o,d}$  and  $V_{o,c}$

$A_v = \frac{-g_m R_{C1}}{1 + g_m 2R_T} = \frac{-200}{1 + 77} = -2.566$

$V_{o1} = -2.6 v_{in1} = -2.6 \sin\left(\frac{2\pi}{T} \cdot t\right)$

$V_{o2} = -0.026 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.52 \sin\left(\frac{2\pi}{4T} \cdot t\right)$

$V_{o,d} = V_{o1} - V_{o2} = 0.052 \sin\left(\frac{2\pi}{T} \cdot t\right)$

$V_{o,c} = \frac{V_{o1} + V_{o2}}{2} = -0.52 \sin\left(\frac{2\pi}{T} \cdot t\right)$

$V_{e1} = v_{in1} \times \frac{2R_T}{2R_T + \frac{1}{g_m}} = v_{in1} \times \frac{2000}{2026} = 0.987 \cdot v_{in1}$

$V_{e2} = 0.00987 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.1974 \sin\left(\frac{2\pi}{4T} \cdot t\right)$

So, the gain of this transistor Q 1 and its corresponding associated bias we can say that its voltage gain equals to  $g_m R_{C1}$  divided by  $1 + g_m 2R_T$  of course, with a minus sign. So, what is the value? Here, we have calculated this is equal to 200 and this is 1 plus close to 77 and this is equal to minus 2.56 or I should say, approximately equal to minus 2.6. So, if I ignore this 1, then you then  $R_{C1}$  divided by  $2R_T$  that gives us 2.6.

So, that is the gain from this point to this point. Which means that for this input, the output signal we are getting namely,  $V_{o2}$  what we are expecting here it is minus 2.6 multiplied by  $V_{in1}$ , alright. And then we do have 2 components, and if you see here so, the first component it is minus  $0.026 \sin 2\pi$  by capital T into small t and then we also have to multiply this point 2 and 2.6 for this component.

So, that is equal to minus  $0.52 \sin 2\pi \times 4T$  into  $t$ . You might have observed that since this circuit, left part it is completely isolated from the right part. So, this circuit of course, it is working as common emitter amplifier having a D-generator of  $2R_T$ .

So, this circuit of course, it cannot distinguish which is common mode part and the differential part. So, both the differential part as well as the common mode part it will amplify and whatever the signal it is coming here it is given here.

And also, if you see the signal at this point and so, if I call that signal it is  $v_{emitter 1}$ . So, what kind of signal do I get? Before we can consider this  $R_T$ , we are getting almost the  $v$  in here and then we do have the output impedance which is  $1/g_{m1}$ .

And then we are connecting  $2R_T$ . Note that this  $v_{in 1}$  it is not this  $v_{in 1}$ , it is the signal coming at this point which is very close to this signal, alright. And so, before we consider this resistance the signal here, if I consider it is having say infinite resistance then at this point the signal it will be same as whatever the signal we are applying here.

So, that is why you are calling it is voltage it is getting translated to emitter or emitter is following the base terminal. And then we do have this resistance which is  $1/g_{m1}$ . So, once this Thevenin equivalent voltage source it is getting loaded by  $2R_T$  then, whatever the voltage we do get here it is nothing, but this  $v_{e1}$ .

So, this voltage it is  $v_{in 1}$ , the reflected signal coming to the emitter multiplied by  $2R_T$  that is because, divided by  $2R_T$  plus  $1/g_{m1}$ . That is because, this signal it is getting divided across this  $1/g_{m1}$  and  $2R_T$  to create this voltage called  $v_{e1}$ .

So, this is the; this is the signal we are getting at this point before connecting the load, it was like this and then once we connect this  $2R_T$  then, whatever the voltage we are getting here. So, if I calculate this one, it is coming  $v_{in 1}$  multiplied by this is  $2k$ . So, 2000 and this is

2000, this is 1 by  $g_m$  that is 26 so, 2026. In fact, this part it becomes very close to 1 this is equal to 0.987, I think that was my calculation 0.9 what is 87 multiplied by this  $v$  in 1.

Which means that, I do have this signal equals to minus so, no I do not have the minus sign here, I do have the signal coming in phase. So, I do have 0.01 multiplied by 0.987; so, I do have  $0.00987 \sin 2\pi$  by capital  $T$  into small  $t$ .

And then we do have this part that is also getting multiplied by this one so, that is equal to plus we do have 4791 point. So, this  $\sin 2\pi$  by 4  $T$  into small  $t$ . So, that is corresponding to this part. So, this is the signal coming at emitter here.

In fact, similar kind of things you will be getting at the other side namely, at this point and likewise, here also we will be getting the signal. So, the signal coming here it will be similar to whatever we obtained namely, the gain of this transistor along with its bias arrangement it will be having the same gain of minus 2.6.

So, we can say that  $v_{o1}$ , this  $v_{o1}$  signal wise, it is equal to this is having minus gain is minus 2.6 and this signal it is minus. So, I do have plus  $0.026 \sin 2\pi$  by capital  $T$  into small  $t$  and then we do have this part. So, it is having a minus and then we do have  $0.52 \sin 2\pi$  by 4  $T$  into small  $t$ .

So, we do have the 2 frequencies again, this amplifier it does not really understand the common mode part and differential part. So, both of these parts are getting amplified by the same gain. So, if I see individual signal, if I see the see individual signal this and this of course, it is having both the frequency component and if you are keeping this node still open and if you consider the differential output say  $v_{od}$  which is  $v_{o1}$  minus  $v_{o2}$  by definition.

And, so if I take the difference of this signal and this signal then, obviously, this part it is getting removed, leaving behind this part and this part multiplied by 2; because they do have opposite sign. So, what we are getting there, it is  $0.052 \sin 2\pi$  by capital  $T$  into small  $t$ , and this part as I said, that they are getting removed.



On the other hand, if I take the average of the 2 signal; so, if I take average of this signal and this signal that gives us the output common mode. And so, if I take average of  $v_{o1}$  and  $v_{o2}$ , in fact, in that case this part and this part they are getting cancelled leaving behind this part and this part.

So, that is equal to  $\sin 2\pi \cdot 4T \cdot t$ . So now if you see, that this part even if you are keeping this is open, the common mode part common mode part it is same as the case when we have connected it or in the previous circuit.

But then, the differential part if you see it is quite small. In fact, if you connect it to get the original circuit, then what we have obtained it is that corresponding differential output; it was having an amplitude it was 4 volt if you recall right, and so, now if I make a connection, what we are expecting that the emitter voltage at this at the emitter of transistor 2 it is also having similar kind of signal as you can see here similar kind.

So, what will be the difference? This part it will be same, but this part it will be having opposite sign. So, if I observe the voltage at this point, before we make the connection and we call this is say  $v_{e2}$ . So, that is equal to this part and the first part it is having a minus sign  $\sin 2\pi \cdot 4T \cdot t$  then whatever,  $\sin 2\pi \cdot 4T \cdot t$  into  $\sin 2\pi \cdot 4T \cdot t$ .


And then this part on the other hand, it will be having plus sign plus exactly this one  $\sin 2\pi \cdot 4T \cdot t$  then whatever it is. So, the moment we make this connection, this part and this part they are getting cancelled out, and also at the output this part and this part they got amplified and both of them this part it was it is getting converted into  $\sin 2\pi \cdot 4T \cdot t$  with this connection, if you make this connection.

Same thing this part is also getting increased to  $\sin 2\pi \cdot 4T \cdot t$  and naturally, the amplitude of the differential part it got changed to  $4 \sin 2\pi \cdot 4T \cdot t$ . So, this got changed to 2 and this is also 2. So, that gives us the amplitude of 4, alright.

(Refer Slide Time: 44:57)

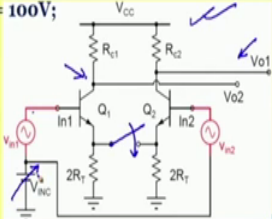**Numerical example: Differential amplifier realized by BJTs**

- $\beta_1 = \beta_2 = 200$ ;  $V_{BE(on)1} = V_{BE(on)2} \approx 0.6V$ ;  $V_{A1} = V_{A2} = 100V$ ;
- $V_{cc} = 12V$ ;  $R_{C1} = R_{C2} = 5.2\text{ k}\Omega$ ;  $R_T = 1\text{ k}\Omega$
- $C_{L1} = C_{L2} = 100\text{pF}$
- $V_{INC} = 2.6V$ ,
- For  $v_{in1} = 0.01 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$
- $v_{in2} = -0.01 \sin\left(\frac{2\pi}{T} \cdot t\right) + 0.2 \sin\left(\frac{2\pi}{4T} \cdot t\right)$
- Find:
  - >  $V_{o1}$  and  $V_{o2}$
  - >  $V_{o_d}$  and  $V_{o_c}$



The slide also features a video feed of a presenter in the bottom right corner and a Windows taskbar at the bottom.

So in fact, in hardware you can make this experiment namely, you can construct this circuit and then if you keep it open and then if you observe the signal here and here, what you will be seeing here, mostly the common mode signal it will be dominating hardly you will be seeing the information out of the differential part because, at the input the strength of the differential signal is very small.

And then, the moment you make this connection all of a sudden, then you will see that the differential part it will be appreciated and then common mode component; however, it will be remaining same.

So in fact, you can do this experiment in the lab, lab setup and you can get a feel of it alright. so next thing is that we will see what will be the suitable range of this input common mode voltage? And so, we have taken a meaningful voltage here, but we like to see what may be its

meaningful range namely, lower limit and upper limit. But then let me take a short break and then we will come back.