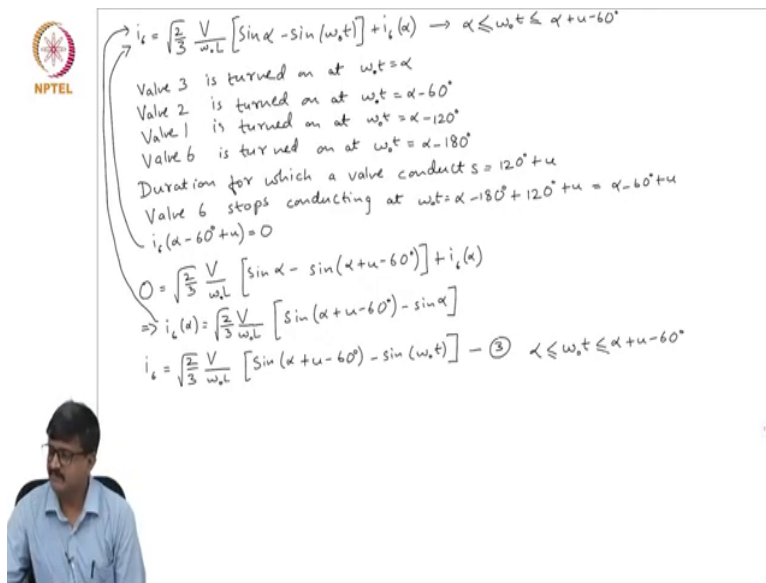


DC Power Transmission Systems
Prof. Krishna S
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture – 29

Analysis of 3 and 4 value conduction mode of 6 pulse LCC: Part 1

(Refer Slide Time: 00:16)



NPTEL

$$i_c = \frac{\sqrt{2}}{3} \frac{V}{\omega L} [\sin \alpha - \sin(\omega_s t)] + i_c(\alpha) \rightarrow \alpha \leq \omega_s t \leq \alpha + u - 60^\circ$$

Valve 3 is turned on at $\omega_s t = \alpha$
 Valve 2 is turned on at $\omega_s t = \alpha - 60^\circ$
 Valve 1 is turned on at $\omega_s t = \alpha - 120^\circ$
 Valve 6 is turned on at $\omega_s t = \alpha - 180^\circ$
 Duration for which a valve conducts $s = 120^\circ + u$
 Valve 6 stops conducting at $\omega_s t = \alpha - 180^\circ + 120^\circ + u = \alpha - 60^\circ + u$
 $i_c(\alpha - 60^\circ + u) = 0$

$$0 = \frac{\sqrt{2}}{3} \frac{V}{\omega L} [\sin \alpha - \sin(\alpha + u - 60^\circ)] + i_c(\alpha)$$

$$\Rightarrow i_c(\alpha) = \frac{\sqrt{2}}{3} \frac{V}{\omega L} [\sin(\alpha + u - 60^\circ) - \sin \alpha]$$

$$i_c = \frac{\sqrt{2}}{3} \frac{V}{\omega L} [\sin(\alpha + u - 60^\circ) - \sin(\omega_s t)] \quad \text{--- (3)} \quad \alpha \leq \omega_s t \leq \alpha + u - 60^\circ$$

So, i_6 is equal to $\frac{\sqrt{2}}{3} \frac{V}{\omega L} [\sin \alpha - \sin(\omega_s t)] + i_6(\alpha)$. Now, this expression is applicable in the first subinterval. Now, one has to note that α is the instant at which valve 3 is turned on, see valve 3 is turned on at $\omega_s t = \alpha$. Then, what about valve 2? Valve 2 is turned on at $\omega_s t = \alpha - 60^\circ$.

Student: (Refer Time: 01:21).

Alpha?

Student: Minus 60 degree.

Minus 60, then valve 1 is turned on at ωt equal to $\alpha - 120$. Then if I take the previous valve that is turned on that is before valve 1 the one valve that is turned on is?

Student: 6.

6. So, valve 6 is turned on at ωt equal to $\alpha - 180$ degrees. Now, what is a duration for which a valve conducts? Duration for which any valve all valves conduct for the same duration. So, duration for which a valve conducts so, duration is an angle what is the duration? 120 degrees plus u ok.

Now, when does valve 6 stop conducting? So, it is turned on at ωt equal to $\alpha - 180$ degrees. So, valve 6 stops conducting; that means, the current through the valve 6 goes to 0; at ωt equal to $\alpha - 180$ plus see $\alpha - 180$ is mentioned it is turned on.

Student: (Refer Time: 03:05).

So, I have to add the duration for which it conducts. So, it is 180 degree plus u . So, this is nothing but $\alpha - 60$ degrees plus u . So, from $\alpha - 60$ plus u is taken as the first subinterval that is the basis for taking this $\alpha - 60$ plus u as the end point of the first subinterval ok. So, what is happening to i_6 at this instant $\alpha - 60$ plus u ?

Student: 0.

0. So, because valve 6 stops conducting. So, i_6 at $\alpha - 60$ degree plus u is 0. So, I substitute this expression for i_6 at this particular instant which is 0, in the general expression for i_6 that I have got ok. So, one should note that this is applicable for what valve use of

ωt . So, this is not an expression which is applicable always this applicable for ωt greater than or equal to α and less than or equal to?

Student: (Refer Time: 04:29) plus u minus 60 degrees.

Alpha plus u minus 60 degrees. So, its of course, applicable at alpha plus u minus 60 degrees. So, if I substitute this here why I do this? I do this to get the expression for.

Student: (Refer Time: 04:45).


i_6 of alpha say only after knowing i_6 of alpha I have so, the solution for i_6 , till then I do not have the solution for i_6 ok. So, if I do that I get. So, what I have to do is, wherever there is ωt replace it by alpha plus u minus 60 and i_6 is equal to 0. So, $\frac{\sqrt{2}}{3} V$ by $\omega L \sin \alpha$ minus $\sin \alpha$ plus u minus 60 degrees plus i_6 of alpha. So, this gives the expression for i_6 of alpha.

So, i_6 of alpha is $\frac{\sqrt{2}}{3} V$ by ωL into $\sin \alpha$ plus u minus 60 degrees minus $\sin \alpha$. So, substitute this explanation for i_6 of alpha in the expression for i_6 that I have got earlier. So, again the same equation, substitute this here. So, from that I get i_6 equal to $\frac{\sqrt{2}}{3} V$ by ωL . So, if I substitute this $\sin \alpha$, which is there in the equation gets canceled with the minus $\sin \alpha$ in the expression for i_6 of alpha.

So, what I am left with is, $\sin \alpha$ plus u minus 60 degrees minus $\sin \omega t$ ok. So, let me call this as equation number 3. So, in the last class we got equations 1 and 2 so, this is 3. This is the expression for i_6 , now as we saw there are 2 loop currents that are unknown, see one loop current is already known that is I_d the other 2 loop current.

So, I am referring to the circuit that was learn in the last class. So, the other loop current is of course, we can solve for any of the 3 quantities. So, we wrote the equations see in terms of i_6 and i_1 . So, will solve for i_1 . So, I will not rewrite those equations 1 and 2; I will just try to use those equations and try to get an expression for i_1 .

(Refer Slide Time: 07:32)




$$\textcircled{1} - \textcircled{2} \times 2$$

$$3L \frac{di_1}{dt} = e_b - e_c - 2e_b + 2e_a = -e_b - e_c + 2e_a = e_a + 2e_a = 3e_a \Rightarrow L \frac{di_1}{dt} = e_a$$

$$L \frac{di_1}{dt} = \frac{\sqrt{2}}{\sqrt{3}} V \sin(\omega t + 150^\circ)$$

$$i_1 = \frac{\sqrt{2}}{\sqrt{3}} \frac{V}{\omega L} [\cos]$$



So, we had equations 1, I just multiply it by equation 2 and subtract it from equation no, I will multiply if equation 1 by 2 and subtract it from equation 2. So, this is for getting the expression for i_1 . So, what do we get?

Student: (Refer Time: 07:57).

$3L \frac{di_1}{dt}$ is equal to $e_b - e_c - 2e_b + 2e_a$ because I am multiplying equation 1 by 2 plus $2e_a$. Is this ok? Or you want me to write equations 1 and 2. I have written I mean I just want do not want to repeat ok, I am presume you have those equations. So, this can be simplified.


So, this is $-e_b - e_c + 2e_a$ and e_a, e_b, e_c are balanced sinusoidal voltages. So, $-e_b - e_c + 2e_a$ is equal to $3e_a$, that is $3e_a$. So, if I substitute the expression for e_a ;

of course, one simplification that is directly possible is in this equation there is a 3 on both sides. So, $L \frac{di}{dt}$ is equal to e_a .

So, this means [inaudible] $L \frac{di}{dt}$ is equal to $\frac{\sqrt{2}}{3} V \sin(\omega t + 150^\circ)$. So, this has to be solved for i . So, if I solve this for i I get $\frac{\sqrt{2}}{3} V \sin(\omega t + 150^\circ)$ into what? So, it is dependent on the instant at which the subinterval starts ok. So, it starts from α .

So, what is the, what is the solution? Cos of say either I can integrate and just find the constant of integration or I can do a definite integral. Say how I do definite integral? See if I want to say I can do both these; I mean will give you the same result I do either I just say integrate this and take a constant of integration find the constant of integration or I can just take this.

(Refer Slide Time: 10:42)



$$\textcircled{1} \times 2$$


$$3L \frac{di}{dt} = e_b - e_c - 2e_b + 2e_a = -e_b - e_c + 2e_a = e_a + 2e_a = 3e_a \Rightarrow L \frac{di}{dt} = e_a$$

$$L \frac{di}{dt} = \frac{\sqrt{2}}{3} V \sin(\omega t + 150^\circ)$$

$$\frac{di}{dt} = \frac{\sqrt{2}}{3} \frac{V}{L} \sin(\omega t + 150^\circ)$$

$$i_1 = \frac{1}{\omega L} \int_{\omega t}^{\omega t} \frac{\sqrt{2}}{3} V \sin(\omega t + 150^\circ) d(\omega t) + i_1(\alpha)$$

$$i_1 = \frac{\sqrt{2}}{3} \frac{V}{\omega L} [\cos(\alpha + 150^\circ) - \cos(\omega t + 150^\circ)] + I_d \quad \textcircled{4} \quad \alpha \leq \omega t \leq \alpha + \omega t_0$$



So, if i_1 by dt is $\frac{\sqrt{2}}{3} \frac{V}{L} \sin(\omega_0 t + 150^\circ)$. So, if I employ the definite integral, it is nothing but integral of the right hand side sorry $\frac{\sqrt{2}}{3} \frac{V}{L} \sin(\omega_0 t + 150^\circ)$ integrate with respect to time. Now, integration with respect to or time will be a bit difficult. So, what I do is, I will multiply and divided by?

Student: Omega.

Omega ω_0 . So, I will just multiply by ω_0 and divided by ω_0 is that ω_0 is a constant. So, that I can put limits on angle instead of time.

Student: Ok.

So, what is the lower limit?

Student: (Refer Time: 11:43).

Student: I knew the I know the both are (Refer Time: 11:45).

Both are equivalent in fact. Now that this is straight forward because, you get the answer in one step otherwise you get it in terms of constant of integration and then you find the concept of integration again put back the put it back in the equation. Now, this is that gives the answer in one shot.

I think you are familiar I presume you are familiar with this. See, you have to integrate from some lower limit and the upper limit is $\omega_0 t$. I presume if there is no cos of confusion; I mean the dummy variable and the upper integral upper limit are one of the same.

Student: Yes.

And I take the value of i_1 at the lower limit. So, what is the lower limit?

Student: Alpha.

It is, see this expression is applicable from what instant?

Student: Alpha to alpha plus (Refer Time: 12:39).


From alpha so, and this is alpha. So, this gives the answer in one step, otherwise you have to write it in terms of a constant of integration and then get the constant of integration again. So, this gives i_1 is equal to $\frac{\sqrt{2}}{3} V$ by $\omega_0 L$ into. So, integral of sin is minus cos. So, I get $\cos \alpha + 150$ degrees, minus $\cos \omega_0 t + 150$ degrees plus what is i_1 at alpha?

Student: I d.


I d. Now is this ok? See what is the other way? Other way is you just do the integration with the constant of integration, I mean both will give the same answer I mean. Now, this is because i_1 of alpha is I d. So, let me call this equation number I have used equations up to 3. So, let me call this 4 this question 4. Now, we have the expression for i_1 and i_6 a in the first subinterval.

Let us go to the second subinterval; sorry the equation 3 is the expression for i_6 in the first subinterval equation 3 ok. Then equation 4 is the expression for i_1 in the first subinterval. Now, let us go to the second subinterval.

(Refer Slide Time: 14:41)



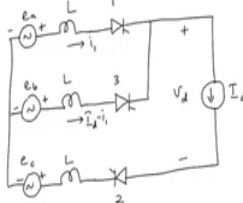Effective circuit diagram in the second subinterval, $\alpha + u - 60^\circ < \omega_s t < \alpha + 60^\circ$



$$L \frac{d}{dt} (I_d - i_1) - L \frac{di_1}{dt} = e_b - e_a$$

$$2L \frac{di_1}{dt} = e_a - e_b$$

$$2L \frac{di_1}{dt} = -\sqrt{2} V \sin(\omega_s t)$$

$$\sqrt{2} L \frac{di_1}{dt} = -V \sin(\omega_s t)$$

$$i_1 = -\frac{V}{\sqrt{2} L \omega_s} \int_{\alpha + u - 60^\circ}^{\omega_s t} \sin(\omega_s t) d(\omega_s t) + i_1(\alpha + u - 60^\circ)$$

$$i_1 = \frac{V}{\sqrt{2} \omega_s L} [\cos(\omega_s t) - \cos(\alpha + u - 60^\circ)] + i_1(\alpha + u - 60^\circ)$$

$$i_a = i_1 - i_2$$

$$i_a = i_1 \quad (\alpha < \omega_s t < \alpha + 60^\circ)$$

From (4), $i_1(\alpha + u - 60^\circ) = \frac{\sqrt{2}}{3} \frac{V}{\omega_s L} [\cos(\alpha + 150^\circ) - \cos(\alpha + u - 60^\circ + 150^\circ)] + I_d$

$$i_1(\alpha + u - 60^\circ) = \frac{\sqrt{2}}{3} \frac{V}{\omega_s L} [\cos(\alpha + 150^\circ) + \sin(\alpha + u)] + I_d$$

$$i_1 = \frac{V}{\sqrt{2} \omega_s L} [\cos(\omega_s t) - \cos(\alpha + u - 60^\circ)] + \frac{\sqrt{2}}{3} \frac{V}{\omega_s L} [\cos(\alpha + 150^\circ) + \sin(\alpha + u)] + I_d \quad (5)$$

$\alpha + u - 60^\circ \leq \omega_s t \leq \alpha + 60^\circ$

So, again we will draw the effective circuit diagram in the second subinterval. So, while effective I mean showing only those elements that conduct current ok, effective circuit diagram then the second subinterval. So, the second subinterval actually starts at alpha plus u minus 60 degrees to?

Student: Alpha plus 60 degrees.

Alpha plus 60 degrees. So, which are the valves that conduct in the second subinterval? 1, 1 3.

Student: 2.

2, 1 2, 1 3 are conducting. See in the first subinterval, 6 1 2 3 were conducting 6 as stop conducting at the end of first subinterval. So, the valves that conduct are 1 2, 1 3. So, if I just draw the effective circuit of course, I have to show all the 3 sources e a, e b, e c this is 1, this is 3, and this is 2. So, the cathodes of 1 and 3 are at the same potential. So, this is I d this is V d. So, there is a current i 1, which is flowing through valve 1 and the current through valve 3 which is i 3 is nothing but for this subinterval it is I d minus i 1.

So, I am again employing Kirchhoff's voltage law or in other words mesh analysis to solve for the unknown current i 1; one of the currents is already known. So, there are 2 loops one loop current I d is known the other current is i 1. So, let us solve for i 1 by employing Kirchhoff's voltage law. So, if I apply Kirchhoff's voltage law to this loop, I get $L \frac{d}{dt} (I_d - i_1) - L \frac{d}{dt} i_1 = e_b - e_a$ I d is a constant. So, derivative with respect to time of I d is 0.

So, what I get is, $2L \frac{d}{dt} i_1 = e_a - e_b$. So, $2L \frac{d}{dt} i_1 = e_a - e_b$ the line voltage. So, what is the expression for e a minus e b? So, peak value is $\sqrt{2} V$. So, e a as a phase angle of 150, e b as a phase angle of 30 degrees so, e a minus e b is $-\sqrt{2} V$.

Student: $\sin \omega t$.

$\sin \omega t$.

So, it is $L \frac{d}{dt} i_1 = \frac{\sqrt{2}}{2} L \frac{d}{dt} i_1 = -V \sin \omega t$. So, solve for i 1. So, again if I tried to directly use the definite integral I get an expression for i 1 as V by $\sqrt{2} \omega L$ into what? See, if I take this i 1 I have to integrate after pushing this $\sqrt{2} L$ to the right hand side I have to integrate with respect to ωt after dividing by ωL and the limits are.

Student: (Refer Time: 19:59).

If I let me some more steps. Minus V by $\sqrt{2} L^{-1}$ by ω integral of $\sin \omega t$ d ωt what are the limits?

Student: Alpha plus u minus 60.

Alpha plus u minus 60 degrees upper limit is?

Student: ωt .

ωt , plus i_1 at?

Student: Alpha plus u minus 60 degrees.

Alpha plus u minus 60 degrees. So, from that we get the expression for i_1 as V by $\sqrt{2}$ ωL . So, integral of minus \sin is \cos . So, I get $\cos \omega t$ minus \cos alpha plus u minus 60 degrees, plus i_1 at alpha plus u minus 60 degrees. Now, this equation will be of will be useful only if I know what is i_1 at alpha plus u minus 60. So, what how to get i_1 at alpha plus u minus 60?

Student: Previous (Refer Time: 21:33).

So, this is nothing but the value of i_1 at the instant of starting of the first sorry second subinterval, see second subinterval starts at alpha plus u minus 60. So, the value of i_1 at this instant is same as the value of i_1 at the instant of the I mean ending of this first subinterval; please note i_1 is continuous why i_1 is continuous?

Student: (Refer Time: 21:59).

i_1 is the current through the inductance. Now, please not i_1 is the valve current but is it also the current through the inductance. See in that in these effective circuit it is of course, say

these things can be used only if say value or the starting of the first subinterval second subinterval is equal to value of the end of the first subinterval can be used as long as i_1 is continuous is i_1 continuous.

Student: (Refer Time: 22:35).

i_1 is continuous why?

Student: (Refer Time: 22:39).

Because, the current no current through the inductance is i_a , how is i_a is continuous does not mean i_1 has to be continuous. So, I mean how do you; how do you say it is continues? Any?

Student: (Refer Time: 23:05).

Sorry.

Student: Both are (Refer Time: 23:11).

In the so, if you go back to the original circuit so, was it connected to in series of the same inductance ok?

Student: (Refer Time: 23:41).

Can I relate 2 valve currents and the face current i_a ? It is i_1 .

Student: (Refer Time: 23:49).

Minus.

Student: i_4 .

i_4 . Now, what was i_4 in the previous first subinterval?

Student: 0.

0 second subinterval? 0. So, for these 2 subintervals i_4 is 0. So, therefore, i_a is i_1 . So, i_1 is the current through the valve ok. So, for i_a is equal to i_1 for α , sorry α less than ωt less than $\alpha + 60$ degrees. So, due to which i_1 happens to be the current through inductor not always in this, interval first interval which consists of 2 subintervals ok. So, I can use the previous equation. So, what is the previous equation? Previous equation is equation 4. So, this equation 4 is applicable up to $\alpha + u$ minus 60.

See it is applicable in the first subinterval. See please note this let me repeat this i_6 expression given by equation 3 is applicable for ωt greater than α and less than $\alpha + u$ minus 60 degrees. And one can check that it is also applicable for ωt equal to α and ωt equal to $\alpha + u$ minus 60. Similarly, the expression for i_1 given by equation 4 is applicable for ωt greater than or equal to α and less than or equal to $\alpha + u$ minus 60 degrees.


So, I use equation 4, which is applicable even for $\alpha + u$ minus 60 degrees and get the expression for i_1 plus α i_1 at $\alpha + u$ minus 60 degrees. So, from 4 i_1 plus i_1 at $\alpha + u$ minus 60 degrees is equal to. So, what you need to do is, wherever there is ωt replace that by $\alpha + u$ minus 60 degrees.

So, what we get is, $\frac{\sqrt{2}}{3} V$ by $\omega L \cos \alpha + 150$ degrees minus $\cos \alpha + u$ minus 60 degrees that replaces $\omega t + 150$ plus I_d . So, that gives i_1 at $\alpha + u$ minus 60 degrees as $\frac{\sqrt{2}}{3} V$ by $\omega L \cos \alpha + 150$; $\cos \alpha + u$ plus 90 degrees can be written as $\sin \alpha + u$ that is all, $\sin \alpha + u$ plus I_d . So, this

gives the expression for i_1 at $\alpha + u - 60$. So, I substitute this in the expression for i_1 here. So, that gives me the expression for i_1 in the second subinterval.

So, i_1 is $\frac{V}{\sqrt{2}\omega L} \cos(\omega t - \alpha + u - 60^\circ) + \frac{V}{\sqrt{2}\omega L} \cos(\alpha + 150^\circ + u)$ ok. So, let me use some number for this equation, equation number 5. So, this is equation 5. So, equation 5 is applicable from $\alpha + u - 60^\circ$ to $\alpha + 60^\circ$.

(Refer Slide Time: 29:11)



$$i_1(\omega t + 60^\circ) = i_6(\omega t)$$

$$i_1(\alpha + 60^\circ) = i_6(\alpha)$$

Expression for i_6 in the 1st subinterval (equation ①) and replace ωt by α
 = Expression for i_1 in the 2nd subinterval (equation ②) and replace ωt by $\alpha + 60^\circ$


$$\Rightarrow \frac{\sqrt{2}}{3} \frac{V}{\omega L} [\sin(\alpha + u - 60^\circ) - \sin \alpha]$$

$$= \frac{V}{\sqrt{2}\omega L} [\cos(\alpha + 60^\circ) - \cos(\alpha + u - 60^\circ)] + \frac{\sqrt{2}}{3} \frac{V}{\omega L} [\cos(\alpha + 150^\circ) + \sin(\alpha + u)] + I_d$$

$$\bar{I}_d = \frac{V}{\sqrt{2}\omega L} [\cos(\alpha - 30^\circ) - \cos(\alpha + u + 30^\circ)]$$

$$\bar{I}_d = \frac{\sqrt{2}V}{2\omega L}$$

$$\bar{I}_d = \frac{I_s}{\sqrt{3}} [\cos(\alpha - 30^\circ) - \cos(\alpha + u + 30^\circ)]$$



Now, if I take the currents i_1 and i_6 , see I have got the expression for i_1 and i_6 in the first subinterval I got the expression for i_1 in this second subinterval of course, in the second subinterval i_6 is 0 ok. So, can I relate i_1 and i_6 , see all the valve currents are identical except for a phase shift. So, if you take the 2 current valve currents i_1 and i_6 where identical expect for a phase shift. So, what is the phase shift between i_1 and i_6 ?

See whatever happens to i_1 would have happened to i_6 , 60 degrees ago say what some instant valve 6 is turned on means, after 60 degrees valve 1 is turned on after 60 degrees valve 2 is turned on ok. So, whatever happens to any valve say i_6 , valve 6 the same thing happens to one after 60 degrees same thing happens two after another 60 degrees and so on ok. So, if I take i_6 of $\omega o t$ it will be equal to i_1 of $\omega o t$.

Student: Plus 60 degree.

Plus 60 degrees not minus plus so, I mean is it plus or minus? i_1 is lagging i_6 by 60 degrees.

Student: Plus.

So, it is plus get this correct ok. Now, what I will do is, I will try to use the 2 equations which gives expression for i_1 in the first subinterval and the second subinterval. And I will replace this in this equation $\omega o t$ by α . So, if I take i_6 of α it is equal to i_1 of α plus 60 degrees. See the previous the first question is applicable for any value of $\omega o t$ ok. So, I just put $\omega o t$ equal to α .

Now, what I will do is, I will take the expression for i_6 in the first subinterval. So, I have the expression for i_6 in the first subinterval. So, it starts from α to α plus u minus 60. So, replace $\omega o t$ by α in the expression for i_6 and take the expression for i_1 in the second subinterval which is applicable from α plus u minus 60 to α plus 60. See what I am trying to do is, take the expression for i_6 in the first sub interval.

So, this is equation number. So, if you go back we got the expression for i_6 as equation number 3; this is equation 3 and replace $\omega o t$ by α . Then what I am saying is this equal to the expression for take the expression for i_1 in the. So, I want to use this equation i_1 at α plus 60 is i_6 is α . So, for that I have to take the expression for i_1 in the?

Student: Second.

2nd subinterval. So, the expression for i_1 in the 2nd subinterval is given by equation 5 so, this equation 5. And replace ωt by $\alpha + 60^\circ$ ok. So, what does this give? So, let me do this or I will take the expression for i_6 in the 1st subinterval and replace ωt by α ok.

So, wherever there is ωt I will just put α ok. So, what I get is $\frac{\sqrt{2}}{3} V \omega L \sin \alpha + u \sin 60^\circ - \sin \alpha$. So, that is the expression for i_6 in the first subinterval after replacing ωt by α .

So, this is equal to expression for i_1 just now I got the explanation for i_1 . So, this is equal to $V \frac{\sqrt{2}}{3} \omega L \cos \alpha + 60^\circ - \cos \alpha + u \sin 60^\circ$, plus $\frac{\sqrt{2}}{3} V \omega L \cos \alpha + 150^\circ + \sin \alpha + u$ plus I_d .

Now, I will leave it to you to simplify this equation some trigonometric manipulations have to be done. So, it can be shown that I_d , which is appearing as the last term on the right hand side is equal to $V \frac{\sqrt{6}}{3} \omega L$, into $\cos \alpha - 30^\circ - \cos \alpha + u$ plus 30° .

So, this I am leaving it to you to derive, its just simplification of the previous equation. Now, if you recall we defined a quantity called short circuit current at the peak value of short circuit current I_s . So, I_s the peak value of short circuit current is $\frac{\sqrt{2}}{2} V \omega L$. So, I can write the expression for I_d in terms of I_s as I_d is equal to $I_s \frac{\sqrt{3}}{3}$. So, I just replace $V \frac{\sqrt{2}}{3} \omega L$ by I_s that is all. So, its $I_s \frac{\sqrt{3}}{3} \cos \alpha - 30^\circ - \cos \alpha + u$ plus 30° .

So, this is the relationship between I_d , I_s α and u in the case of 3 and 4 valve conduction mode. So, we got similarly a relationship between I_d , I_s α and u for 2 and 3 valve conduction mode, this is applicable for 3 and 4 valve conduction mode.