

DC Power Transmission Systems
Prof. Krishna S
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture – 41

6 pulse LCC with resistance, inductance and voltage source on the DC side: Part 1

(Refer Slide Time: 00:31)

$$\begin{bmatrix} i_1(\frac{s}{\omega_0}) \\ i_6(\frac{s}{\omega_0}) \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} i_1(\frac{s}{\omega_0} + T_1) + \begin{bmatrix} I_d \\ 0 \end{bmatrix}$$
$$F = \begin{bmatrix} 0 \\ 1 \end{bmatrix}, G = \begin{bmatrix} I_d \\ 0 \end{bmatrix}$$



Now one can have more complicated circuits. So, the method actually is useful only for more complicated circuit. So, if I have on the DC side something other than a current source then it becomes more complicated.

Now, let us look at one circuit which is actually more complicated than the circuit, so we have seen so far.

(Refer Slide Time: 00:49)




So, the circuit I am considering now is on the AC side I have a 3-phase balanced voltage source. In each phase there is a resistance and an inductance; valves 1, 3, 5, valves 4, 6, 2.


Now, on the DC side, we consider a model consisting of a resistor, an inductor and a voltage source a DC voltage source. So, V_d is the voltage across this voltage source, R_d is the resistance, L_d is the inductors. So, we have the same expressions for e_a , e_b , e_c which we have been using $\frac{\sqrt{2}}{3} V \sin \omega t + 150$ degrees, e_b is $\frac{\sqrt{2}}{3} V \sin \omega t + 30$ degrees and e_c is $\frac{\sqrt{2}}{3} V \sin \omega t - 90$ degrees.

So, if I want to analyze this circuit. So, I can imply the general steady state analysis. So, let us try to do the steady state analysis; so, essentially finding x_1 , x_2 , a_1 , u_1 , a_2 , u_2 , f_g . So, let us start with the 2 and 3 valve conduction mode.

(Refer Slide Time: 04:14)



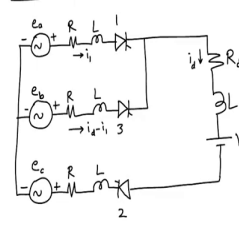2 and 3 valve conduction mode
1st subinterval



$$\begin{cases} e_a - e_b = R i_d + L \frac{di_d}{dt} - R(i_d - i) - L \frac{d}{dt}(i_d - i) \\ e_b - e_c = R(i_d - i) + L \frac{d}{dt}(i_d - i) + R_d i_d + L_d \frac{di_d}{dt} + V_d + R i_d + L \frac{di_d}{dt} \end{cases}$$

$$\begin{bmatrix} -L & 2L \\ 2L+L_d & -L \end{bmatrix} \begin{bmatrix} \frac{di_d}{dt} \\ \frac{di_d}{dt} \end{bmatrix} = \begin{bmatrix} R & -2R \\ -2R-R_d & R \end{bmatrix} \begin{bmatrix} i_d \\ i_d \end{bmatrix} + \begin{bmatrix} e_a - e_b \\ e_b - e_c - V_d \end{bmatrix}$$

$$A_1 = \begin{bmatrix} -L & 2L \\ 2L+L_d & -L \end{bmatrix}^{-1} \begin{bmatrix} R & -2R \\ -2R-R_d & R \end{bmatrix}$$

$$u_1 = \begin{bmatrix} -L & 2L \\ 2L+L_d & -L \end{bmatrix}^{-1} \begin{bmatrix} e_a - e_b \\ e_b - e_c - V_d \end{bmatrix}$$

$$x_1 = \begin{bmatrix} i_d \\ i_d \end{bmatrix}$$

So, if I take 2 and 3 valve conduction mode; so, if I take the first sub interval. So, there are 3 valves conducting in the first sub interval. So, I will show only those valves that conduct current. So, the equivalent circuit is like this. This valve 1, valve 3 and valve 2. This is i_d , sorry. We have a different circuit now on the DC side, so I have a resistance inductance and a voltage source. So, this is R_d , L_d , V_d . So, how many elements are there in the state vector x_1 ?

This is unlike the previous circuits where there was a constant current on the DC side. So, there is no longer a constant current or if I consider the current instantaneous current i_d it is not necessarily a constant. So, we cannot actually ignore the slope while I mean we have to include this loop consisting of R_d , L_d , V_d also in the equations.

So, if I take x_1 , then what are the elements of x_1 ? So, there are two loops, so there should be two elements. The first element is i_d and the second element is nothing but the current in the outgoing valve, the current the outgoing valve is nothing but i_1 , value 1 is outgoing valve. So, i_d and i_1 are the elements of x_1 .

So, let us try to write the equations for the circuit by applying Kirchhoff's voltage law and once we bring it to the standard form, we can get A_1 and e_1 . So, if I take the loop consisting of e_a , e_b , R and L in series with a , R and L in series with e_b and valves 1 and 3, then I have by Kirchhoff's voltage law e_a minus e_b is equal to $R i_1$ plus $L \frac{di_1}{dt}$. So, if I take the current here this is i_d minus i_1 , minus $R i_d$ minus i_1 , minus $L \frac{d}{dt}$ of i_d minus i_1 .

If I take the loop consisting of e_b , e_c , R and L in series with e_b , R and L in series with the e_c , the valves 3, 2, R_d , L_d , V_d . So, if I take this loop and apply Kirchhoff's voltage law, I get e_b minus e_c is equal to R into i_d minus i_1 plus $L \frac{d}{dt}$ of i_d minus i_1 , plus $R_d i_d$ plus $L_d \frac{di_d}{dt}$ plus V_d and the current through valve to R and L in series with e_c is nothing but i_d plus $R i_d$ plus $L \frac{di_d}{dt}$.

So, these are the two equations. So, we can write these equations in the standard form. So, I will write this as a equation in the vector metrics form. So, I will take the terms involving the derivative of the state variables, so $\frac{di_d}{dt}$, $\frac{di_1}{dt}$. So, let me first consider the terms involving $\frac{di_d}{dt}$ and $\frac{di_1}{dt}$, in these two equations, ok.

So, in the first equation if I take the coefficient of $\frac{di_d}{dt}$. So, there is a $L \frac{di_d}{dt}$ with a negative sign, so minus $L \frac{di_d}{dt}$. And if I look at the coefficient of $\frac{di_1}{dt}$, so there are two terms in valve I mean 2 times $L \frac{di_1}{dt}$ is appearing twice. So, $2L$ is coefficient of $\frac{di_1}{dt}$.

If I look at the second equation the coefficient of $\frac{di_d}{dt}$. So, I have $L \frac{di_d}{dt}$ plus $L_d \frac{di_d}{dt}$ [inaudible] plus $L \frac{di_d}{dt}$, so it is $2L$ plus L_d . So, $2L$ plus L_d is the coefficient of $\frac{di_d}{dt}$. Then the coefficient of $\frac{di_1}{dt}$ is minus L_d . So, I will equate this to the remaining terms on the other side. So, first I will take the terms involving i_d and i_1 . So, in the first

equation the coefficient of $i d$ is R , the coefficient of $i 6$ is sorry the coefficient of this is $i 1$ sorry, sorry. So, the coefficient of $i 1$ in the first equation is $\text{minus } 2 R$. In the second equation the coefficient of $i d$ is $2 R$ plus $R d$ with a negative sign. So, it is $\text{minus } 2 R$ minus $R d$. And the coefficient of $i 1$ is R .

Then there are other terms in both equations. So, in the first equation I have $e a$ minus $e b$. In the second equation I have $e b$ minus $e c$ minus $V d$. So, if I pre-multiply this equation by the inverse of this square metrics on the left hand side I get the equation in the standard form, so from that I can get $A 1$ and $U 1$. So, I can write $A 1$ as $\text{minus } L, 2 L, 2 L$, plus $L d$ minus L ; inverse R , $\text{minus } 2 R$, $\text{minus } 2 R$, $\text{minus } R d$, R . So, this is $A 1$. And $u 1$ is $\text{minus } L, 2 L, 2 L$ plus $L d$, $\text{minus } L$; inverse $e a$ minus $e b$ $e b$ minus $e c$ minus $V d$.