

DC Power Transmission Systems
Prof. Krishna S
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture – 44
Capacitor commutated converter: Part 1

So, today we will actually consider converter which is actually different from the other circuits we have seen so far. See, the converter is just a consisting of 6 valves, the ones which you have studied 6 pulse converters. But what is different in the circuits is the model of the AC side and the DC side ok.

Now, we will consider actually a different converter where the circuit of the converter itself is different. So, in addition to the 6 valves we will have what is known as a capacitors on the AC side. So, what we get is a capacitor commutated converter. So, a capacitor commutated converter is same as the line commutated converter with some addition.

(Refer Slide Time: 01:04)

Capacitor Commutated Converter

$C \frac{dV_c}{dt} = i_c$

$e_a = \frac{\sqrt{2}}{3} V \sin(\omega t + 120^\circ)$
 $e_b = \frac{\sqrt{2}}{3} V \sin(\omega t + 30^\circ)$
 $e_c = \frac{\sqrt{2}}{3} V \sin(\omega t - 90^\circ)$

α : Instant at which valve 3 is turned on
 $\alpha < \omega t < \alpha + 60^\circ$
 Voltage across valve 1
 $= e_a - V_a - e_b + V_b$
 $= e_a - e_b - V_m - V_m + \frac{3V_m}{\pi} (\omega t - \alpha)$

So, I have 3 legs corresponding to the three phases of the AC side and in each leg there are 2 thyristor valves. So, there is an addition of a capacitor in each phase on the AC side. So, there is a series capacitor on the AC side. So, we will call these valves as 1, 3, 5, 4, 6, 2.

So, there are two terminals on the DC side the DC side terminals and three terminals on the AC side. So, this is the circuit of a capacitor commutated converter. So, in addition to the 6 thyristor valves we have the 3 thyristor 3 capacitors.

So, again if I want to explain what is the necessity of having a capacitor. What we will do is we will try to take a circuit that is a model of the AC side and the DC side. The simplest model on the AC side is just a three phase voltage source the simplest model on the DC side is a constant current source.

So, first we will consider the simplest model. Of course, we will not be going into any detail model, but one can easily extend this to any other model of the AC side or DC side. So, I have a constant current I_d on the DC side the voltage the instantaneous voltage on the DC side is v_d and the AC side is represented by a three phase balanced sinusoidal voltage source.

So, the capacitance of all these capacitors is c . So, they are identical capacitors. So, e_a , e_b and e_c are three balance voltages. So, we will use the same expression for e_a , e_b , e_c that we have been using $\sqrt{2} \cdot 3 V \sin(\omega t + 150 \text{ degrees})$. e_b is $\sqrt{2} \cdot 3 V \sin(\omega t + 30 \text{ degrees})$ and e_c is $\sqrt{2} \cdot 3 V \sin(\omega t - 90 \text{ degrees})$. So, we already have a notation for the currents that are flowing on the AC side i_a , i_b , i_c .

We use some notations for the voltages across these capacitors v_a , v_b , v_c . So, I call this as v_a ; the instantaneous voltage across this capacitor in phase a similarly, this is v_b and this is v_c . So, we will analyse this circuit. So, in the process of course, we will see what is the purpose of having a capacitor on there on the AC side.

So, we know that a when there is no inductance on the AC side, the current can be changing suddenly. So, at any instant only two valves are conducting, either 1 and 2, 2 and 3, 3 and 4, 4 and 5, 5 and 6 or 6 and 1 ok. So, there are 6 intervals and in each interval we need two I mean one valve from the upper commutation group and one from the lower commutation group is conducted.

So, for the sake of explanation; we will try to look at one of the capacitor voltages. So, we have been using this notation α . So, what is α ?

Student: P is (Refer Time: 06:40).

So, it is instant at which valve three is turned on. So, instant is see though I say instant I mean it is angle ok, because our most of the times our independent variable is angle instant at which valve 3 is turned on.

So, let us try to plot the voltage across the capacitor in one of the phases say b phase. So, suppose I want the plot of v_b ok. So, if I want plot of v_b , what should I do? How can I get plot of v_b ? v_b is the voltage across the capacitor in b phase. So, how to get the capacitor voltage waveform?

Student: We write the KVL equation.

Why should I write KVL equation? I mean why?

Student: (Refer Time: 07:40).

What is the voltage see if I want the voltage across the capacitor can I not find the voltage by knowing the current, capacitance is known. So, can I not get the expression for v_b if i_b is known. Now what is i_b ? So, have we already seen the waveform of i_b ?

See, suppose the capacitors are not there we know i_b , now will anything change as far as the currents i_a i_b are concerned if these will these currents change due to the presence of capacitor is a question. See we said it is still 2 valve conduction mode.

Student: yeah (Refer Time: 08:20).


So, it is still 2 valve conduction mode. So, as long as it is 2 valve conduction mode let us assume 2 valve conduction mode than say it is allowed actually, 2 valve conduction mode is allowed here. So, that is the only thing 2 and 3 will not happen, because we will see that there is no inductance on the AC side. So, if these 2 valve conduction mode then we know the waveforms of i_a , i_b , i_c . So, what are the possible values of i_a , i_b or i_c ?

Student: It is i_d or minus i_d .

Its i_d or minus i_d or.

Student: 0 0.

(Refer Slide Time: 08:55)

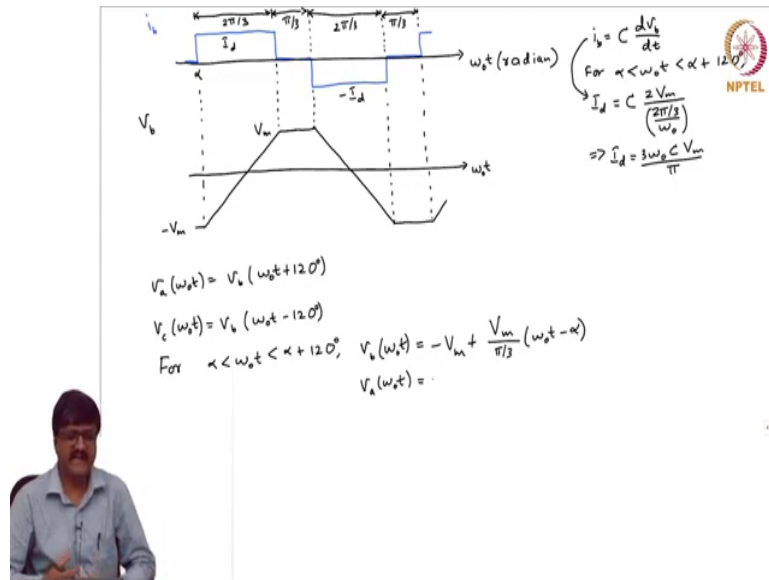

0 ok. So, suppose I take the waveform of i_b . So, let me plot i_b first. So, from i_b , I can get the other waveforms ok. What I will do is (Refer Time: 09:06). So, this is $\omega_s t$ suppose I plot i_b . I start plotting from α ok. So, at α , what is what is i_b ?

Student: id id (Refer Time: 09:37).

It actually goes from 0 to I_d , it goes from 0 to I_d . So, it is 0 at α till α and it goes to I_d and it remains at I_d for.

Student: 120.

For how many degrees?

Student: 120.

120 degrees, then it goes to.

Student: 0.

0, for how long it remains at 0?

Student: 60 degrees.

60 degrees. Then after 60 degrees it again goes to.

Student: Minus Id.

Minus id and it remains at minus Id for 120 degrees, then again it goes to 0. It remains at 0 for 60 degrees and then it becomes again Id and the cycle repeats ok. So, I have i b equal to Id or minus Id or 0. And this is alpha and this duration is. So, this duration is 120 degrees in radian it is 2π by 3. So, I will show this in radian. So, let me show these distances in radian.

So, this is π by 3, this is 2π by 3 and this is π by 3. So, if this is i b, what is v b? So, go back to the circuit see if you look at the circuit what is v b? V b can be related to ib.

Student: 1 by c (Refer Time: 11:50).

How v b and i b are related?

Student: 1 by c integral (Refer Time: 11:56).

1 by c.

Student: Integral i_b .

Integral i_b . So, I can write i_b as $C \frac{dv_b}{dt}$. So, I have to take a waveform for v_b such that its derivative is similar to i_b . Of course, except for that constant C . C is a constant. So, except for C , the derivative of v_b it should be similar to i_b . So that means; if I want v_b ok, let me use a different colour suppose I want v_b ok. So, how will v_b vary from α to $\alpha + 120$ degrees.

Student: (Refer Time: 12:39) α minus α .

It is a, it increases linearly.

Student: (Refer Time: 12:44) transfer function.

It is a linear function right it is ramp then from $\alpha + 120$ to $\alpha + 180$.

Student: decrease (Refer Time: 12:52) constant.

Decrease.

Student: Constant, constant (Refer Time: 12:54).

Constant, it is constant. Then when i_b is minus I_d negative then it decreases linearly then again for another sixty degrees it remains constant. Now the question is if I plot v_b it is like this let me so, it increases linearly then it remains constant for 60 degrees then for the next 120 degrees it decreases linearly then again it remains constant.

Then the cycle repeats it again starts increasing. So, before alpha it would have remained constant ok. So, let me just now what should be the average value of v_b ? What do you expect the average value of v_b to be ok? So, I forgot to use the what should be the average value.

Student: (Refer Time: 14:22).

Ha?

Student: Looks like it will be 0.

Looks like?

Student: It will be 0.

Looks like it will be 0. Why, why it should be 0? And that to are not certain.

Student: (Refer Time: 14:37).

Yeah, I am asking you to just guess ok. Why it should be 0?

Student: Because, i_b is like symmetry across (Refer Time: 14:50) so.

Sorry.

Student: v_d got average of voltage across thyristor to minus thyristor valves.

No. I see when I know current through the capacitor I need not worry about anything else in the circuit, say i_b is known to me i_b is known to me. So, when I know the i_b is the current through a capacitor. So, from i_b I am trying to plot v_b , but the only question that cant be answered using this i_b is what is the.

Student: Average value.

What is the average value? So, average value I mean; it should depend on the initial value. Now the question is even if initial value is not known can we plot v_b is the question.

Student: (Refer Time: 15:36).

Ha?

Student: (Refer Time: 15:39).

Sorry.

Student: Access.

What access?

Student: (Refer Time: 15:43).

I have not drawn because I do not know average. If I knew the average I would have drawn, I would deliberately not drawn the access omega or access that because I do not know the average.

Student: (Refer Time: 15:55).

So, what is the average?

Student: (Refer Time: 15:58).

Ha.

Student: t times (Refer Time: 16:01) steady state (Refer Time: 16:04).

T tends to.

Student: (Refer Time: 16:08).

See when in steady state what should be the average.

Student: Actually average will be 0.

Why?

Student: Because q is equal to 0 and the charge is current into time. So, we see that the same amount of charge is getting into the capacitor and the same amount is coming out so.

Yeah see.

Student: And also there is no charge.

Answer is; it depends on the initial charge of the capacitor, but what happens in practice is something different. See we have taken an ideal case if you look at the circuit that we have considered on the AC side, just a voltage source, that is an ideal case in practice it is an voltage source in series with inductor in series with.

Student: Resistor.

Resistor. So, whenever there is a resistor, you will see that there will be always decaying. So, any DC value will decay to 0. See the resistor will ensure that on the flow of the AC side any

DC value will decay to 0, because of the resistor. Now this resistor is something which is always present of course, we have not modelled it. So, we have ignored that ok. So, assuming that there is a very small negligible resistance we can always say that the steady state waveform.

So, I am always trying to plot only steady state waveforms no transient no transient analysis done here. So, steady state waveform will have a average value of 0 ok. So, that cannot be inferred from the circuit that I have drawn. So, that can be inferred only by the fact that there is always a resistance only thing is we ignore that resistance that is all. So, the plot is something like this where the average value happens to be 0.

Student: Sir that argument is not valid.

Which one?

Student: The same charge is going in and out (Refer Time: 17:58).

See if when you just take a circuit without resistor it is only dependent with their initial charge is say 0 ok. So, it can have a nonzero average value. It can have a nonzero ok. Let me just slightly deviate let me slightly deviate.

(Refer Slide Time: 18:25)

The slide contains the following content:

- Circuit Diagram:** An AC voltage source labeled $\sin(\omega t)$ is connected in series with a switch and a 1H inductor. The switch is shown closing at $t=0$. The current through the inductor is labeled i .
- Handwritten Notes:**
 - At $t=0$ $i=0$
 - $i = 1 - \cos(\omega t)$
 - $i = -\cos(\omega t)$ in steady state
- Plots:**
 - The top plot shows the source voltage $\sin(\omega t)$ as a sine wave starting at the origin (0,0) and increasing.
 - The bottom plot shows the current i as a horizontal line at 0.
- NPTEL Logo:** Located in the top right corner of the slide.

I have this circuit ok. I have an inductor suppose, this is $\sin \omega t$ suppose this is 1 henry, the switch is close to $t = 0$ then the current flows after closing the switch. So, if I plot the $\sin \omega t$, I know $\sin \omega t$ it is like this this is $\sin \omega t$ this is 0. Now, what will be the plot of current?

Student: Minus $\cos \omega t$ (Refer Time: 19:16) 0.

Ha minus?

Student: Minus $\cos \omega t$.

Minus, do you get minus $\cos \omega t$ if you solve this circuit. See the circuit as a solution say at t equal to 0, I is equal to 0, that should be satisfied. Because switch is closed only at t equal to 0. So, there is no current before closing the switch. So, if you take $\cos \omega t$ or $1 - \cos \omega t$ is expression for I there is a problem.

Student: (Refer Time: 19:43) minus.

So, it is.

Student: $1 - \cos \omega t$.

$1 - \cos \omega t$, $1 - \cos \omega t$. So, if I is $1 - \cos \omega t$, what is the average value?

Student: Average value.

Average value of I is 1. Now, if this goes against what I mean does it go against what we have learned already. See AC circuit the current should just lag the voltage by 90 degrees.

Student: Yes.

But it is not just lagging, it is lagging and getting shifted vertically upwards.

Student: Yes (Refer Time: 20:20).

Now, that is because this is a I mean there is no resistance. So, the DC value is not decaying. See if there is a very small resistance steady state would have been the one the waveform which we expect. Now this is actually an ideal circuit we have ignored the resistance it is not that resistance is 0, we have ignored it. So, in any circuit that we study in engineering when we say a resistance is not there it means that it is not that, it is not there it is ignored it is a

small value that is all. So, when we plot the waveform, we still say that it I mean I is minus cos omega ot in steady state.

So, what I want is in steady state ok. So, so it is because if I just look at this circuit the solution is $1 - \cos \omega t$, but if this circuit represents some physical circuit in practice then it is an approximation. So, yeah we are not worried say to start with in a I mean study some circuits which are by itself, but as we go on we are only considering circuits which represent some physical system.

So, when you are considering a circuits with represent some physical system resistance equal to 0 does not mean there is no resistance, it just means resistance is negligible, that is all ok. So, the steady state waveform will be equal to minus cos omega ot because resistance is ignored that is all. I hope it is clear, please note that. There is a difference between studying the this circuit as a circuit by itself and studying the circuit as a representation on of some physical arrangement that is all.

So, what we are considering is a physical arrangement. Please note we are not considering some imaginary circuit, it is a what we are studying is representations of some actual circuits which are there in practice. So, by that argument v_b is a waveform which has a 0 average value ok. Now the question is can we get a v_a , v_c . What is v_a ? Can I get v_a , v_c I mean in terms of v_b . So, v_a can be set to be identical to v_b except that there is a phase shift phase shift of.

Student: (Refer Time: 22:51).

120 degrees. So, can I say that v_a is v_b of to be very precise what I should do is I should write v_a of omega ot is equal to v_b of omega o t.

Student: Minus sir no sir plus.

Plus or minus?

Student: (Refer Time: 23:15).

Plus or minus?

Student: Plus.

Plus. Similarly, v_c of ωt is v_b . Now, why I write in terms of v_b so I have shown v_b we have got v_b that is all is ωt minus 120 degrees. So, just take v_b and shift it by 120 to the right you get v_c to the left you shift it you get v_e that is all ok.

So, now let us come back to this. Now the question is what is the purpose of capacitor. So, can you guess why I have put a capacitor. And there is a purpose. So, which is actually hinted by the name itself capacitor commutated converter.

Student: (Refer Time: 24:02).

Sorry,

Student: To remove any DC (Refer Time: 24:05).

To remove any?

Student: DC from the voltage source.

Dc from where.

Student: Voltage sources.

Voltage source is perfectly sinusoidal. No if you are familiar with this term of commutation what is commutation?

Student: (Refer Time: 24:22) current from.

A current gets transferred from one valve to another. Now to get that current transfer one valve should turn off actually. So, the turning off is also I mean you would have studied commutation to be the word used even for turning off of a valve. Only when it turns off the current that was flowing in that valve would go which shift to the another valve.

So, capacitor is seen to help that commutation process. Now when is commutation a problem. So, inverter operation is actually the operation for which the commutation margin angle will be small. So, we will see that for inverter operation this having a capacitor on the AC side will help ok.

So, let us see how it helps. So, alpha is the instant at which valve 3 is turned on. Now if I take the duration alpha to alpha plus 60 degrees ok. Now, for this duration valve 1 would have just been turned off ok. So, what is the voltage across valve 1? It should be negative for a long duration that is what we want. So, what is the voltage across valve one in this interval alpha to alpha plus 60.

So, we can try to get a get the expression for voltage across valve 1 from this circuit. So, alpha to alpha plus 60 means; valve 3 is conducting. So, it is irrelevant whether valve 2 conducts or not, valve 3 is conducting. So, by Kirchhoff's voltage law valve 1 is not conducting it has stopped conducting. So, the voltage across valve 1 is e_a minus.

Student: e_a minus v_a .

e_a minus v_a .

Student: Minus e_b .

Minus e_b .

Student: Minus.

Plus.

Student: Plus.

Plus v_b ok. So, let us plot let us try to get the expression for v_a and v_b . So, it is e_a minus e_b what is v_a what is the expression for v_a say we already have the waveform of v_b ok. So, let me try to get the expression for v_b for α to $\alpha + 120$ degrees.

What is v_b ? Ok. So, what I will do is, I will try to denote this minimum value as minus V_m , m for maximum value maximum value is plus V_m , V_m is positive. Of course, we can get an expression for V_m itself in terms of $i_d c$ and ωt_0 what is the what is the relationship between V_m $i_d C \omega t_0$.

See we know that i_b is $C dv_b$ by dt ok. Now if I take ωt between α and $\alpha + 120$ or 60 or 120 . So, up to 120 $\alpha + 120$, what is i_b ? i_b is.

Student: i_d .

i_d . So, this equation can be written as $i_d C dv_b$ by dt . So, v_b goes from minus V_m to.

Student: Plus V_m .

Plus v_m . So, the change in v_b is $2 V_m$ divided by the time taken. So, it is linear in fact, it is linearly increasing. So, the slope is constant for this 120 degrees. So, what is the duration? What is the duration?

Student: (Refer Time: 28:42).

See what I am trying to do is I am just writing the right hand side $C \frac{dv_b}{dt}$. So, $\frac{dv_b}{dt}$, the rate of change of v_b with respect to time.

Student: 120 degree equal to (Refer Time: 28:53).

It is 120 degree. So, I mean. So, 2π by 3 in radian by.

Student: Omega.

Omega ω , is that? So, the time is angle divided by the angular frequency. So, this actually simplifies to I_d is equal to $\omega C V_m$ into 3 divided by π ok

So, I can relate I_d ωC and V_m yeah based on. So, can I write the expression for v_b for α to $\alpha + 120$. In terms of V_m , it is easy to write in terms of V_m . So, that is why I introduced a notation V_m .

So, what is v_b in terms of V_m see it is just a straight line segment say from α to $\alpha + 120$, v_b is a straight line segment. What is the equation of the straight line segment? That is all I am asking.

Student: (Refer Time: 30:10).

Student: v_b .

V ?

Student: V_m .

V_m into.

Student: $2\omega \sin(\omega t)$ (Refer Time: 30:35) minus $\omega \sin(\omega t)$.

Sorry.

Student: (Refer Time: 30:41).

See, I want it as a function of ωt that is all $C \cos(\omega t)$ as a function of ωt .

Student: $I \cos(\omega t)$.

We need not I mean it is easy to write it in terms of V_m instead of writing it in terms of I . So, let us write it in terms of V_m .

Student: $\sin(\omega t)$.

$\sin(\omega t)$.

Student: $\cos(\omega t)$.

$\cos(\omega t)$.

Student: $V_m \sin(\omega t)$.

$V_m \sin(\omega t)$.

Student: $V_m \cos(\omega t)$.

$V_m \cos(\omega t)$.


Student: Into omega t minus alpha.

Omega t minus?

Student: Minus alpha.

Minus alpha, that is all. That is the equation of a straight line. So, we know the expression for v_b . So, let me come back to the previous page. See why I want this expression for v_b . So, I want the voltage across valve 1, voltage across the outgoing valve from alpha to alpha plus 60. So, that is in terms of v_a and v_b . So, we got the expression for v_b . what is the expression for v_a ? What is the expression for v_a ? We know that v_a and v_b are identical except that v_a leads v_b by 120 degrees it may be easier.

(Refer Slide Time: 32:06)

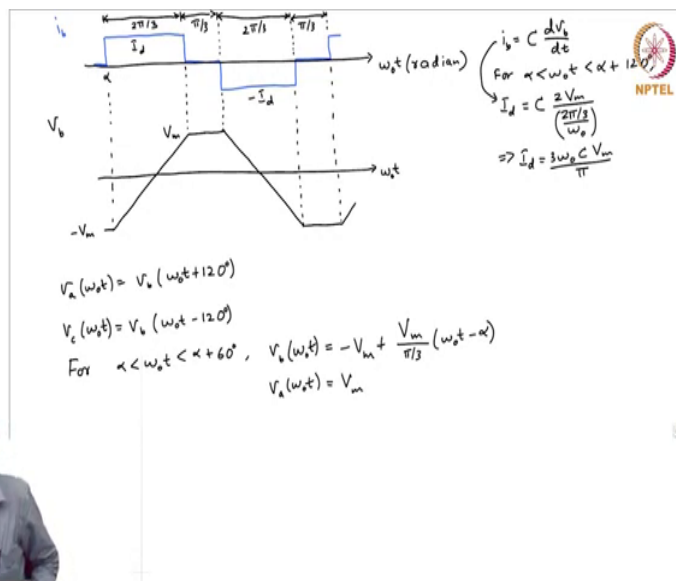

If I instead of taking it up to 120° if I make it $\alpha + 60^\circ$. It may be easier to write the expression for v_a . What is v_a ?

Student: Minus

Student: (Refer Time: 32:25) depends the α ..

Why should it see that is what I am saying from α to $\alpha + 60^\circ$, what is v_a ?

Student: (Refer Time: 32:40) v_b from α plus 2α .

Hmm So, what it is.

Student: V_m .

It is nothing but?

Student: V_m .

V_m . See from α to $\alpha + 60^\circ$ v_a is V_m see you have v_b shifted to the left by. By how much?

Student: 120° degree.

120° to get v_a , you have to shift it we shift v_b to the left by 120° . So, for α to $\alpha + 60^\circ$ v_a is equal to.

Student: V_m .

V_m . So, we have the expressions for v_a and v_b for α to from α to $\alpha + 60$. So, substitute this in the expression for voltage across valve 1. So, I have minus v_a is nothing, but minus V_m and minus sorry, not minus v_b plus v_b . So, plus v_b is minus V_m plus $3 V_m$ by π omega α minus α . So, this is the expression for voltage across valve 1. Now what is the voltage across valve 1 without a capacitor?

Student: e_a minus e_b .

It is e_a minus e_b . So, with the addition of a capacitor there are a few more terms. Now because of these few more terms will the voltage across valve one be negative for a longer duration.

Student: (Refer Time: 34:32).

(Refer Slide Time: 34:51)

For $\alpha < \omega t < \alpha + 60^\circ$

(LCC) Without capacitor, voltage across valve 1 = $e_a - e_b$

(CCC) With capacitor, voltage across valve 1 = $e_a - e_b - 2V_m + \frac{3}{\pi} V_m (\omega t - \alpha)$

Voltage across outgoing valve is negative for a longer duration compared with that for LCC.

\Rightarrow Permits operation with α close to 180°

$\alpha < \omega t < \alpha + 60^\circ$

$V_a = ?$

$V_b = ?$

RMS value of fundamental component of voltage across capacitor = ?

NPTEL

Let me summarize here. See what I am trying to say is without capacitor ok. So, we are only talking about alpha to alpha plus 60 degrees. So, for one interval for which what is the I mean we want to see what happens to the voltage across valve 1. So, without capacitor, voltage across valve 1 is $e_a - e_b$. With capacitor; that means, for a capacitor commutated converter see without capacitor means it is LCC Line Commutated Converter this is LCC.

So, capacitor commutated converter CCC is. In fact, an abbreviation for capacitor commutated converter. So, with capacitor voltage across valve 1 is in addition to this $e_a - e_b$ I have minus $2V_m$ plus $\frac{3}{\pi} V_m (\omega t - \alpha)$ yeah. Now, what we want for the voltage across valve one it should be as.

Student: Negative.

As negative as possible for a long I mean for as long a duration as possible. Now first of all do you see that this voltage across valve 1 with capacitor is more negative.

Student: Yes.

Minus $2 V_m \sin 3 \pi \omega t - \alpha$ do you see that it is negative.

Student: Yes.

So, it is always negative. For α to $\alpha + 60$, it is negative. So, due to that it takes longer for the voltage across valve one to become positive. So, it helps in commutation that is all. So, that is the idea. So, the purpose of capacitor is only that ok. So, for inverter operation we can go for α closer to 180. So, in the in the previous case of LCC, there was a limit on α . So, one cannot go to values up to close to 180. So, now, we can go even with I mean even for inverter operation.

So, voltage across outgoing valve. So, though I have taken just the example for a valve 1, any outgoing valve is negative for a longer duration ok. So, this is compared with the the situation of LCC, compared with that for LCC ok.

So, this means that it permits operation with α close to 180 close to 180. We have the expressions for v_b and of course, from that I can get the expressions for v_a and v_c can I get the expression for DC side voltage v_d and from that get the expression for the average v_d . See what is the instantaneous v_d . First of all one has to note that what will be the time period of minimum possible time period of v_d .

Student: 60.

60 degrees, 60 degrees. So, if I can get for any interval say α to $\alpha + 60$, what is v_d ? So, for α to $\alpha + 60$, what is v_d ? Then from that get the average Value of v_d ok. So, I would suggest that you please try to get these things. Now, there are a few other things

which are very easy I would also suggest that try to get the expression for RMS value of voltage across capacitor I mean to be precise RMS value of fundamental component of voltage across capacitor ok.

So, please try to get these expressions. I think they are straightforward, I will not be trying to do the I mean do I mean I will not be trying to do this in the class, but I will give the answers ok.

So, we will stop here we will continue the discussion on this in the next class.