

DC Power Transmission Systems
Prof. Krishna S
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture – 09
Analysis of 6 pulse LCC neglecting inductance

So, we will start with a simplified circuit where I have a converter with 3 legs.

(Refer Slide Time: 00:29)

NPTEL

Gate current is continuously applied
 \Rightarrow Thyristor behaves as a diode

$$e_a = \frac{\sqrt{2}}{3} V \sin(\omega t + 150^\circ)$$
$$e_b = \frac{\sqrt{2}}{3} V \sin(\omega t + 30^\circ)$$
$$e_c = \frac{\sqrt{2}}{3} V \sin(\omega t - 90^\circ)$$

And in each leg there are 2 thyristor valves. So, there are 3 leg shown here and in each leg we say there are 2 thyristor valves. So, they there are two ways of saying, one is one can say that a converter consist of 2 basic commutation groups connected in series or there are 3 legs which is the usual term used in many books, 3 legs connected in parallel.

So, there is 1 leg corresponding to each phase of the ac side. So, we denote the 3 phases by the letters abc. So, I have on the ac side a balanced 3 phase voltage source. So, let me call this

voltage e_a , this voltage is e_b and this is e_c . So, the valves are numbered as 1 3 5 4 6 2. On the dc side, the representation is a current source which is constant. So, I have a constant current I_d on the dc side the voltage across, the dc side terminals is V_d ok.

So, this is the simplest circuit where I actually ignored the inductance on the ac side. So, let us try to analyze this. So, we saw that in the in the last class I can divide the converter into 2 basic commutation groups; upper commutation group and a lower commutation group. 1 3 5 from the upper commutation group, 4 6 2 valves form the lower commutation group. Now, at any instant only one thyristor valve in any commutation group conducts, that is one among 1 3 5 and one among 4 6 2 ok.

Now, for the sake of simplicity what we will do is, we will assume that gate currents are continuously given ok. So, if gate currents are continuously given it is as good as thyristor acting as diodes ok. So, if I say gate current is continuously applied. This is as good as saying that thyristor behaves as a diode. So, behaving as a diode means if it is forward by a state conducts, if it is reverse bias state stops conducting ok.

Now, the question is in any commutation group 1 3 5 or 4 6 2 which is the thyristor valve that conducts? Suppose, I take the commutation group 1 3 5, so how do we decide which one of the 3 valves 1 3 5 conducts at anytime? If you notice the cathodes of all these thyristor valves 1 3 5 are at the same potential. So, the one that conducts is the one with which has the highest potential for the.

Student: Anode.

Anode. Similarly, if you take the lower commutation group 4 6 and 2 the anodes are at the same potential. So, the one that conducts is like one which is having the least cathode potential ok. So, that is the idea ok. So, of course, one has to note that I mean of course, 1 can verify when 1 of the thyristor valves; 1 of the thyristor valves is conducting, the other 2 thyristor valves are reversed bias ok. So, that will verify it ok.

So, we will assume some expression for this e_a , e_b , e_c . So, I said they are balanced sinusoidal; that means, they are having the same RMS value or peak value and the phase angle difference between e_a and e_b or e_b and e_c or e_c and e_a is 120 degrees ok. So, let me assume some expression for e_a , e_b , e_c . Now, the only choice I have is assuming the absolute phase angle, I have no choice over the relative phase angle. So, any two voltages will have a phase shift or phase difference of 120 degrees.

So, I will use this expression $\sqrt{2} \cdot 3 V \sin(\omega t + 150^\circ)$. I could have chosen any angle instead of 150, I mean any arbitrary angle can be chosen, but I'm choosing 150 for some reason; it will be a bit convenient for me as we will see ok. So, V is a constant, ω is a constant. So, it is a sinusoidal waveform. So, what is this V ? So, if I say this is the expression for e_a , what is V ?


Student: It is the RMS.

Student: Value.

RMS value of line to line voltage. So, please note the 3 voltages e_a , e_b , e_c , the 3 voltage sources single phase voltage sources are connected in a star. So, if you look at the line to line voltage it as an RMS value V ok, so that is e_a . So, once I have e_a , I choose I mean I have no choice over e_b it has the same RMS or peak value.

And it lags e_a by 120 degrees. So, this is $\sin(\omega t + 30^\circ)$. And e_c lags e_b by 120 degrees. So, it is $\sqrt{2} \cdot 3 V \sin(\omega t - 90^\circ)$ ok. So let me try to draw the waveform of e_a , e_b and e_c .

(Refer Slide Time: 07:37)

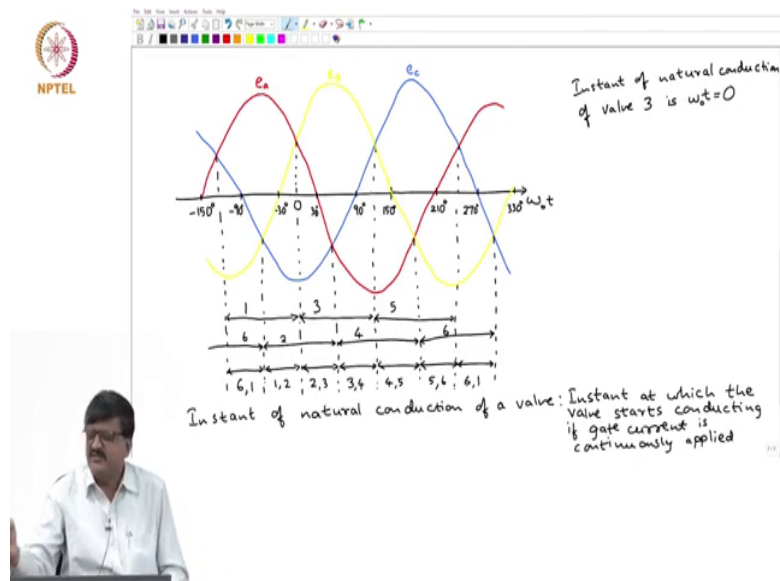

Suppose so this is e b is the yellow line visible ok. Then e c lags e b by 120 degrees ok. So, since it is free hand drawing please not all these wave forms are sinusoidal wave forms, though it may not slightly appear like that and they are balanced; that means, they have equal I mean equal peak values. So, this is e c ok.

So, I will mark some angles on the axis. So if I try to take this instant as 0. The instant at which e a and e b are positive and equal in value. So, what will be the instant at which e a is having a 0 crossing from negative to positive. Please note our expression for a is this, it is $\sqrt{2} \times 3 \text{ V} \sin \omega t + 150$ ok. So, this will be minus.

Student: Minus 150.

150. So, what I have shown is every 60 degrees, so this is minus.

90 degrees. This is minus 30, this is plus 30, this is 90, 150, 210, 270 and 330. So, I have shown every 60 degrees, only I mean only thing is I have showed an additional instant 0 also ok.

Now, just now we saw that if I look at the commutation group consisting of valves 1 3 5. At any instant, the valve with the highest anode potential conducts. So, let us try to see or let us try to first mark the instants of the conduction of different valve, so based on the one with the highest anode potential.

So, if I take this instant ok; so if I take this instant and if I take this instant. Now, from this instant to this instant, can I say one of the thyristor valves in the upper commutation group has the highest anode potential? Among 1 3 5; among 1 3 5 which one has the highest anode potential?

Student: 1.

1, so it is 1. Similarly, from here to here from this instant to this instant one of the thyristor valves among 1 3 5 has the highest anode potential that is?

Student: 3.

That is?

Student: 3.

3. And again from this instant to this instant the thyristor valve 5 is at the highest potential ok. So, now, we know which one among the thyristor valves of the upper commutation group conducts. So, if you have noticed we have considered one full cycle 360 degrees. So, we

started from minus though I have not marked it is minus 120; minus 120 and we go up to not again marked here between 210 and 270 there is a 240.

So, minus 120 to 240, so for one full cycle 360 degrees of the ac side. We have noted which thyristor valve of the upper commutation group conducts. Now we have to also find out which one among the lower commutation groups conducts ok. So, I will just extend these lines. So, this is corresponding to 1, this is corresponding to 3 and this duration is corresponding to 5 ok.

Now, to find out which one among the lower commutation group conducts, I take this instant and this instant ok. Suppose I take the duration though I have not marked minus 60 to plus 60; minus 60 to plus 60 so from this point to this point. So, there is one thyristor valves which is the least cathode potential which one is that?

Student: e c.

From here to here.

Student: (Refer Time: 14:42) e c.

Sorry.

Student: Seconds.

Yeah please go to the circuit 4 6 2 which one among these? 2, so it is 2. Again from 60 degrees to 180 degrees, so for this duration. One of the thyristor valves is at the least cathode potential 4 and from 180 degrees to 300 degrees, it is 6. Now, though I have not shown for the duration up to 60 degrees sorry up to minus 60 degrees. So, if I take this duration again this is of 120 degree width, but I am not showing the entire duration. So, if I take for this duration which is up to minus 60 degrees, which thyristor valve is conducting?

Student: 6.

6, ok. Now, again I have covered 1 cycle see if you look at the durations for which either 2 4 or 6 conducts I mean the total duration is 360. Now, what we will do is we will try to consider intervals of length 60 degrees. Suppose I take this or this or this all these are intervals of duration 60 degrees ok.

So, at any instant one thyristor valve in the upper commutation group conducts; one thyristor valve in the lower commutation group conducts. So, in the first 60 degree interval it is 1 and 6 ok. So, instead of writing 1 and 6 I say, 6 and 1 6 comma 1. Then in the second interval of 60 degree duration it is 1 and 2. Then it is 2 and 3, then it is 3 and 4, then it is 4 and 5, then it is 5 and 6. Now, that actually completes one cycle. So, if you go to the next interval it is corresponding to the next cycle again this same sequence follows.

Now, what we have done here is first of all we should note that we have assumed that the thyristors are acting as diodes. So, continuous gate current is applied so, thyristors are acting as diodes. So, we will go to the general case of thyristors are acting for as devices for which they are they are used to ok. See; obviously, if I use thyristors I invest more money than that I do for the diode and obviously, it is used for control purpose ok.

So, there is a provision to delay the instant of giving the gate pulse. So, actually gate current is not continuously applied gate current pulse is given so, that I can delay the instant of turn on. So, that I get some control over some quantity ok.

So, essentially I can get control over say the DC voltage, for a given AC voltage I can get control over the average value of the DC side voltage ok. Now, we define one thing which is called instant of natural conduction. Now. this is a quantity which is defined for any valve any of the 6 valves so, instant of natural conduction of a valve. So, what is this instant of natural conduction of a valve? It means the instant at which the valves start conducting; if the gate current is continuously applied. So, that is the definition.

So, this is instant of or instant at which, instant at which. So, please note this is defined for each and every valve all the 6 valves. So, if I take one particular valve the instant of natural conduction of that valve is nothing, but the instant at which the valves starts conducting; instant at which the valve starts conducting provided I give continuous gate current ok.

So, if gate current is continuously applied; continuously applied. So, that is the definition of instant of natural conduction of a valve ok. Let us see for one of the valves, what is the instant of natural conduction. Suppose I take the instant of natural conduction of say valve 3. So, we I mean the independent variable is normally the angle ωt . So, though we say instant we refer to even ωt as well ok. So, ωt is equal to.

Student: 0.

0. So, you see that at ωt equal to 0, 3 starts conducting. So, the instant; at which, 3 starts conducting is ωt equal to 0. Now, this is the instant at which its starts conducting if gate current is continuously applied ok. So, what we do in practices instead of continuous gate current; gate current pulses are actually applied which are delayed by a certain angle. Say it is as good as applying see there is one more equivalence instead of continuous gate current diode operation is possible even if I just apply gate pulse at.

Student: At the right instant.

At the right instance. So, in the case of ah valve 3 if I apply the gate pulse at ωt equal to 0.

Student: 0.

And the next gate pulse for the same valve.

Student: At for 60 degree (Refer Time: 21:32).

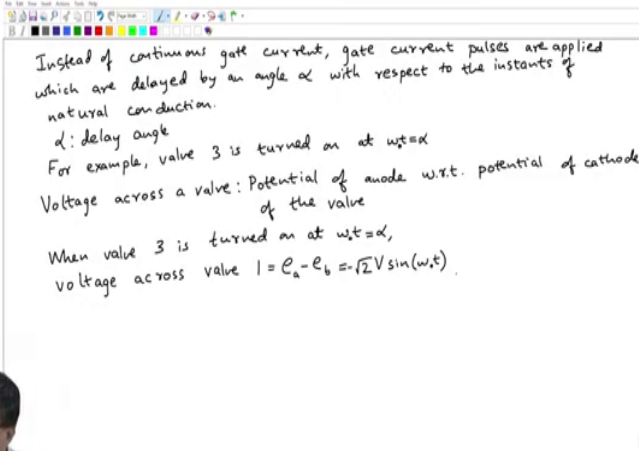

At the for the same valve, I am talking about the same valve.

Student: 180 degree.

Student: 180, 360 degree.

360 degrees. See you apply gate pulse only once in one cycle. So, say there is a diode operation possible even with gate pulse, if I apply a gate pulse to valve 3 at ωt equal to 0, 360, 720 and all multiples of 360 ok. So, similarly for each valve instead of giving continuous gate current, I can apply gate pulses every 360 degrees at the appropriate instant to get diode operation ok. So, what is actually done is not is neither a continuous gate current, nor gate pulse to achieve diode operation ok.

(Refer Slide Time: 22:20)




Instead of continuous gate current, gate current pulses are applied which are delayed by an angle α with respect to the instants of natural conduction.

α : delay angle

For example, valve 3 is turned on at $\omega t = \alpha$

Voltage across a valve: Potential of anode w.r.t. potential of cathode of the valve

When valve 3 is turned on at $\omega t = \alpha$,
voltage across valve 1 = $e_a - e_b = -\sqrt{2}V \sin(\omega t)$.



So, we want to how control so, what we do is instead of continuous gate current, what is actually done is, gate current pulses gate current pulses are applied which are delayed by an angle; so which are delayed by an angle. So, we give a notation for this angle alpha. Now, this delay is measured with respect to the instant of natural conduction ok. So, by an angle alpha with respect to the instants of natural conduction.

So, for this converter there are 6 thyristors valves so; that means, there are 6 instants of natural conduction. Now, for each thyristors valve we delay the instant of gate current pulse by the same angle. Please note this alpha is not different for different valves. So, alpha is same for all the valves ok. For all the 6 valves they delay is same so, that is denoted by alpha.

So, there is a name for this I mean alpha is called delay angle ok. So, for example, if I take valve 3; for example, if I take valve 3, valve 3 is turned on; that means, gate per gate current pulse is given at so, if the delay angle is alpha what is the instant of the gate current pulse or the instant of turn on for valve 3. See what was the instant for of natural conduction for valve 3?

Student: 0.

0. So, this will be I mean the instant of turn on in general is $\omega t = \alpha$. See if you take valve 4, what is the instant of natural conduction for valve 4?

Student: 60.

60 degrees.

Student: 60 degree.

60 degree. So, the valve 4 is turned on at 60 plus alpha. The instant of natural conduction for valve 4 is 120. So, valve 5 is turned on at 120 plus alpha so on ok. So, for valve 3 it is alpha, just alpha ok. So, what happens to the valve which was conducting earlier, say valve 3 is

turned on at ωt equal to α . What was the valve that was conducting before valve 3 is turned on?

Student: (Refer Time: 25:27) valve.

Which valve was conducting; valve 1. So what happens to that?

Student: Has to turn off.

That will turn off it gets reversed biased. So, it gets reversed biased and it turns off. Now, this is irrespective of whether I give continuous gate current or gate pulse, it is irrespective of that. Say initially I considered continuous gate current I mean to explain the operation that was operation as if everything is work I mean all valves are working as diodes.

So, irrespective of continuous gate current or gate pulses as soon as valve 3 is turned on and it starts conducting valve 1 will turn off. And of course, one can verify that it is reversed biased, is it not reverse biased what will be the voltage across valve one as soon as valve 3 is turned on.

Student: E_b minus e_a .

E_b minus e_a . So, what happens to e_b minus e_a .

Student: Actually, I know cathode will be a minus e_b , but a minus.

Yeah.

Student: E_b will be negative.

Say we define one quantity here for convenience voltage across a valve; voltage across a valve; whether it is valve 1 2 3 4 5 or 6. By definition it is the potential of anode so every

time I will not say the potential of anode with respect to cathode. So, I will just say voltage across valve 1, potential of anode with respect to cathode of the valve. So, I was asking what happens to the voltage across valve 1, when valve 3 is turned on.

Student: (Refer Time: 27:23).

Let us find out the expression for voltage.

Student: C_a minus c_a .

So, when valve 3 is turned on at ωt equal to α , turned on at ωt equal to α , then the voltage across valve 1 voltage across valve 1 is equal to. So, let us go back to the figure the circuit diagram.

So, 3 is turned on; so 3 is turned on means the valve 3 acts as a short circuit. See, we are assuming ideal thyristors. So, the voltage across the thyristors or thyristors valve is 0, when it is on or when it is conducting ok. So, this is a short valve 3 is a short. So, what is the voltage across valve 1?

Student: P_a minus; p_a minus.

It is anode potential minus cathode potential. So, it is e_a minus.

Student: e_b .

e_b . So, it is e_a minus e_b which can be obtained from the circuit diagram, e_a minus e_b . Now, we have expressions for e_a and e_b . Now, using the expressions for e_a and e_b can I say what is e_a minus e_b . E_a is having a phase angle 150° , e_b is having a phase angle of.

Student: $\sqrt{3} V$.

30.

Student: $\sqrt{2} V$.

$\sqrt{2}$ first of all this is a line voltage please note $e_a - e_b$ is line voltage. So, the peak value is $\sqrt{2} V$.

Student: $\sin \omega t$.

$\sin \omega t$.

Student: 180.

180. So, can I say that it is $-\sqrt{2} V \sin \omega t$.

Student: minus (Refer Time: 29:21).

Ok. Now, for the time being let us assume that, α is taking such a value that voltage across valve 1 is actually negative as soon as it stops conducting ok. So, then what should be the range of α ?

Say α can be 0, see α is equal to 0 corresponds to diode operation. Now, if α is increased ok. Now, beyond a certain value what happens to voltage across valve 1? See please note this voltage across valve 1 is negative only for ωt less than; less than?

Student: (Refer Time: 30:14).

Look at the expression $-\sqrt{2} V \sin \omega t$; it is negative only from 0 to.

Student: 0 to $\pi/2$.

Pi by 2. Is it pi by 2?

Student: 1.

0 to?

Student: 0 to pi.

0 to pi ok. So, for the time being we will assume that alpha is close to 0 ok. We will consider the general case shortly. So, if alpha is say close to 0 ok, so then as soon as valve 3 is turned on voltage across valve 1 is negative as soon as it stops conducting ok. Now actually that is a mandatory requirement because if the voltage across valve 1 is not equal to a negative value for a certain minimum duration then it will again start conducting without gate pulse.

Student: It is because the current is not (Refer Time: 31:06).

So, that is a property of a thyristor I will not get into the device physics here. So, I mean I do not know whether you are familiar with that. A thyristor will actually start conducting again, see one the thyristors once it stops conducting because current goes to 0 ok.

So, if it currents goes to 0, it starts conducting sorry current goes to 0 it stops conducting. Then as soon as it stops conducting the voltage across the thyristors should be negative, that is anode to cathode voltage should be negative. If it becomes positive it is forward biased and without gate current it will start conducting, if it is not negative for a certain minimum duration ok.


So, that is one property of thyristors which we have to consider in this course of course, in the analysis of any converter though we are assuming ideal thyristors. See please note in other ways it is ideal, but as far as this aspect is concerned we have to take that practical operation of thyristors here. So, there is a certain minimum duration say we do not want the thyristors to

conduct as soon as it is forward biased; we want the thyristors to conduct when we want, that is when we give the gate current pulse.


So, if it conducts just because it is forward biased than the control is lost ok. So, whenever a thyristors valve stops conducting then there is a minimum duration for which the voltage across the thyristors valve should be negative. If that is not maintained if it again becomes positive, the thyristors starts conducting again without gate pulse ok.

So, this is something we will come back again ok. So, we will come back to that analysis again. Now, what we will do is we will try to look at the different intervals that we have seen in the previous page see there are 6 intervals in one cycle each interval is off duration 60 degrees ok. So, we will try to form a table and do further analysis.

(Refer Slide Time: 33:01)



Interval	Values that conduct	V_d	Voltage across valve 1
$\alpha < \omega_s t < \alpha + 60^\circ$	2, 3	$e_b - e_c$	$e_a - e_b$
$\alpha + 60^\circ < \omega_s t < \alpha + 120^\circ$	3, 4	$e_b - e_a$	$e_a - e_b$
$\alpha + 120^\circ < \omega_s t < \alpha + 180^\circ$	4, 5	$e_c - e_a$	$e_a - e_c$
$\alpha + 180^\circ < \omega_s t < \alpha + 240^\circ$	5, 6	$e_c - e_b$	$e_a - e_c$
$\alpha + 240^\circ < \omega_s t < \alpha + 300^\circ$	6, 1	$e_a - e_b$	0
$\alpha + 300^\circ < \omega_s t < \alpha + 360^\circ$	1, 2	$e_a - e_c$	0



So, I will list all the 6 intervals and in each interval we will see what are the valves. There are 2 valves; 1 valve from the upper commutation group, 1 valve from the lower commutation group that conducts; so valves that conduct. And we are interested in what is happening to the DC side voltage ok. So, we look at the expression for the DC side voltage V_d . See V_d is see if you go back to the circuit V_d is the voltage across the DC side terminals ok.

So, we look at the expression for V_d . And we will also look at voltage across one of the valves, there are six valves. Now, one can show that there is symmetry, if you look at the voltage across one of the valves; say valve 1. The voltage across valve 2 will be similar to valve 1. In fact identical to valve 1, except for a phase shift.

So, voltage across all the valves are identical, except for phase shifts ok. So, I will I can just see what is happening to voltage across one of the valves. So, voltage across say valve 1; so I will try to form a table. So there are 6 rows in this table.

So, the 6 rows corresponds to the 6 intervals ok. So, what is the first interval?

Student: (Refer Time: 34:33).

Ok, I am not going by this figure see this figure has 6 intervals, but this first was corresponding to diode operation. See please note here this is something which is corresponding to continuous gate current ok. So, if I assume a general case where there is a delay, if there is a delay in giving a gate current pulse with respect to instead of natural conduction. What is the first interval? See suppose I take valve 3, valve 3 is turned on at α ok. Now it continues to be on up to what instant.

Student: Alpha plus (Refer Time: 35:14).

Alpha plus?

Student: 120.

12. So, each thyristors valve conducts for 120 ok. But I mean before the next thyristor in the same commutation group starts conducting there is one more thyristors valve in the other commutation group which starts conducting that is 4. See 3 is in the upper commutation group, 4 in the lower commutation group. So, 4 is turned on at, see you can refer to this figure, where I have considered a continuous gate current.

Student: 60 to 70.

So, at 60 plus alpha. So, here the only thing is the gate pulses are as good as giving gate pulse at 0 for valve 3, at 60 for valve 4 and so on. Now, in general it is alpha for valve 3, alpha plus 60 for valve 4, alpha plus 120 for valve 5 and so on ok. So, I can say that I can consider the cycle which is of duration 360 degree to be divided into 6 equal parts ah. So, each of this is called an interval. So, the first interval is between alpha and alpha plus 60 degrees ok.

Then the second interval is between alpha plus 60 degree, see what I have written here is in the first case ωt is greater than alpha and less than alpha plus 60. Then the third interval is alpha plus 120 to alpha plus 180 degrees, then alpha plus 180 degrees to alpha plus 240 degrees, alpha plus 240 degrees to alpha plus 300 degrees. And the last interval is alpha plus 300 degrees to alpha plus 360 degrees ok.

So we have just listed all the 6 intervals in one full cycle. See this one cycle is for the AC side or AC side period is 360 degrees please note that ok. So, if I take the first interval alpha to alpha plus 60 ,what are the valves that conduct? Valve 3 is turned on at.

Student: (Refer Time: 37:53).

Alpha. So, there is one more valve in the lower commutation groups that is conducting that is.

Student: (Refer Time: 37:58) 2.

2. So, valves that conduct in the first interval are 2 and 3. Then the next interval 3 4, 4 5, 5 6, 6 1, 1 2, then if you take the next interval of course, the cycle repeats. Now, can I write the expression for V_d in terms of say e_a , e_b , e_c looking at the circuit diagram. See in the first interval 2 and 3 are conducting.

So, if you look at the circuit diagram. From the circuit diagram if 2 and 3 are conducting can I get an expression for V_d . Say it is as good as saying 2 is a short circuit; valve 2 is acting as a short circuit, valve 3 is acting as a short circuit, other valves are open acting as open circuits. So, the positive terminal of the DC side is connected to the positive terminal of e_b through this valve 3 which is acting as a short circuit.

See what I am trying to say is in the first interval 2 and 3 are conducting so they are acting a short circuit. So, the positive terminal of the DC side is connected to the positive terminal of e_b , the voltage source e_b through valve. The negative terminal of the DC side is connected to the negative terminal sorry positive terminal of e_c through valve 2 which is again acting as short circuit. So, what is V_d ?

Student: E_c (Refer Time: 39:26).

E_b minus?

Student: E_c .

E_c ok. So, it is e_b minus e_c . so let us write that, so e_b minus e_c . So, looking at the circle diagram we can say what is the expression for V_d because based on what are the thyristors valves that conduct I mean they are acting as short circuit. So, you can easily get the expression for V_d in terms of e_a , e_b and e_c . So, when 3 and 4 conduct e_b minus.

Student: E a.

E a. So, the valves that conduct are actually acting as short circuits that is all. When 4 and 5 conduct?

Student: E c minus.

E c minus.

Student: E a.

E a. When 5 and 6 conduct, e c minus.

Student: E b.

E b fine. Then when 6 and 1 conduct.

Student: E a minus e b.

Ea minus e b. When 1 and 2 conduct.

Student: E a minus e c.

E a minus e c fine, this can be easily obtained from the circuit diagram ok. Then let us look at the voltage across one of the valve say valve one. Now, how to get the voltage across valve 1, again go back to the circle diagram. So, 2 and 3 are conducting in the first interval. So, what is the voltage across valve 1?

Student: (Refer Time: 40:59).

Now, it does not matter whether 2 conducts the point is 3 is conducting. So, once I know 3 is conducting, 3 is acting as a short circuit and the cathode of valve 1 is connected to the positive terminal of the voltage source e_b and the anode of valve 1 is connected to the positive terminal of e_a . So, from that I can say what is the voltage across valve 1.

Student: E_a minus e_b .

So, it is e_a minus e_b yeah. So, I will stick to the definition of voltage across the valve it is always the voltage of the anode with respect to the cathode fine. Similarly can we say what is the voltage across valve 1 when 3 and 4 conduct, again go back to the circuit diagram. Now, it does not matter whether 4 conducts or not 3 is conducting. So, it has the same as what happened in the previous interval. So, 3 whenever 3 is conducting it means it is e_a minus e_b .

Student: E_b .

Now, in the next interval 4 and 5 conducts. So, please note again it does not matter whether 4 conducts or not 5 is conducting what matters is 5 is conducting. So, since 5 is conducting, 5 is acting as a short circuit. So, voltage across valve 1 is e_a minus.

Student: E_c .

E_c . Again in the next interval it does not matter whether 6 conducts or not. Say whether 4 conducts or 6 conducts, it does not matter. The point is 5 is conducting so the expression is e_a minus e_c and the last two cases are very easy.

So, in the next 2 intervals; one is conducting. So, one is conducting means by your assumption of ideal thyristors valve this voltage is 0. So, we will try to analyze further by using this table and a few other explanations that was done in this class. So, I will continue with this in the next class.

