

**Introduction to Time - Varying Electrical Networks**  
**Professor Shanthi Pavan**  
**Department of Electrical Engineering**  
**Indian Institute of Technology Madras**  
**Lecture 52**  
**Input impedance of the 4-path filter at  $f_s$**

(Refer Slide Time: 0:25)



The slide shows a circuit diagram of a 4-path filter. It consists of an AC voltage source  $e^{j2\pi f_s t}$  in series with a resistor  $R_s$ . This is followed by a series inductor  $L$  with impedance  $j\omega L$ . The circuit then splits into four parallel branches, each containing a capacitor  $C$  with impedance  $1/(j\omega C)$ . The output voltage is  $V_o$  and the current is  $i$ . The input impedance is denoted as  $Z(j2\pi f_s) = ?$ .

Handwritten notes on the slide include:

- $\frac{1}{2\omega LC} = f_s$
- $\frac{V_o}{V_i} @ f_s \neq 1 \text{ but } \frac{8}{\pi^2}$
- $Z(j2\pi f_s) \neq \infty$
- $V_o = H(j2\pi f_s) e^{j2\pi f_s t}$
- $i = e^{j2\pi f_s t} [1 - H_i(j2\pi f_s)]$
- $\therefore Z(j2\pi f_s) = \frac{V_o}{i} = \frac{R_s}{\frac{H_o(j2\pi f_s) e^{j2\pi f_s t}}{[1 - H_i(j2\pi f_s)] e^{j2\pi f_s t}} \cdot R_s}$
- $= \frac{R_s \cdot \frac{8}{\pi^2}}{1 - \frac{8}{\pi^2}} = \frac{R_s \cdot 8}{\pi^2 - 8}$



Now, another thing that I would like to draw your attention to is the following. So, this is  $v_i$ , this is  $v_o$ . So, when we look at an LC resonant network we always say that at resonance or at the center frequency the impedance of the offered by the LC parallel network is infinite because the inductive impedance and the capacitive impedance cancel each other. What should we expect now intuitively?

Student: Here it should be large.

Professor: It should be large but it will not be infinite. Why?

Student: Because gain is not there.

Professor: Very good. So, basically we should expect that the we know that we  $v_o$  by  $v_i$  at  $f_s$  is not 1 but  $8$  over  $\pi$  square. So, therefore we should expect that  $Z$  of  $j 2 \pi f_s$ , yeah, is not infinity, but presumably some large value. Let us calculate what that large value is. So, if this is  $v_i$ , this  $v_o$  is nothing but at the frequency  $f_s$  is nothing but  $H_0$  of  $j 2 \pi f_s$  times.

So, if  $v_i$  is  $e^{j 2 \pi f_s t}$  then this is  $H_0$  of  $j 2 \pi f_s t$  times  $e^{j 2 \pi f_s t}$ . And therefore, what comment can you make about the current flowing through the resistor? That is all. So,  $i$  is nothing but  $e^{j 2 \pi f_s t}$  times  $1 - H_0$  of  $j 2 \pi f_s t$  that is the difference in voltage divided by  $R_S$ . And therefore what is  $Z$  at  $j 2 \pi f_s$ ?

Is nothing but the voltage  $v_0$  by, we are trying to find looking an impedance of the set of 4 capacitors which are periodically switching. The voltage we want is known and the current  $i$  is also known. So,  $v$  by  $i$  and therefore  $v$  is nothing but  $H_0$  of  $j 2 \pi f_s t$  times  $e^{j 2 \pi f_s t}$ , this divided by  $e^{j 2 \pi f_s t}$  times  $1 - H_0$  of  $j 2 \pi f_s t$  times  $R_S$ . Which therefore it is easy to see that this goes away and this is going to be  $R_S$  times  $H_0$  is  $8$  over  $\pi^2$  divided by  $1 - 8$  over  $\pi^2$  which is  $R_S$  times  $8$  divided by  $\pi^2 - 8$ .

(Refer Slide Time: 5:46)



$1 - \frac{8}{\pi^2}$      $\frac{8}{\pi^2 - 8}$

Therefore, at the center freq,  $Z(j 2 \pi f_s) = \frac{8 R_S}{\pi^2 - 8} \approx 4 R_S$

Limiting case as  $N \rightarrow \infty$

$\frac{k}{k} @ f_s = 1$   
 $Z_c(j 2 \pi f_s) = \infty$



So, therefore, at the center frequency the looking in impedance of this so called switch capacitor resonator is  $8 R_S$  by  $\pi^2 - 8$  which is approximately  $\pi^2$  is about 10,  $10 - 8$  is 2 is roughly about  $4 R_S$ . If the gain was infinite, then it should be infinite. So, if you go on increasing the number of phases. So, for example, if you made an 8 path filter where each phase is now on for a  $T_s$  by 8 what comment can we make about that all these quantities and what comment can you make about the gain for instance?

In the limit as the number of phases become infinite what comment can you make with respect to the gain at  $f_s$ ? In the limiting case let us say you have an infinite bank of capacitors, each with an infinitesimally small width clockwork.

Student: Average will be 2 by pi.

Professor: No, average will not be 2 by pi, it will be exactly what that input voltage is at that point. So, the voltage across the different capacitors will be the same as the input sine wave. So, if you look at the output voltage, it will be a sine wave which whose amplitude is the same as that of the input. So, the gain will be 1. If the gain is 1, the, yeah. So, the limiting case, so this is  $v_i$  is  $R_s$  and then you have  $\phi_1$  let us say blah, blah, blah, blah.

So, and then each one of these is infinitesimally, so this is an example  $\phi_1$ . And if you put a cosine here what will happen, this will sample the cosine at one point. So, the voltages across these capacitors will actually do, will do this. So, they will go from, so this is these are the VCs. So, this will go all the way from 1 to I mean back here. So, the voltage here is therefore going to be exactly, yeah, so  $V_o$ . So, as  $N$  tends to infinity,  $V_o$  by  $V_i$  at  $f_s$  is going to be 1 and  $Z_{in}$  of  $j 2\pi f_s$  is going to be infinite.

(Refer Slide Time: 10:32)

The slide contains the following content:

- NPTEL Logo**
- Circuit Diagram 1:** A series combination of a resistor  $R_s$  and  $N$  capacitors. The input voltage is  $e^{j2\pi f_s t}$  and the output voltage is  $V_o = H_s(j2\pi f_s) e^{j2\pi f_s t}$ . The current is  $i = e^{j2\pi f_s t} [1 - H_s(j2\pi f_s)]$ .
- Equation 1:** 
$$\therefore Z(j2\pi f_s) = \frac{V_o}{i} = \frac{R_s H_s(j2\pi f_s) e^{j2\pi f_s t}}{[1 - H_s(j2\pi f_s)] e^{j2\pi f_s t}} = \frac{R_s \frac{8}{\pi^2}}{1 - \frac{8}{\pi^2}} = \frac{R_s 8}{\pi^2 - 8}$$
- Text:** Therefore at the center freq  $Z(j2\pi f_s) = \frac{8R_s}{\pi^2 - 8} \approx 4R_s$
- Text:**  $Z_s(j2\pi f_s)$  depends on  $R_s$ !  $\left\{ \begin{array}{l} LTV \text{ Behavior} \end{array} \right.$
- Text:** Limiting Case as  $N \rightarrow \infty$
- Circuit Diagram 2:** A resistor  $R_s$  in series with an infinite number of capacitors, indicated by an ellipsis. The output voltage is  $V_o$ .
- Equation 2:** 
$$\frac{V_o}{V_i} @ f_s = 1$$
  
$$Z_s(j2\pi f_s) = \infty$$

Another thing that I would like to draw your attention to with this case is the following. See one strange thing that we are seeing here or seemingly strange thing is that the looking in impedance

of this circuit, yeah, the looking at impedance towards the right, it depends on  $R_S$  which is something that we will never see in a time invariant circuit.

So,  $z_{naught}$  of  $j 2 \pi f_s$  depends on  $R_S$  which is something which is this is due to LPTV behavior. The only thing we can say is that the  $z_{naught}$  has contributions from frequency, frequencies other than that at  $f_s$  because its time varying behavior and basically those components are all responsible for the, they depend evidently on  $R_S$  and therefore it is not surprising that it depends on  $R_S$ .

The only valid treatment of impedance I mean you cannot, I mean this  $z_{naught}$  which relates the fundamental voltage to the fundamental current is only one part of that  $Z$  that matrix which relates the harmonic components of the voltage developed across the network to the harmonic components of the currents being injected. So, and therefore, you can have a component at  $f_s$  due to down conversion of currents at frequencies of the form  $f_s$  plus multiples of  $f_s$ .