

**Phase-Locked Loops**  
**Dr. Saurabh Saxena**  
**Department of Electrical Engineering**  
**Indian Institute of Technology Madras**

**Lecture – 27**  
**Problems in Charge Pump PLL – Reference Spur**

So, we were looking at the problems in the charge-pump PLL which we have introduced just a few sessions back. So, let us look at another problem in the charge-pump. And another problem in the charge-pump is associated with the charge-pump and loop filter action together.

(Refer Slide Time: 00:39)

The slide shows a circuit diagram of a charge pump with a PMOS transistor (WP) and an NMOS transistor (WN) connected to a load resistor R and a capacitor C1. The input current is Icp. The control voltage Vctrl is shown with a ripple. The output voltage Vr is also shown with a ripple. The waveforms show the reference clock period T and the resulting reference spurs. The ripple is labeled as 'Control Voltage ripple'.

$V_R$  modulates oscillator frequency every reference clock period.

$$V_R = \sum a_n \cos(n\omega_R t) + b_n \sin(n\omega_R t)$$

$$\omega_R = \frac{2\pi}{T} \text{ reference frequency.}$$

—  $(\omega_{ind} \pm k\omega_R)$  Reference Spurs



The slide shows the same circuit diagram as Slide 1, but with an additional bypass capacitor C2 connected in parallel with the load resistor R. The waveforms show the reference spurs and the control voltage ripple. The ripple is labeled as 'Control Voltage ripple'.

$V_R$  modulates oscillator frequency every reference clock period.

$$V_R = \sum a_n \cos(n\omega_R t) + b_n \sin(n\omega_R t)$$

$$\omega_R = \frac{2\pi}{T} \text{ reference frequency.}$$

—  $(\omega_{ind} \pm k\omega_R)$  Reference Spurs

Transfer function analysis:

$$\frac{1}{R} \ll \frac{1}{j\omega_R C_2} \ll \left| R + \frac{1}{j\omega_R C_1} \right|$$

$$\approx \frac{1}{j\omega_R C_2} \ll \frac{|1 + j\omega_R C_1 R|}{\omega_R C_1}$$

$C_2 \gg \frac{C_1}{|1 + j\omega_R C_1 R|}$

—  $C_2$  is called ripple bypass capacitor.

So, let me just redraw the charge-pump plus loop filter. So, you have this  $I_{CP}$  followed by the loop filter response. So, this is UP and DN, let us not worry about UP and DN now,  $I_{CP}$  and this is  $i_{cp}$  going in the system. Now, what happens is we have seen this multiple times that let us say the UP and DN pulses are such that you have some kind of phase error.

So, I am going to draw the UP pulse like this. It is periodic in nature, you can think about it and this is UP, and DN will also be a similar square pulse with a lesser width. Whether UP is larger or DN is larger, that depends on the phase error. So, in response to these UP and DN pulses, these UP and DN pulses, you have  $i_{cp}$ , small  $i_{cp}$ , the current which flows through the loop filter is shown here.

Now, when this particular  $i_{cp}$  current is pumped into the loop filter, earlier we drew the control voltage, this voltage is by the way control voltage. The control voltage happens to be like this, a jump, integration and jump like this and then comes back. If you think about it, what I am trying to do is, suddenly, you can think that suddenly you have  $i_{cp}$  current flowing through a resistor and capacitor. So, whatever value of the voltage, if this particular voltage before this rising edge may not be equal to zero, it will be some voltage. So, as soon as you start pumping the current  $i_{cp}$ , the capacitor voltage cannot change instantaneously. So, what you see here is a jump in the voltage and this jump is equal to  $I_{CP}R$ , the jump here is  $I_{CP}R$  and then the current keeps on integrating over the capacitor, and the voltage keeps on increasing linearly.

So, if I call this as  $V_C$ ,  $V_C$  is initially 0 and then it keeps on increasing. So,  $V_C$  and  $V_R$ , the voltage across the capacitor and resistor respectively can be drawn here. So, I will say that there is a voltage like this. So, you have a voltage like this. This is  $V_R$  voltage across the resistor and voltage across the capacitor is something like this. The voltage across the capacitor changes slowly, and  $V_{ctrl} = V_R + V_C$ .

So, what is the problem with this? Well, the problem is that the control voltage which is connected to the oscillator is changing every reference frequency and for multiple reasons. You have this oscillator here, this is your control voltage. So, the control voltage of the oscillator changes every reference frequency for multiple reasons whether you have phase error, some problems in the charge-pump and other things, those things will happen.

So, because of this change in the control voltage at the reference frequency, you modulate the frequency of the oscillator with  $V_R$  like pulse waveform. So, I will say  $V_R$  modulates oscillator frequency every reference clock period, this is my reference clock period.

Now, well, the waveform which you are seeing is more or less square waveform or square waveform with duty cycle and this is whatever  $\Delta t$  error you are going to have in steady state, it depends, the pulse width depends on that. So, this  $V_R$  can be written in terms of the Fourier series as follows:

$$V_R = \sum a_n \cos(n\omega_R t) + b_n \sin(n\omega_R t)$$

where,  $\omega_R = \frac{2\pi}{T}$  is the reference frequency in rad/sec.

So, now you can write the Fourier series for this  $V_R$  waveform, it is modulating your oscillator's frequency and if you pick up even the first one, where  $n=1$ , then you see that you are modulating oscillator's voltage at  $\omega_R$  which is finally leading to  $\omega_{out} \pm \omega_R$ . These components will come and the components at  $\omega_{out} \pm \omega_R$  are normally termed as reference spurs.

So, if you look at the spectrum of the oscillator in a given PLL, you will find that you have  $\omega_{out}$  and you have other components also and one of the dominant components is  $\omega_{out} + \omega_R$ , another is  $\omega_{out} - \omega_R$ . So, the problem of reference spur exists because there is an instant change in the control voltage of the oscillator. It is more prominent and it is not only that you are going to have  $\omega_{out} \pm \omega_R$ , depending on your output frequency, you are going to see other higher order harmonics also such as  $\pm 2\omega_R$  and so on.

So now, we realize that this is the problem because of this control voltage variation which we also term as control voltage ripple. It is a ripple at the control voltage. Because of the control voltage ripple, we modulate the output frequency of the oscillator and we have unwanted components in the form of reference spurs. If we know the problem, then it is really good, we can find a solution.

So now, what we need to do is this. We cannot avoid the phase error information coming from the PFD plus charge-pump every reference frequency, that is not avoidable. So, what we need to do is the following. Let us say that I am going to get this current  $i_{cp}$  coming from the charge-pump in the loop filter.

And if I have this loop filter, I know that what will happen is there will be a jump. So, if I do not want that this should have a jump, what I can do is I can provide another low impedance path to the  $i_{cp}$  current which is coming at every reference frequency. So, that low impedance path can be provided by a capacitor with value  $C_2$ .

So, just for hand-waving analysis, let me put it that way, I have  $i_{cp}$ , it sees two paths, one with  $C_2$  and other with  $R$   $C_1$ . If I make sure that the impedance provided by  $C_2$  at  $\omega_R$  frequency or your reference frequency is much smaller than the impedance provided by  $R$  and  $C_1$ , then it will help in reducing the ripple on the control voltage. So, we have,

$$\left| \frac{1}{j\omega_R C_2} \right| \ll \left| R + \frac{1}{j\omega_R C_1} \right|$$

$$\left| \frac{1}{C_2} \right| \ll \left| \frac{1 + j\omega_R C_1 R}{C_1} \right|$$

$$C_2 \gg \frac{C_1}{|1 + j\omega_R C_1 R|}$$

where,  $\omega_R$  refers to the reference frequency.

So, if you look at it, I need to provide, just from this, earlier we have seen that we chose  $C_1$  and  $R$  such that we had proper phase margin and other things. Now, I have to choose  $C_2$  which is larger than some particular component value and depending on the  $C_2$  capacitor, I can bypass the ripple voltage. So, this  $C_2$  is often termed as ripple bypass capacitor because we introduce it as a ripple suppressant.

Now, if we have  $C_2$  as a ripple bypass capacitor, this analysis is just a hand-waving that the impedance provided by the two, but the combined impedance here of  $R$   $C_1$  plus  $C_2$  actually introduces another pole in the loop filter which increases the order of the PLL and it questions the stability of the PLL.

(Refer Slide Time: 13:28)

NPTEL

Poles  $\lambda_1 = 0, \lambda_2 = 0, \lambda_3 = -\omega_{p3}$

Zero  $z_{e0} = -\frac{1}{RC_1}$


$\omega_{p1} = \omega_{p2} = 0, \omega_{p3} = \frac{1}{RC_1 C_2}$

$\omega_z = \frac{1}{RC_1}$

$L(s) = \frac{I_{cp} K_{vc0}}{2\pi^2 (s_1 t_{s2})} \frac{(1 + s/\omega_z)}{(1 + s/\omega_{p3})}$

$\angle L(s) = -180^\circ + \tan^{-1}(\omega/\omega_z) - \tan^{-1}(\omega/\omega_{p3})$

 $L(s) = \frac{I_{cp}}{2\pi} \frac{(1 + sRC_1)}{(1 + sRC_1 C_2)} \frac{K_{vc0}}{s^2 (C_1 + C_2)}$




NPTEL

$L(s) = \frac{I_{cp} K_{vc0}}{2\pi^2 (s_1 t_{s2})} \frac{(1 + s/\omega_z)}{(1 + s/\omega_{p3})}$

$\angle L(s) = -180^\circ + \tan^{-1}(\omega/\omega_z) - \tan^{-1}(\omega/\omega_{p3})$

$L(s) = \frac{I_{cp}}{2\pi} \frac{(1 + sRC_1)}{(1 + sRC_1 C_2)} \frac{K_{vc0}}{s^2 (C_1 + C_2)}$

 $\omega_{p3} < \omega_{p3}$   
 $C_1 > C_2$



So now, let us just redraw our PLL with the ripple bypass capacitor. So, the charge-pump, another set of switches controlling here and then this goes through a loop filter using  $R, C_1$  and then  $C_2, R, C_1$  which goes to the VCO. So, what you see here is that we when we try to solve the problem, if we create another problem. We have to check that how much problem we solved and how much problem we created.

So here, we have the reference voltage, this is our OUT, this comes  $i_{cp}$  and this is the control voltage. The small signal model of this PLL, this again a simple one that you have the phase error multiplied by, I will write it as  $\frac{I_{CP}}{2\pi}$  going into the loop filter with  $C_1$  and  $C_2$  which gets multiplied

by  $\frac{K_{VCO}}{s}$ , this is +, this is -, this is  $i_{CP}$ , this is  $V_{ctrl}(s)$ , so,  $\varphi_{REF}$  and  $\varphi_{OUT}$ . Look at the loop gain now.

So, loop gain for this particular PLL is given by,

$$LG(s) = \frac{I_{CP}}{2\pi} \frac{(1 + sRC_1)}{\left(1 + \frac{sRC_1C_2}{C_1 + C_2}\right)} \times \frac{K_{VCO}}{s^2(C_1 + C_2)}$$

So now, with this new loop gain, we will see whether this loop is stable or not. So, here you have two poles, at  $\omega_{p1} = \omega_{p2} = 0$ , and you have the third pole at  $\omega_{p3} = \frac{1}{\frac{RC_1C_2}{C_1+C_2}}$ . By the way, you must be used to writing these poles whether it is a left half plane pole or right half plane pole. Here when I am writing  $\omega_{p3}$ , I am saying it is a pole but it is just the frequency part  $\omega_{p3}$ . Poles are  $s_1 = 0$ ,  $s_2 = 0$  and  $s_3 = -\omega_{p3}$ .

So, I want to avoid any confusion here.  $\omega_{p3} = \frac{1}{\frac{RC_1C_2}{C_1+C_2}}$  is not our pole. Now, zero in Laplace domain is actually at  $-\frac{1}{RC_1}$  and the zero frequency which I use in the expression is  $\omega_z = \frac{1}{RC_1}$ . So, the loop gain expression can be rewritten as given below.

$$LG(s) = \frac{I_{CP}K_{VCO}}{2\pi s^2(C_1 + C_2)} \frac{(1 + s/\omega_z)}{(1 + s/\omega_{p3})}$$

The angle of this loop gain at any given frequency is given by,

$$\angle LG(j\omega) = -180^\circ + \tan^{-1}(\omega/\omega_z) - \tan^{-1}(\omega/\omega_{p3})$$

So, let us see whether our system is stable or not. First I am going to plot the loop gain with respect to  $\omega$ , so, this is  $|LG|$  in dB. What you see is that you are having two poles at 0, so, you will have -40 dB/dec, then you have a zero. So, it will be like this. Then depending on the position of our  $\omega_{p3}$ , I am going to have the second pole. This is one option which you see that  $\omega_{p3}$  is coming after  $\omega_u$ . Looking at these things you can very well say  $\omega_{p3}$  is surely going to be larger than  $\omega_z$  because  $\frac{C_1C_2}{C_1+C_2} < C_1$ , but whether  $\omega_{p3}$  is going to be greater than  $\omega_u$  or less than  $\omega_u$ , that we do not know.

So, if we have such a kind of loop gain, then the corresponding phase plot is going to be like this. So, at  $\omega_u$ , you will have, so, I will just take another line here. So, this is  $-180^\circ$ ,  $-135^\circ$ ,  $-90^\circ$ ,  $-45^\circ$ . So, it starts with  $-180^\circ$ , it has a zero, so, it goes to  $-135^\circ$ . If  $\omega_{p3}$  comes much later, then it may reach close to  $-90^\circ$  and when it comes  $\omega_{p3}$  it may again go to  $-135^\circ$  and then finally what you see here is that  $\omega_{p3}$  is a pole. So, at maximum this can introduce  $90^\circ$ , this can introduce  $90^\circ$  which cancels out. So, as frequency tends to infinity, you may go to  $-180^\circ$ . So here, the phase margin which you may calculate appears to be this.

Now, in place of the  $\omega_{p3}$  location which we have seen, if it happens that  $\omega_{p3}$  comes here because you increase  $C_2$ , so,  $\omega_{p3}$  can change its location. If  $\omega_{p3}$  comes here, then what you see is that you will surely have  $-135^\circ$  and then you have another pole. So, before it reaches what you can say is your frequency comes, it does not reach  $-90^\circ$ .

So, what you may see is that the phase is actually much lesser. It is not going to be  $-135^\circ$ , it will be slightly larger than may be  $-135^\circ$  and then it will finally go like this. So, these are the two cases which I have seen and if you now want to calculate the phase margin, it is going to be only this much. So, this I will write this as  $\omega_{p3}'$ . So, we have,

$$\omega_{p3}' < \omega_{p3}$$

$$C_2' > C_2$$

$C_2'$  is the capacitor which you are using for  $\omega_{p3}'$  and it appears that the phase margin is reduced.

So now, as we introduced another pole in the system, what we found is that yes you can reduce the control voltage ripple but you make your PLL more susceptible to instability. Well, we will not have a PLL which is unstable. So, we will try to make it stable with the desired phase margin. But if you do not pay attention, if you just use  $C_2$  with a very large value, then what you will see as phase margin is not there, zero and pole cancel out, and with no phase margin, you will have an unstable PLL. So, we need to look at how we are going to choose this phase margin and how we place  $\omega_{p3}$  in our system. Thank you.