


**Higher Engineering Mathematics**  
**Prof. P.N. Agrawal**  
**Department of Mathematics,**  
**Indian Institute of Technology Roorkee**  
**Karnaugh Map - I**  
**Mod05\_Lec24**

(Refer Slide Time: 0:25)

**Method for simplifying the Boolean functions**

By simplifying a Boolean function we can reduce the required number of gates and so we can reduce the size of the circuit and thereby reduce cost also.

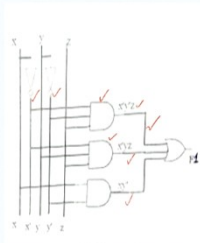**Example:** Consider a Boolean function  $F_1 = x'y'z + x'yz + xy'$  To implement this Boolean function, we need two NOT gates, two 3 input AND gates, one 2 inputs AND gate and one 3 inputs OR gate.




*2 AND gates  
1 OR*



**Method for simplifying the Boolean functions**

By simplifying a Boolean function we can reduce the required number of gates and so we can reduce the size of the circuit and thereby reduce cost also.

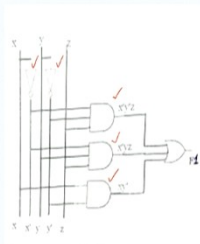**Example:** Consider a Boolean function  $F_1 = x'y'z + x'yz + xy'$  To implement this Boolean function, we need two NOT gates, two 3 input AND gates, one 2 inputs AND gate and one 3 inputs OR gate.



*Two NOT gates x', y'  
Three AND gates  
one OR gate*



Hello friends, welcome to my lecture on Karnaugh maps. In this lecture we shall discuss the matter of simplifying Boolean functions. Why we simplify Boolean function? Okay, if we simplify a Boolean function, we can reduce the required number of the gates and so we can reduce the size of the circuit and thereby reduce the cost also. Say for example, consider this

Boolean function,  $F_1 = X'Y' + X'YZ + XY'$  Now this is the figure of this Boolean function, you see this is X, this is X conjugate, sorry this is X, this is X', this is Y, this is Y' and this is Z.

Okay, so then  $X'Y'Z'$ , okay,  $X'Y'$ , so we have this input X', then we have this input Y' and then we have this input Z. Okay and  $X'Y'Z'$ , to implement  $X'Y'Z'$ , we have consider this AND gate, okay. So when these are 3 inputs  $X'Y'Z'$  then to get the output  $X'Y'Z'$  we have used this AND gate. Okay, then  $X'YZ$ , so we have this X' input then Y and then Z. Okay, so 3 inputs are there, X'Y and Z and to get the output as  $X'YZ$  we accused again another AND gate, okay.

So, then the third term is  $XY'$  so we have this input X okay and this input Y' okay, so 2 inputs are here X and Y' and to get the output  $XY'$  we use the AND gate. Okay, so in the first AND gate there are 3 inputs  $X'Y'Z$ . Okay, in the second AND gate there are 3 inputs again X'Y and Z and in the case of third AND gate there are 2 inputs X and Y'. So, there are 3 AND gates, first AND gate considers two, 3 inputs, okay, this AND gate has 3 inputs, this AND gate has 3 inputs again and this AND gate has 2 inputs and there are two NOT gates, this is one, okay, X' and Y', there are two NOT gates.

So, there are two NOT gates, okay, two, 3 input AND gates, there are 3 input AND gates okay, there are 3 input AND gates here and then to obtain  $F_1$  okay, the output  $F_1$  okay, we have to use this OR gate okay, so for OR gate there are 3 inputs  $X'Y'Z$ . Okay,  $X'YZ$  and  $XY'$  so there are 3 inputs and to get the output  $F_1$  we use this OR gate okay, so there are 3 AND gates with one has 3 inputs, the one other has 3 inputs again, the third one has 2 inputs and 3 AND gates and one OR gate.

So there are two NOT gates okay, X' and Y', to get X'Y' okay and there are 3 AND gates okay, this, this and this 3 AND gates, two NOT gates this and this okay and there is 1 OR gate, okay, to get the desired output  $F_1 = X'Y'Z + X'YZ + XY'$ . Now that is simplify this Boolean expression. Okay, using the postulates and the theorems that we are earlier studied.


(Refer Slide Time: 4:55)

Cont..

Let us simplify this Boolean function using postulates and theorems, then

$$\begin{aligned} F_1 &= \underline{x'y'z} + \underline{x'yz} + xy' \\ &= \underline{x'z}(y+y') + xy' \\ &= \underline{x'z} + xy' \quad (\text{because } y+y'=1) \end{aligned}$$

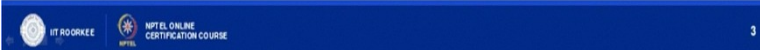*Handwritten notes:*  
 $a \times (b+c) \checkmark$   
 $= a \times b + a \times c$   
 $y+y'=1$   
 $x'z \times 1 = x'z$   
because  
 $a \times 1 = a$   
 $\forall a \in B$




Okay, but we will have them, so let us simplify this Boolean function using postulates and the theorems  $F_1 = X'Y'Z + X'YZ + XY'$ , we can then use this distributive law and we say that

$A \times (B+C) = A \times B + A \times C$  Okay, so  $X'Y'Z + X'YZ + XY'$  can be written as  $X'Z * (Y+Y')$  by using this distributive law, so  $X'ZY + Y' + XY'$ , now  $Y+Y'=1$  okay.

So, we have  $X' * X'Z * 1$  here. Okay and this is equal to  $X'Z$  because  $A * 1 = A \forall A \in B$  okay, this we know for all  $A \in B$ ,  $A * 1 = A$ , 1 is the unit element, so here  $X'Z * 1 = X'Z$  and therefore we will have  $X'Z + XY'$  making use of  $Y+Y'=1$ . Now, let us see how to get this desired this output  $X'Z + XY'$ , let us again draw the gates.

(Refer Slide Time: 6:34)

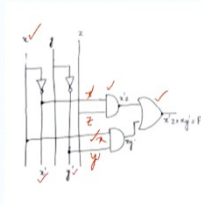Now let us implement this simplified Boolean function



Two NOT gates  
Two AND gates  
one OR gate

$$F_1 = \underline{X'Z} + \underline{XY'}$$

After simplification of Boolean function, now we need two NOT gates, two 2 inputs AND gates and one 2 inputs OR gate.



Cont..

Let us simplify this Boolean function using postulates and theorems, then

$$\begin{aligned} F_1 &= \underline{X'Y'Z} + \underline{X'YZ} + XY' \\ &= \underline{X'Z}(Y + Y') + XY' \\ &= \underline{X'Z} + XY' \quad (\text{because } Y + Y' = 1) \end{aligned}$$

$a \times (b+c) \checkmark$   
 $= a \times b + a \times c$   
 $Y + Y' = 1$   
 $X'Z \times 1 = X'Z$   
became  
 $a \times 1 = a$   
 $\neq a \times b$



So, here we have this, this is your X, this is  $X'$  okay, the output, so we have one NOT gate and then for Y we have one NOT gate  $Y'$ , so there are two NOT gates, okay, and since our output

$F_1 = X'Z + XY'$ , how to get is  $X'Z$ ? We take the input  $X'$ , okay, this is input  $X'$ , and this is input Z. Okay, so  $X'$ , this is  $X'$ , this is Z, to get  $X'Z$  we used this AND gates, okay, so 1 AND gate we use to get the  $X'Z$ , so there are 2 inputs  $X'Z$  and 1 AND gate to get the output  $X'Z$  and then for the other term  $XY'$  we use again 2 inputs this is X and this is  $Y'$ , okay, so two inputs X and  $Y'$  with an AND gate then gives us  $XY'$  okay.

So, and to get then  $X'Z + XY'$  we use one OR gate okay, so this is one OR gate, so we have two NOT gates, two AND gates and one OR gate, okay, and we get  $F_1 = X'Z + XY'$ . So you can see now the number of gates that we need are less, okay, in comparison to the previous case and number of inputs also are less, okay, there we had 3 inputs, okay, if we see this one, this figure we had two NOT gates okay, we also have two NOT gates there, we have three AND gates here, while we have one AND gate there, we have two AND gates there.

So, this three AND gates reduced to two AND gates and moreover the inputs like here in this two AND gates the inputs were three each. Okay, here, three and here also three and there we see that we have two AND gates with inputs 2 each. So, by using postulates and the theorem we can simplify given Boolean expression, so that many draw the figure okay, we use less number of AND or OR gates and NOT gates to get the desired output, so that actually reduces the cost of the output, to get the desired output, we have to spend much less okay, by using the theorems and postulates to simplify the given Boolean function.

(Refer Slide Time: 9:38)

Methods to simplify the Boolean functions

- 1 Simplification of Boolean functions using postulates and theorems.
- 2 Simplification of Boolean functions using Karnaugh map.

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 5

Now, let us consider methods to simplify the Boolean functions. Okay, one method that we have just now seen by using postulates and theorems, we can simplify the Boolean functions, the other method is using Karnaugh map okay, so let us see how we use Karnaugh map to simplify the given Boolean functions.

(Refer Slide Time: 10:00)

To simplify the Boolean function using postulates and theorems, there are no specific rules. The only way to simplify is that applying postulates, basic theorems and many other familiar manipulation methods.

**Example:**  $f = x(x' + y)$  ✓

$$\begin{aligned} f &= x x' + x y \\ &= 0 + x y = x y \end{aligned}$$

$$a * (b + c) = a * b + a * c$$

$$a * a' = 0$$

$$a + 0 = a, \forall a \in B$$



Now, let us say to simplify the Boolean function if you use postulates and theorems okay, then there are no specific rules. The only way to simplify is that the apply postulates and basic theorems and some other manipulation methods to arrive at the simplification of the given Boolean expression, let say for example, let us consider  $F = X X' + Y$  okay, then we can simplify this, so F is equal to we use distributive law  $a * (b + c) = a * b + a * c$  okay and this gives us  $X X' + XY$ . Now, we know that  $a' * a = 0$ . Okay, so this is equal to  $0 + XY$ , okay, and we know that by identity law  $A + 0 = A \forall A \in B$  okay, so  $0 + XY = XY$  So, we see that the expression  $F = X X' + XY$  can be simplified to  $F = XY$  by using the postulates and theorems.

(Refer Slide Time: 11:23)

**Example:**

$$f = xy + x'z + yz$$

$$= xy + x'z + xyz + x'yz$$

$$= xy(1+z) + x'z(1+y)$$

$$= xy + x'z$$

**Example:**

$$f = (x+y)(x'+z)(y+z)$$

$$= (x+y)(x'z + yz)$$

Now, let consider another example  $XY + X'Z + YZ$ , let consider this Boolean function, we can write it as  $XY + X'Z$  and then  $YZ$ ,  $YZ$  can be written as  $X + X'YZ$ . Okay, because  $X + X' = 1$  okay, so this  $YZ$  can be written as  $X + X'Z$  and then this is equal to by distributive law

$XYZ + X'YZ$ , so we have  $XY + X'Z + XYZ + X'YZ$  here. Okay, now  $X'XY + XYZ$  can be combined and we can write  $XY * 1 + Z$ , Okay.

So,  $XY + XYZ$  can be combined and we have  $XY * 1 + Z$ . Okay, so we have this, now we know that  $A + 1 = 1$ ,  $A + 1 = A$ ,  $A \forall A \in B$ , so

$XY * 1 + Z$ ,  $1 + Z = 1$  okay, so this will be  $XY * 1$  okay, this is equal to  $XY * 1$  and  $XY * 1 = XY$  okay, because we know that  $A * 1 = A$ ,  $A \forall A \in B$ . Okay, B, so this gives us  $XY$  and similarly we combine  $X'Z$  and  $X'YZ$  so  $X'Z * 1 + Y$  we can write,  $1 + Y = 1$ , okay, so we have

$X'Z * 1$ ,  $X'Z * 1$  we get X,  $X'Z$  by using this result, this theorem. So we have

$XY + X'Z$ . Okay, so this given expression which consisted of the 3 terms  $XY$ ,  $X'Z$  and  $YZ$  is reduced to now 2 terms  $XY$  and  $X'Z$ .

Okay, now let us consider this another Boolean function  $F = ZX + YX' + ZY + Z$ . Okay, then what you notice is that if you take the, these 2 terms  $X' + Z$  then  $X' + ZY + Z$ , we can write as

$X'Y + Z$  by using  $a * (b + c) = a * b + a * c$  okay, we can write it as X plus,  $X' + Z$ .  $y + z$  we can literally write as  $Z + X'Z + Y$ , okay. So then it is equal to  $Z + X' * Y$ , okay. So, we have or we

can write it as  $X' * Y + Z$ . Okay, so  $X' Y + Z$  we have here, okay, so the function F which consisted of 3, product of 3 terms, now has been reduced to product of 2 okay,  $X + Y$  and  $X' * Y + Z$

(Refer Slide Time: 15:04)

**Minterm:** A product term in which all the variables appear exactly once, either complemented or uncomplemented, is called a minterm. A minterm represents exactly one combination of the binary variables in a truth table. It has value of 1 for that combination and 0 for the others.



Now, let us define a Minterm, a product term in which all the variables appear exactly once. Okay, either complemented or uncomplemented is called a minterm, okay. So a product term in which all the variables appear exactly once, okay, either complemented or uncomplemented is called a minterm. This we define or in the previous lecture also. Okay, we have defined it again to emphasise it because we are using, going to use it when we discuss Karnaugh maps, so we have defined it earlier. Again here, a minterm represents exactly one combination of the binary variables in a truth table. Okay, it has the value 1 for that combination and 0 for the others and we shall see while discussing Karnaugh maps.



(Refer Slide Time: 15:52)

### Karnaugh maps

The Karnaugh map method is a graphical technique which provides a simple straightforward procedure for simplification of Boolean expressions up to six or fewer variables.

A Karnaugh map is a diagram made up of a number of squares. If the expression contains  $n$  variables, the map will have  $2^n$  squares. Each square represents a minterm and 1's are written in the corresponding squares for the minterms present in the expression and 0's are written in those squares which correspond to the minterms not present in the expression. Once the map is filled with 0's and 1's, the canonical sum of products expression for the output can be obtained by grouping together those squares that contain 1.



So, the Karnaugh map method is a graphical technique, it is a graphical technique which provides a simple procedure for simplification of Boolean expressions and it can be applied to six or fewer variables beyond that it is not easy to handle this situation, so Karnaugh maps can be used to Boolean expressions containing up to six variables, Karnaugh map it is a diagram made up of a number of squares, okay.

If the expression contains  $N$  variables, the map will have  $2^N$  squares, each square represents a minterm, okay, and 1s are written in the corresponding squares for the minterms present in the expression and 0s are written in those squares which correspond to the minterms not present in the expression okay, so those minterms which are present in the expression, in the corresponding boxes.

Okay, we shall write 1 and the minterm which are not present in the expression in those boxes, we shall in those squares, we shall put 0. Okay, now once the map is filled with 0s and 1s the canonical sum of products expression. Okay, for the output is obtained by grouping together those squares that contain 1, okay, so we shall then group those squares that contain 1 to get the desired output.


(Refer Slide Time: 17:28)

### 2-Variable Karnaugh Maps

Since the number of variables are two, the map will have 4 squares. The values of one variable, say A, are listed above the top horizontal line and the values of other variable, say B, are listed on the left side. Four possible minterms with two variables A and B

$$AB, AB', A'B, A'B'$$

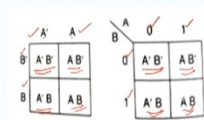are represented by the four squares in the map as shown below:



Now, let us consider two variable case for Karnaugh maps. So, if you consider a Boolean expression having with two variables then the number of, since the number of variables are two, the map will have, Karnaugh map we have 2 the power 2 that is 4 squares. The values of one variable okay, the values of one variable say A, are listed above the top horizontal line like here okay, the values of A are listed above the top horizontal line, this is top horizontal line. Okay, and the values of the other variables say B are listed on the left side.


So here they are listed, the 2 values of B, B and B' okay, four possible minterms okay, with variables A and B, what are the minterms? There are 4 minterms, AB, AB', A'B, A'B' okay, so those 4 minterms are than represented by four squares, so you can see A', B' okay, this is A'B', then AB', this is AB' and then A'B okay, this is A'B and then AB, this is AB.

Now if you use the value of A=1 then value of A dash will be 0, value of B if you take as 1 value of B' will be 0, so we can use the alternate Karnaugh map, this one also to find the desired output, here instead of A and B and A', B' we use their values. Okay, so A has value 1, A' has value 0, B has value 1, B' has value 0. Okay, then 0, 0, this is A', B' okay, A' has value 0, B' has value 0, so A', B' 0, 0 means A', B' 1, 0, 1 0 means AB' okay and then 0, 1 means, 0, 1 means A'B, 1, 1 means AB okay, so this also can be use.

(Refer Slide Time: 19:26)
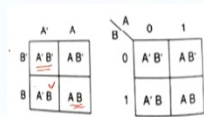
### Adjacent squares

Squares are said to be adjacent if the minterms that they represent differ in exactly one literal. For instance the squares representing  $A'B$  is adjacent to the squares representing  $AB$  and  $A'B'$ ,



Now, let us define adjacent squares, which squares are called adjacent, okay, so squares are said to be adjacent if the minterms that they represent define in exactly one literal. Okay, two squares will be called adjacent, if the minterms that they represent. Okay, differ in exactly one literal. For instance, the squares representing  $A'B$  okay, you can see here  $A'B$  okay, representing  $A'B$  it is adjacent to this one  $AB$  because  $A'B$  differs with  $AB$  only in one literal, okay, and here  $A', B'$  and  $A'B$  differs with  $A'B'$  only in one literal that is  $B$  okay. So this square  $A'B$  this square is called adjacent to the square representing  $AB$  and the square representing  $A'B'$ , okay, so we can easily see which square is adjacent to which one using the definition of the adjacent squares, okay.

(Refer Slide Time: 20:38)


The expression can be simplified by properly combining those squares in the K-map which contain 1's. The process for combining 1's is called looping. Whenever there are 1's in two adjacent squares in the K-map, the minterms represented by these squares can be looped and it eliminates the variable that appear in complemented and uncomplemented form.

Now, let us go to how to simplify the Boolean expression using Karnaugh maps, so the expression can be simplified by properly combining those squares in the K-map which contain 1's. Okay, the process for combining, how will we combine? The process of combining 1's is called looping okay, wherever there are 1's in two adjacent squares in the K-map, the minterms represented by these squares can be looped and it eliminates the variable that appear in complemented and uncomplemented form.

(Refer Slide Time: 21:15)

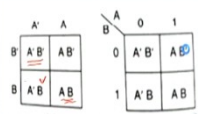**Adjacent squares**

Squares are said to be adjacent if the minterms that they represent differ in exactly one literal. For instance the squares representing  $A'B$  is adjacent to the squares representing  $AB$  and  $A'B'$ ,




Say for example here. Suppose this value is 1 and this value 1, we will consider loop about that and then we will draft that variable, which appears in complemented and uncomplemented form in the adjacent squares. So let us see how we do this.

(Refer Slide Time: 21:37)

### Example

Find Karnaugh maps and simplify the expressions:

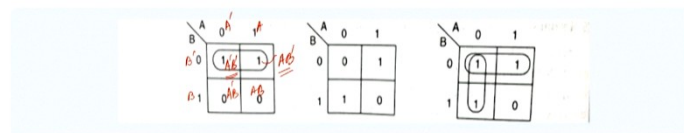- (a)  $AB' + A'B'$
- (b)  $AB' + A'B$
- (c)  $AB' + A'B + A'B'$



$$AB' + A'B' = B'$$

$$AB' + A'B = (A+A')B'$$

$$= 1 \cdot B' = B'$$

$$a \times (b+c) = a \times b + a \times c$$

$$(b+c) \times a = b \times a + c \times a$$

$$A + A' = 1$$

$$a \times 1 = a, \forall a \in B$$



For example, find Karnaugh maps and simplify this expression,  $AB' + A'B'$  okay, so let us see okay, if we have used this one. So  $AB'$  and  $A'B'$  okay, we have this. Okay, so this is  $A'$ , okay, this is  $A$  dash, this one is  $A$ , this one is  $B$  dash, this one is  $B$ , and so therefore,  $A$  dash  $B$  dash, this is  $A'B'$ . No, we have  $A'B'$  okay,  $AB'$  means  $A$  will have value 0,  $B'$  will have value, this is  $AB'$  okay, this is  $AB'$  okay and this is  $A'B'$  okay and this one is  $A'B$ , this one is  $AB$ .

Now, what is our first part  $AB' + A'B'$ .  $AB' + A'B'$  okay. Now, these two squares representing  $AB'$  and  $A'B'$  are adjacent because they differ only in one variable, that is B okay, that is A okay, so here we have A, here we have  $A'$  and  $B'$  is same, so they differ only in one variable that is A and therefore, they both have value 1, so we combine them, be it consider loop, this loop okay and then,  $(AB)' + A'B'$  will be equal to, now see, this A appears, this square it appears in the uncomplemented form, here it appears in the complemented form.

So, will consider  $AB' + A'B' = B'$  okay by using this Karnaugh method. Karnaugh method says that eliminate the variable that appear in complemented in uncomplemented form after you have taken the loop okay. So here we are considered the loop okay and then we eliminate the variable, which appears in the complemented and uncomplemented form, so

$AB' + A'B' = B'$ . Now you can also verify this by using the postulates and theorems that we have done studied so far.

So,  $AB' + A'B' = B'$ , if we use the postulates and theorems, we can write it as  $A + A'B'$  if we use the distributive formula,  $A*(B+C) = A*B + A*C$ . Okay, if we use this formula and the commutative with formula of commutative law also. Okay, because we have here the situation, by using commutative law we can write it as  $B+C*A, B+C*A = B*A + C*A$ , okay.


So using this formula  $AB' + A'B'$  can be written as  $A + A'B'$  and  $A + A'$ ,  $A + A' = 1$ , we know okay, so  $1.B'$  and we know that  $A*1 = A, \forall A \in B$ , so  $B'*1 = B'$  okay, so by using postulate theorems  $AB' + A'B'$  turns out to be  $B'$  and by using Karnaugh map also  $AB' + A'B'$  comes out to be  $B'$ .

(Refer Slide Time: 25:59)

### Example

Find Karnaugh maps and simplify the expressions:

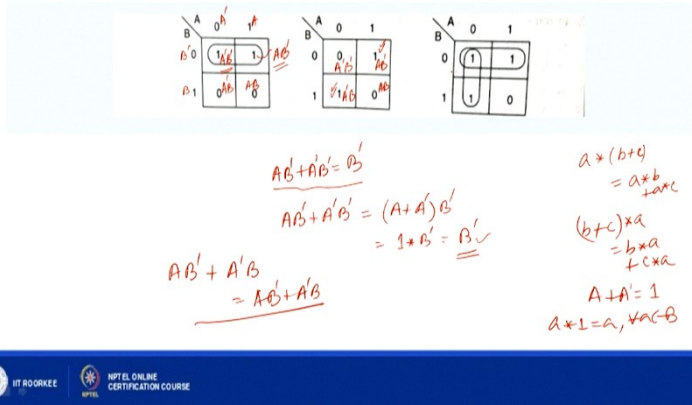- (a)  $AB' + A'B'$
- (b)  $AB' + A'B$
- (c)  $AB' + A'B + A'B'$



$$AB' + AB' = B'$$

$$AB' + A'B' = (A+A')B' = 1 \cdot B' = B'$$

$$AB' + A'B = A'B + AB' = A \oplus B$$

$$AB' + A'B + A'B' = A'B + AB' + A'B' = A'B(1) + A'B' = A'B + A'B' = A'(B+B') = A' \cdot 1 = A'$$

$a \cdot (b+c) = a \cdot b + a \cdot c$   
 $(b+c) \cdot a = b \cdot a + c \cdot a$   
 $A + A' = 1$   
 $a \cdot 1 = a, \forall a \in B$

Now, let us go to the second part is  $AB' + A'B$  okay, so  $AB' + A'B'$  okay, now this is  $A'B'$ , this is  $A'B$ , we have  $A'B$  here and we have  $AB$  here. Okay, so which squares represent  $A'B$  and  $AB'$ , is this, okay, and  $AB'$  is this. Now, so these two are not, these two squares are not adjacent okay, because that of the fact that  $AB'$  and  $A'B$  okay, they do not differ in just one literal okay, in exactly one literal, so they are not adjacent squares and therefore we cannot make looping okay, so  $AB' + A'B = AB' + A'B$  okay.

(Refer Slide Time: 27:02)

### Example

Find Karnaugh maps and simplify the expressions:

- (a)  $AB' + A'B'$
- (b)  $AB' + A'B$
- (c)  $AB' + A'B + A'B'$

Handwritten work for the three expressions:

(a)  $AB' + A'B'$ : K-map shows 1s at (A=0, B=0) and (A=1, B=0). Simplification:  $AB' + A'B' = B'$ .

(b)  $AB' + A'B$ : K-map shows 1s at (A=0, B=1) and (A=1, B=1). Simplification:  $AB' + A'B = B$ .

(c)  $AB' + A'B + A'B'$ : K-map shows 1s at (A=0, B=0), (A=1, B=0), and (A=0, B=1). Simplification:  $AB' + A'B + A'B' = A + B'$ .

Algebraic steps shown:

- $AB' + A'B' = B'$
- $AB' + A'B = (A+A')B = 1 \cdot B = B$
- $AB' + A'B + A'B' = A(B' + B) + A'B' = A \cdot 1 + A'B' = A + A'B'$
- $A + A'B' = A + B'$  (using  $A + A'B = A + B$ )

Now, let us consider the third part which is  $AB' + A'B + A'B'$ . So  $AB' + A'B + A'B'$  okay, now let us see this is  $A'B'$ , this is square represents minterm  $A'B'$ , this is represents  $AB'$  and this represents  $A'B$  okay. So here  $A'B'$  and  $A'B$ , this square and this square, they differ in exactly one literal okay, that is B okay, so they are adjacent squares and we can have looped this 1 and 1 okay, so we have this looping okay and this looping then eliminates the variable which appears in, eliminate the variable which appears in complemented as well as uncomplemented form and which is B, here it appears as B, here it appears as  $B'$ .

So,  $A'B + A'B'$  that will be equal to  $A'$  okay. Now let us consider this square, this square represents  $A'B'$  and this represents  $AB'$  then here are we see that  $B'$  is same in the two minterms that they are representing, A is occurring here in the uncomplemented form, here it



is occurring in the complemented form. So  $A'B'$ , we have considered this loop,  
 $A'B'+AB', A'B'+AB'$

when you find it will give you  $B'$  because  $A$  occurs in the complemented and uncomplemented form.

So,  $AB'+A'B+AB'$  is then the sum of this  $B'$  okay, which is the result of looping, this looping, it gives us  $B'$  okay and at the result of this looping, as the result of this looping we get  $A'$ , so we get the output as  $B'+A'$  or we can say  $A'+B'$  in the third part.

(Refer Slide Time: 29:20)

**Example**  
 Draw Karnaugh map:

$AB + AB' + A'B'$

*Handwritten algebraic simplification:*

$$\begin{aligned}
 & AB + AB' + AB' + A'B' \\
 &= (AB + AB') + (AB' + A'B') \\
 &= A(B + B') + (A + A')B' \\
 &= A \cdot 1 + 1 \cdot B' \\
 &= A + B'
 \end{aligned}$$

*Handwritten Karnaugh map:*

	$A'$	$A$
$B'$	1	1
$B$	1	1

$A'B' + AB' + AB = B' + A = A + B'$

Now, let us draw Karnaugh map for  $AB + AB' + A'B'$ , so we have seen that this is  $A'$  okay, this let us say is A, this is  $B'$  this is B okay, so the value here is 0, here the value is 1, here the value is 0, here the value is 1 okay, then  $A'B'$ , this box, this square represents the minterm  $A'B'$ , this represents the minterm  $AB'$  and it represents the minterm  $A'B$  and this square represents the minterm  $ABB$ ,  $AB$  okay, now we see  $A'B' + AB' + AB$ .

Let, us look at this square and this square okay, the two squares are adjacent because they differ in just one literal that is B okay, so this square and this square are adjacent and this is 1, 1, this is 1 okay, so we considered this loop because we give the value 1 to the minterm that is occurring here in the given Boolean expression, so  $A'B'$  is occurring here,  $AB$  is occurring here, so there squares will be represented by the 1, they will have value 1 and then we have  $A'B'$ , so this is  $A'B'$ , okay, this has a value 1 and then  $A'B'$  and  $AB'$ , this square which represents  $A'B'$  and this square which represents  $AB'$  they are also adjacent because they differ in one literal that is A okay.

So we loop 1 here, 1 here. Okay. Now, because of this looping okay, if you consider this loop first, this loop first, then as the result of this looping the value will be  $B'$  because A and  $A'$  are occurring here, so A is occurring in the complemented form, as well as uncomplemented form, so as a result of this looping  $A'B' + AB' = B'$  okay  $A'B' + AB' = B'$ , and as a result of this looping okay, as a result of this looping B is occurring in the complemented and uncomplemented form, so the result will be A okay, so  $A'B' + AB' + AB$  will be equal to  $B' + A$

okay or you can say  $A+B'$  so this is how we can use Karnaugh map to simplify this expression, this can be obtained, this output well can be obtained by using postulates also, a postulate and theorem, what we can do is.

Okay, now let us get this output  $A+B'$  by using postulates and theorems, so  $AB+AB'+A'B'$  I can also write as  $AB+AB'+AB'+A'B'$  because

$A+A=A, \forall A \in B$  okay. Now what we can do? We can combine this and this. Okay, so

$AB+AB'$  we can combine and we can combine  $AB'+A'B'$ , then this equal to, now using distributive law this is  $A*(B+B')$ ,  $A*(B+B')$  and here we get  $A+A'*B'=1$ , so  $A.1+1.B'$  and this is equal to  $A+B'$ , so that is how we can arrive at the output given by the Karnaugh map, that is all in this lecture. Thank you very much for your attention.