


Indian Institute of Science

Design of Photovoltaic Systems

Prof. L. Umanand
Department of Electronic Systems Engineering
Indian Institute of Science, Bangalore

NPTEL Online Certification Course

(Refer Slide Time: 00:17)

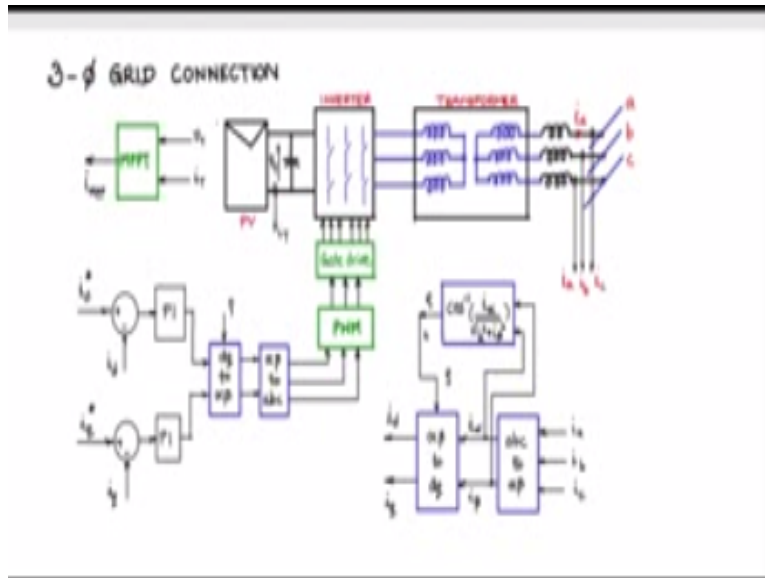

Let me now revisit the three phase grid connection to apology that we discussed earlier and see how we can apply the various transformation that we learned into this and we can do a set point controller now let me remove these unwanted lines now, because we need to introduce new blocks we are measuring the currents now I would like to rename this ryd into abc let me do that.

And induced of igr I will just use ibic so let me female that I will mark that ia I have put them as abc softer having done that renaming here also I would like to change, change that later at a proper time now this iaibic are the feedback signals these are AC signals now what you want to do with them let me put a block te inputs are ia ,ib and ic now this ia ,ib,ic which are measured A3 face AC currents .

I would like to convert them into $I \propto \beta$ two face AC currents in the $\alpha \beta$ co-ordinate system so what should I do .i should use a ABC do $\alpha \beta$ transformation and how would will be $I \propto \alpha$ and $I \propto \beta$ now this α and β I would like to transformed into the DQ co-ordinate reference time it as one

more input and that is rope the angle between α β co-ordinate and the DQ co-ordinate so what should I used here.

I should use α β to DQ transformation the output this block will be ID,IQ now as the DQ co-ordinate system is rotating along these specter the current specter ID and IQ will be C quantities ,ID and IQ are the projection of the current specter on the D axis and the Q axis respectively so these are DC quantities now we will setup the controller here now let me have a current reference +- I will call the current reference as i_d^* .

And what do I feedback I will feedback this i_d here, I will not draw the line so that it will clutter up the place I will just indicate i_d . So it means that I have connected this line, now output of the comparator goes to a pi controller so simple pi controller. Now I will do that for i_q also, so I will have here i_q^* and feedback i_q which means I will be feeding back this line here, plus and minus and goes to another pi controller block.

Now outputs of these two are suppose to actually generate finally the pwm, which will generate the voltage to appropriately drive the current, so the output of the pi are basically the d and q axes voltages, the voltages in the d and q axes, so let me do at dq to α β the outputs of the two controllers. One of the controllers the d axes portion of the controller is giving you v_d let us say q axes portion the controller give v_q this will go through a dq at α β transformation and I will get 2 outputs, these two outputs are let us say v_α and v_β this is the same ρ which I have used here because the dq and α β are having the same different angle. Now α β to a b c I will do one more transformation which will give me the reference v_a v_b v_c .

So I will draw these lines so this will be giving me the reference v_a , v_b , v_c to the PWM which will have the carrier triangle compare and then generate the necessary PWM signals for the gate drive to go and switch on and off these switches accordingly and supply a voltage here such that i_a , i_b , i_c flows according to this control which we have given such that this error here and here becomes 0.

So this is the control principle that we use, now I will remove those three quantities and output of the MPP I will use a single output of the MPP to indicate to represent i_{MPP} I at maximum power point and let me see what I have to do with that ultimately I have to give it as a references to i_d^* I will discuss that a bit later but right now the MPP will taking v_d and i_d and use the power


calculated to and the MPPT algorithm to give out an output which we will call it as i_{MPP} which represents the current at maximum power.

Now what is remaining is how to obtain and give the value of θ to these two blocks this is and defined as z , so θ we said was the angle between the $\alpha\beta$ axis, co-ordinate axis and the dq axis and we know that we want that the dq axis to be rotating along the space vector current space vector so if the dq co-ordinate system is also rotating along the current space vector then the current space vector and the dq axis are sink annoyed and rotating together and therefore the idea i_q will be dc.

Therefore what we will do, we will take i_α i_β and generate ρ so the angle of the current space vector will be ρ let us say. So let me say $\cos^{-1} \frac{i_\alpha}{\sqrt{i_\alpha^2+i_\beta^2}}$ is the block will give me ρ , so what should be the input I will take the input from i_α and i_β as indicator the output will be ρ and that output I will use here and the same output I will also use here, so I have ρ . So in this case the i_d will get aligned along the current space vector i_q will be 0 because i_d is aligned along the current space vector itself there will not be any quadrature component so this can be 0 and the only the i_d controller will exist.

However, this is one way of obtaining ρ but we would like to see that the currents which are flowing air or in phase with the voltage, so it is it would be appropriate to taking the voltage wave shapes, wave forms v_a , v_b , v_c and use the voltage wave forms to obtain ρ then i_d and i_q will be such that it will be with the respect to the voltage space vector as the d axis, what is the advantage we will see and I will discuss that shortly. Let me now focus on this aspect on this generation of ρ .

(Refer Slide Time: 09:44)

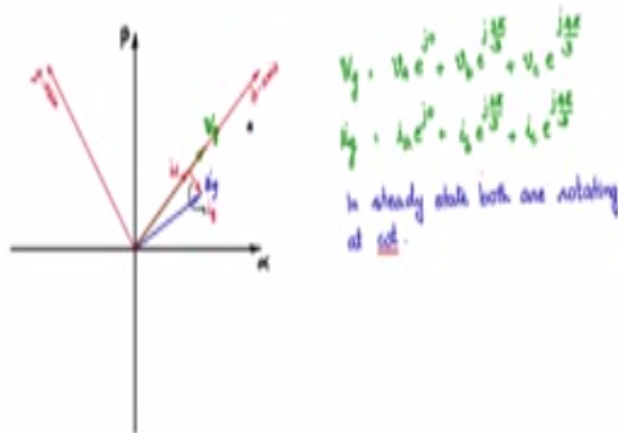

Consider the special co-ordinates $\alpha\beta$ because $\alpha\beta$ co-ordinate system and in that co-ordinate system let me have a voltage space vector shown like that, that is a resultant voltage space vector and this voltage is the grid voltage and likewise I will also have another space vector the grid current, this is the resultant meaning that it is composed of $V_A V_B V_C$ and this is composed of $I_A I_B I_C$ and resulting in this space vector in fact you can write down the V_g vector is given by $V_A e^0 + V_B e^{j2\pi/3} + V_C e^{j4\pi/3}$ we know how to do this you will land up with $\beta\alpha + j b\beta$ likewise I can also get the current space vector $I_A e^0 + I_B e^{j2\pi/3} + I_C e^{j4\pi/3}$ in this study state both the voltage space vector.


And the current space vector or rotating at ωd angle now let me position the q axis write the position that d axis so I am positioning that d axis which is aligned along the voltage space vector V_g so this is our d axis and the q axis is orthogonal to the d axis and that is the q axis and if you do this you will see that because the d_q axis is aligned along the V_g space vector and it is rotating along with the V_g space vector there is no quadrature component of the voltage space vector only V_d is there.

Because there is no projection on to the quadrature axis so V_g magnitude will be V_d that is the dc value now I_g is let us say lacking V_g by some angle it is having two components and the projection of I_g on to the d axis and the orthogonal component, so this portion is projection will be I_d the direct component and that would be the quadrature component I_q so the current space

vector can be resolved into I_d and I_q now let us say we put the requirement that the current that is pumped into the grid I_g should be in phase with V_g .

Then I_g and V_g should be aligned so what does it mean from the control point of view it means that I_q should be 0, so I go and set the I_q star send point to 0 then in the steady state I_q will be 0 so I_d will be same as I_g and it will be in line with V_g and then you will see that the current is pumped into the grid in unity power factor, so this is the advantage you would get if you aligned d axis along V_g so now let us do this updation in the three phase grid connected block diagram grid connected in.

(Refer Slide Time: 14:08)

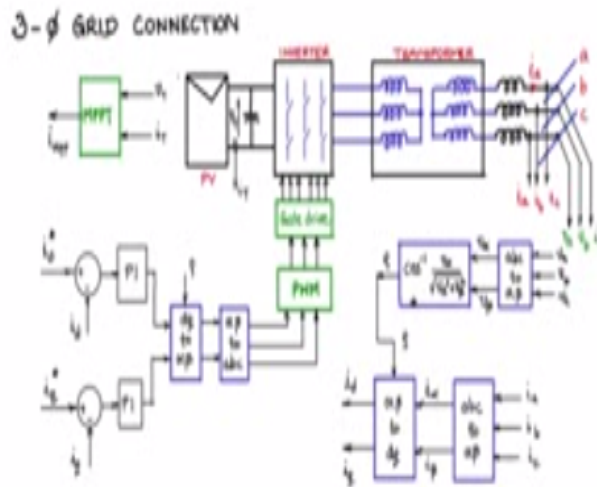


As we discussed is now let me make the update for the row generation block instead of aligning it along the current space vector I will align it along the voltage space vector for the modification is as follows let me first remove the current inputs I will shift that out of bit make some space and then I will measure the phase voltages V_A V_B and V_C I will have block here I am going to take an input V_A V_B V_C and have a abc to α β transformation just like this and output how the VBC to α β will give me V_α V_β and I will use $V_\alpha / \sqrt{V_\alpha^2 + V_\beta^2}$ to generate ρ .

So now this ρ is giving the space vector position of the voltage V_A V_B V_C composed into I will now update this ρ generation block instead of ρ being the current space phaser angle I would like to replace it with the voltage space spacer angle, so for that let me remove this let me move this up to clear up some space and then let me taken the voltage measurements these are the phase

voltages V_A V_B and V_C and I will have a block here and this block will take an inputs V_A V_B V_C and I will use a abc to α β transformation.

I will get at the output of this block V_α and V_β I will use V_α V_β to determine the ρ which will be the angle of the voltage space phaser $V_\alpha / \sqrt{V_\alpha^2 + V_\beta^2}$ will give you the angle ρ this angle ρ will give the displacement of the voltage space vector from the α β from the α axis.

(Refer Slide Time: 16:52)

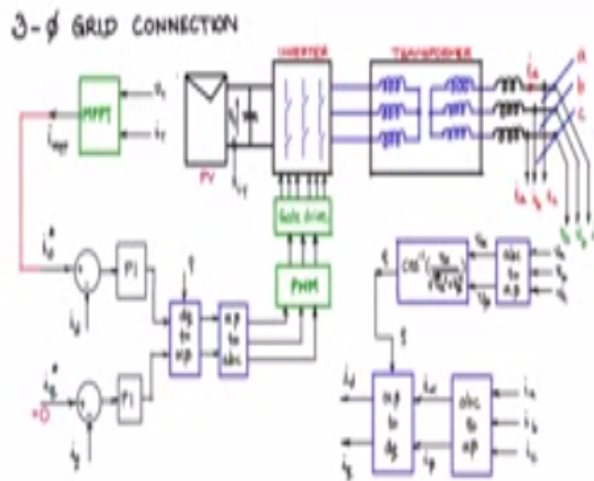

Now when you have to look at this voltage space vector so now the b axis is aligned along the voltage space vector V_g because we have taken this ρ and we see that the current has now to be controlled in such a way that I_q is made 0, so that the current space vector also aligned itself so we can now go to the block diagram make this set point 0, if you make this set point then the state is state you will see that I_q will reach 0 that p_i controller will see in to that the error here is 0 which means I_q will become 0.

I_q is 0 then with means the currents that are being fed in will be in phase and I_d is representing the current space vector because I_q is 0 now in that case the output can directly dictate the set point for I_d are I_d so now I_d 's are actually the set point which defines dictates the current that are being pumped into the grid.


It dictates the total overall space current space vector that is fed into the grid as the grid voltage is fixed by the grid the current actually will dictate how much amount of power is being put into

the grid therefore if I_d is actually representing the peak power point of the pv panel then the maximum power is put into the grid.

So let us say this block which is taking the terminal voltage of the pv modular and the pv current into it and the power calculated based on V_t it is used for determining the maximum power point the output of torque is now connected to I_d like this say and I_d is representing the value to which is indicating the maximum power point so this I_d is used as a set point and why do you tried to match it on the in such a way.

That maximum current can be fed into grid and the grid can be the voltage which needs that maximum power is being into the grid so in this way also integrated iteratively within the inverter control the computation of this row by this method here is algebraic it is also open loop so it is not resilient to harmonics which are there in the remains voltage is formed it is not resilient to surges to spikes, noise, and due to various many uncertainties which may cause the ρ value to drift, so to make it more robust a close loop modification is suggested it is also call the pll, let us see how it works.

(Refer Slide Time: 20:34)

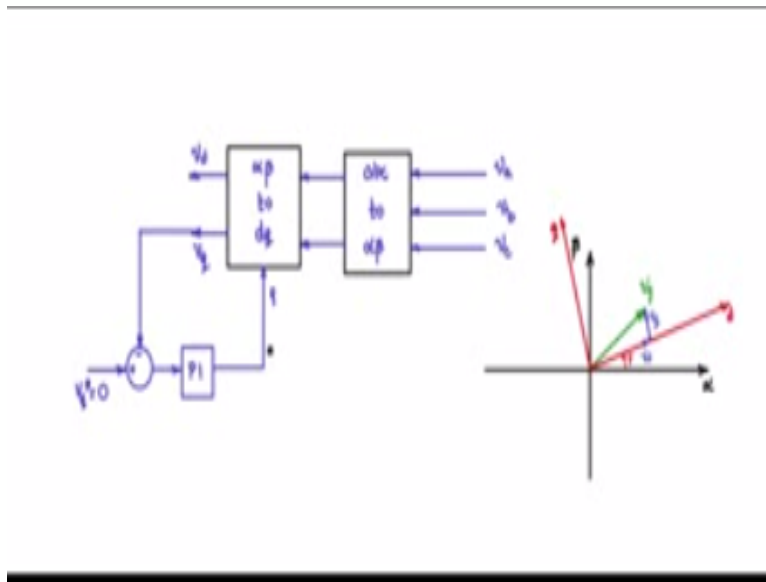

Consider the phase voltages $v_a v_b v_c$ I will pass it through a b c to $\alpha \beta$ transformation I will get $v_\alpha v_\beta$, and I will pass that to $\alpha \beta$ to deuce transformation and I will get $v_d v_q$, now there is ρ requirement here how will like you this ρ by the following method so let me built a small

controller here, I will set v_q^* I will say this is the set point $v_q^* = 0$ and then I will feedback the v_q which is coming out of this $\alpha \beta$ to dq block.


And the error I pass it through a pi controller and deviate as ρ how does this work? This is like a pll it is also call pll in many literature, let me visualize the coordinate system and I have $\alpha \beta$ coordinate system and let me have a voltage space vector like this v_g of the grid voltage. Now let us say that the d axes is miss align like this it is not aligned along the v_g space vector, it is missed aligned by some angle and as a consequence the projections on the d axes will give the v_d and v_q , so there is a VQ component also if it had been aligned along v_g if d axes had been aligned along v_g then v_q component would have been 0, now this is ρ , ρ is nothing but the angle between the $\alpha \beta$ coordinate and the dq coordinate.

Now let us see how this works, now let us say due to some reason due to many uncertainties the dq axes is miss aligned with respect to the voltage space vector which means v_q is not 0 then this compares with the v_q it goes negative the pi controller will become active it will initiate a ρ change in to initiate a ρ change in such a direction that the input to the pi controller which is the error will 10 to 0.

If this tends to 0 then v_q here will 10 to $v_q^* = 0$ that is the command value or the represent value, we are said $v_q^* = 0$ therefore v_q will tend to 0 so the pi controller will see to it that v_q will tend to 0 which means the ρ will keep adjusting it will adjust such that it will aligned the d axes along the voltage space vector, and such a value of ρ will come up out because of the control action such that v_q here will become 0.

Under such condition the ρ value here is the correct value of ρ which will give you the value of the difference between the d q axes coordinates system and the $\alpha \beta$ coordinate system such a way that d axes is aligned along the voltage space vector, which is what we would like to have. This is a very robes mechanism because it is close loop and then there is a pi component there is history in it which will filtering effect on harmonings, surges, spikes and such than uncertainties. So if we incorporate this modification in to our entire 3 phase grid connected inverter block diagram then it will be a complete workable solution, let us do that.

(Refer Slide Time: 24:52)

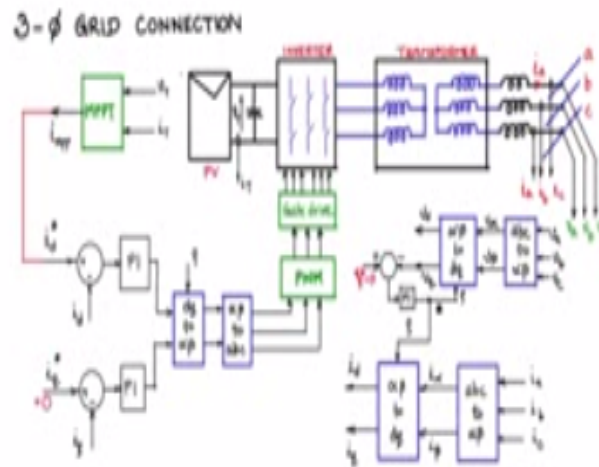

Let us now modify this ρ generation which is open loop and not very robust and is also algebraic we will replace this with the close loop pll based type of technique that we just discussed let me do that let me erase out this blocks let me clear, now let me first start with the a b c $v_a v_b v_c$ which are the phase voltages I will do a a b c to $\alpha \beta$ conversion transformation which will give me $d \alpha$ and $d \beta$, and I will pass it through an $\alpha \beta$ to dq transformation which will give me v_d and v_q I will not do anything with v_d .

I will now introduce a control mechanism this is the reference plus minus v_q is given as the feedback to the control mechanism. The error is given to a v_i controller which will generate the ρ for the dq block it will generate \sin such a way that v_q will go and take the value set by this reference. Now this ρ value I can take it up and then connected here, now this v_q start set point for this control mechanism will set pq start to 0 as I discussed so that eventually v_q will reach v_q^* .

So v_q will become 0 in which case v_d will be aligned along the voltage space vector and because you are going to use this ρ for all your $\alpha\beta$ to dq conversion that dq axes will be taking this value of ρ and therefore will be aligned along the voltage space vector. So we have now here the complete block diagram of the three phase grid connected inverter topology and which take \sin to account all issues.

And this is an implementable block it contains dq transformation it contains the dq axes theory principles frame transformations from the 3 phase to two phase AC to dq and having set point controller the number of controllers are only two as against three in the AC control tracking

control, we now have MPPT integrated in to the inverter and the power block is simple it has just only one power stage and then we have a robust pll based ρ determination algorithm.